

- כל חומר עזר מותר
- אין להעביר חומר בין הנבחנים
- שימוש במחשבוניס כולל מחשב מטלטל מותר

השאלות מתייחסות לדפי מפרט של LM2698.
יש לענות על 3 מתוך 4 השאלות הנתונות.

שאלה מס' 1

השאלה מתייחסת למעגל בעמוד ראשון.

מניחים $V_{in}=4.5V$, נגד עומס - 40Ω .

1.1 (50%)

חשב את A_p לסליל בהנחה $K=0.4$; $J=4.5 A/mm^2$; $B_{max}=0.2 Tesla$

1.2 (50%)

בהנחה ש- (זו איננה התוצאה הנכונה של סעיף 1.1) $A_p=245 mm^2$; $l_e = \sqrt{6A_w}$, $\frac{A_w}{A_e} = 5$
והפסדי גרעין לפי: $P = f^2(\Delta B_{pp})^2 10^{-7} (mW/cm^3)$ חשב הפסדי הגרעין.

שאלה מס' 2

השאלה מתייחסת לשרטוט 6 בעמוד 13. מניחים עומס 50Ω ומתקיים: $\frac{i_L}{v_C} = 3 A/V$ (אות קטן ממוצע)

2.1 (65%)

שרטט A_{OL} ו- $1/\beta$ של המערכת ומצא רוחב הסרט של $\beta A_{OL}(f_0)$.

2.2 (35%)

הסבר איכותית מה התלות של f_0 בנגד העומס ב- CCM ו- DCM.

שאלה מס' 3

השאלה מתייחסת לשרטוט מס' 7 בעמוד 14.
מניחים שמתח הכניסה – 5V והעומס 10Ω .

3.1 (50%)
שרטט צורת הזרם בכל אחד מהסלילים, בדיודה וצורת המתח ברגל 5 של הבקר.

3.2 (25%)
תן הערכה להפסדי ההולכה במתג ($R_{dsON} = 0.3\Omega$) ובדיודה ($V_d = 0.4V$).

3.3 (25%)
חשב באיזה הספק מוצא יכנס הממיר למצב DCM (בהזנחת ההפסדים).

שאלה מס' 4

4.1 (33%)
שרטט מעגל ממוצע מקורב של שרטוט מס' 6 בעמוד 13. נגד העומס - 50Ω . מניחים שקבועי המערכת (למשל K_S, M_C) ידועים.

4.2 (33%)
הסבר כיצד תמדוד את הגבר החוג, אימפדנס מוצא (לאות קטן) ודחיית אות AC קטן מפריע בכניסה $\left(\frac{V_O}{V_{IN}} \right)$.

4.3 (34%)
הסבר עקרונית מה הצעדים הדרושים כדי לחלץ ביטוי אנאליטי לפונקצית התמסורת $\frac{i_L}{v_C}$ (אות קטן ממוצע).

Problem 1

$$V_{in} := 4.5V$$

$$L := 10\mu H$$

$$mT := 10^{-3}T$$

$$R_o := 40\Omega$$

$$V_o := 12V$$

$$mW := 10^{-3}W$$

1.1

Find A_p for the inductor. Assume $K := 0.4$, $J := 4.5 \frac{A}{mm^2}$, $B_{max} := 0.2T$

$$A_p = A_w \cdot A_e = \frac{L \cdot I_{pk} \cdot I_{rms}}{J \cdot K \cdot B_{max}}$$

For Boost topology:

$$\frac{V_o}{V_{in}} = \frac{1}{1-D}$$

$$D := \frac{V_o - V_{in}}{V_o}$$

$$D = 0.63$$

$$I_o := \frac{V_o}{R_o}$$

$$I_o = 0.3 \text{ A}$$

Pin FSLCT is grounded, so switching frequency $f_{sw} := 600kHz$.

$$\Delta I := \frac{V_{in} \cdot D}{L \cdot f_{sw}}$$

$$\Delta I = 0.469 \text{ A}$$

Output current for CCM \rightarrow DCM condition is $\frac{\Delta I}{2} \cdot (1-D) = 0.088 \text{ A} < I_o$, so the converter is operating in CCM.

$$I_{pk} := \frac{I_o}{1-D} + \frac{\Delta I}{2}$$

$$I_{pk} = 1.034 \text{ A}$$

$$I_{Lav} := \frac{I_o}{1-D}$$

$$I_{Lav} = 0.8 \text{ A}$$

RMS current $I_{rms} = \sqrt{I_{av}^2 + I_{ac}^2}$, for triangular wavelshape I_{ac} is approximately $\frac{\Delta I}{\sqrt{12}}$

$$I_{rms} := \sqrt{I_{Lav}^2 + \frac{\Delta I^2}{12}}$$

$$I_{rms} = 0.811 \text{ A}$$

$$A_p := \frac{L \cdot I_{pk} \cdot I_{rms}}{J \cdot K \cdot B_{max}}$$

$$A_p = 23.313 \text{ mm}^4$$

1.2

Assuming $A_p := 245 \text{ mm}^4$, $l_e = \sqrt{6 \cdot A_w}$, $A_w = 5 \cdot A_e$, find core dissipation if

$$P_v = \left[f^2 \cdot (\Delta B_{pp})^2 \cdot 10^{-7} \right] \frac{\text{mW}}{\text{cm}^3}$$

$$P_{core} = P_v \cdot V_e$$

$$V_e = A_e \cdot l_e = A_e \cdot \sqrt{30 \cdot A_e}$$

$$A_p = A_w \cdot A_e = 5 \cdot A_e^2$$

$$A_e := \sqrt{\frac{A_p}{5}}$$

$$A_e = 7 \text{ mm}^2$$

$$V_e := A_e \cdot \sqrt{30 \cdot A_e}$$

$$V_e = 0.101 \text{ cm}^3$$

$$\frac{\Delta B}{B_{max}} = \frac{\Delta I}{I_{pk}}$$

$$\Delta B := B_{max} \cdot \frac{\Delta I}{I_{pk}}$$

$$\Delta B = 90.6 \text{ mT}$$

$$P_{core} := (600 \cdot 10^3)^2 \cdot (0.0906)^2 \cdot 10^{-7} \cdot 0.101$$

$$P_{core} = 29.8$$

Core dissipation - 29.8 mW

Problem 2

$$R_o := 50\Omega \quad \frac{i_L}{v_c} = 3 \frac{A}{V} \quad R_{FB1} := 1M\Omega \quad R_{FB2} := 140k\Omega$$


$$V_{in} := 3V \quad V_o := 10V \quad R_c := 20k\Omega \quad C_c := 4.7nF$$

$$C_o := 10\mu F \quad \mu S := 10^{-6}S$$

2.1

Draw A_{OL} and $1/\beta$. Find the bandwidth of $\beta A_{OL} - f_0$.

The output filter for small signal is:

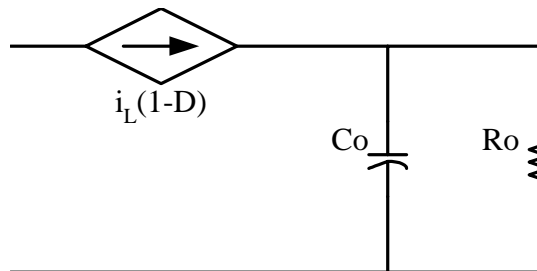

Transfer function A_{OL} defined by:

$$A_{OL} = \frac{v_o}{v_c} = \frac{v_o}{i_L} \cdot \frac{i_L}{v_c}$$

$$v_o = i_L \cdot (1-D) \cdot Z_o \quad Z_o = \frac{1}{\frac{1}{R_o} + j\omega \cdot C_o}$$

$$A_{OL} = \frac{(1-D) \cdot R_o}{1 + j\omega \cdot C_o \cdot R_o} \cdot 3 \frac{A}{V}$$

$$D := \frac{V_o - V_{in}}{V_o}$$

$$D = 0.7$$

The pole in A_{OL} : $f_p := \frac{1}{2\pi \cdot C_o \cdot R_o}$

$$f_p = 318.31 \text{ Hz}$$

$$A_{OL}(f) := \frac{(1-D) \cdot R_o}{1 + j \cdot \frac{f}{f_p}} \cdot 3 \frac{A}{V}$$

$$A_{OL}(0\text{Hz}) = 45$$

The transconductance of error amplifier $g_m := 135 \mu S$

Transfer function of error amplifier with compensation network:

$$\beta_c = \frac{v_c}{v_{FB}} = \frac{i_c \cdot Z_c}{v_{FB}} \quad \frac{i_c}{v_{FB}} = g_m \quad Z_c = R_c + \frac{1}{j\omega \cdot C_c}$$

$$\beta_c = g_m \cdot Z_c = g_m \cdot \left(R_c + \frac{1}{j\omega \cdot C_c} \right) = g_m \cdot R_c \cdot \left(1 - j \cdot \frac{f_c}{f} \right)$$

Where $f_c := \frac{1}{2\pi \cdot C_c \cdot R_c}$

$f_c = 1.693 \text{ kHz}$


Transfer function β from v_o to v_c :

$$\beta = \beta_c \cdot \frac{v_{FB}}{v_o} = \beta_c \cdot \frac{R_{FB2}}{R_{FB1} + R_{FB2}}$$

$$\beta(f) := g_m \cdot R_c \cdot \frac{R_{FB2}}{R_{FB1} + R_{FB2}} \cdot \left(1 - j \cdot \frac{f_c}{f} \right)$$

$start := 1 \quad stop := 6 \quad N := 100$

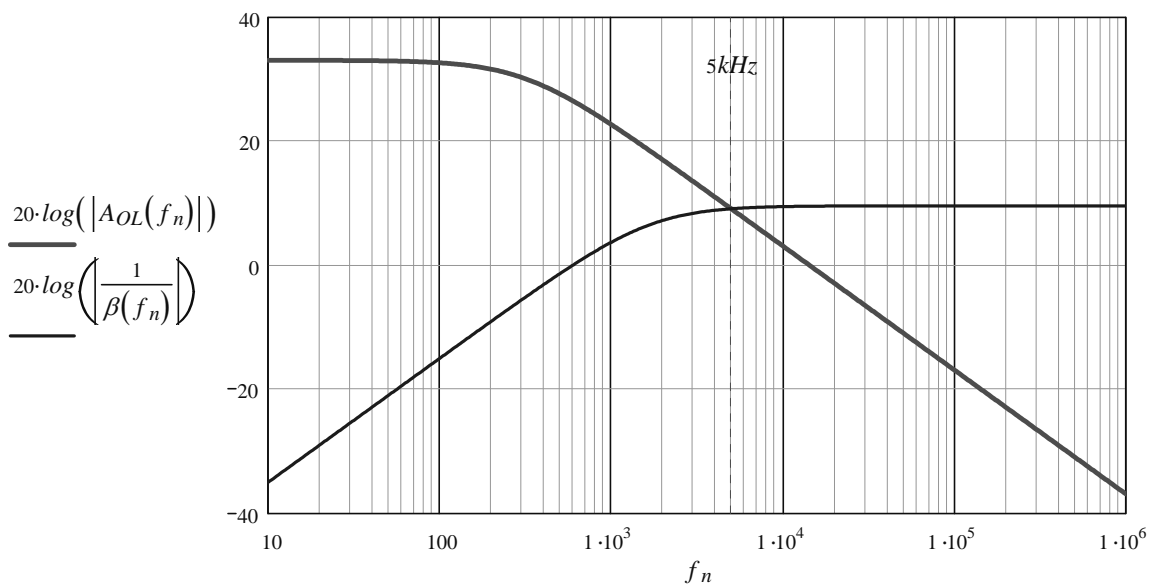$n := start \cdot N .. stop \cdot N \quad f_n := 10^{\frac{n}{N}} \text{ Hz}$



The bandwidth of close loop system - $f_o = 5 \text{ kHz}$

2.2

From the equation of A_{OL} it's clear that in CCM, for high frequencies (greater than f_p) valid $1/R_o \ll 2\pi f C_o$, Therefore R_o is not effecting f_0 .

$$A_{OL} = \frac{(1-D) \cdot R_o}{1 + j\omega \cdot C_o \cdot R_o} \cdot 3 \frac{A}{V} = \frac{(1-D)}{\frac{1}{R_o} + j\omega \cdot C_o} \cdot 3 \frac{A}{V}$$

In DCM the inductor behaves like current source, that's why R_o has no effect on bandwidth f_0 .

Problem 3

$$V_{in} := 5V$$

$$V_o := 3.3V$$

$$L := 10\mu H$$


$$R_o := 10\Omega$$

$$V_d := 0.4V$$

$$f_{sw} := 1.25MHz$$

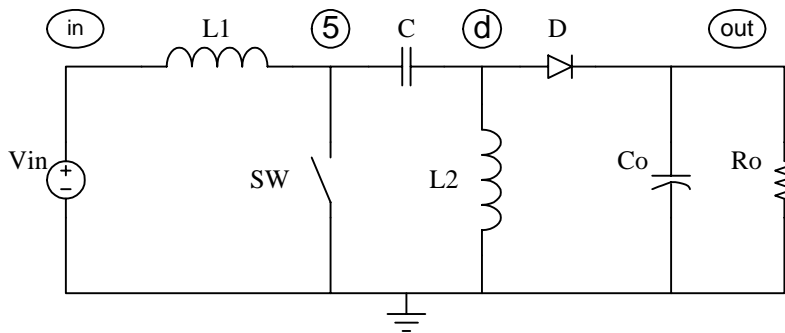3.1

Draw the waveforms of currents through inductors and diode and voltage on pin 5



Average voltage on both inductors must be zero. Therefore average voltage on the node "5" is V_{in} and average voltage on the node "d" is zero. Then the average voltage on the capacitor C is V_{in} .

When the switch is conducting, current through $L1$ and $L2$ grows linearly with the slope $V_{in}/L1$ and $V_{in}/L2$ (voltage on the node "5" is zero and voltage on the node "d" is $-V_{in}$).

When the switch is off voltage on the node "5" is $V_{out} + V_d + V_{in}$, therefore the current through $L1$ decreases linearly with the slope $(V_{out} + V_d)/L1$; voltage on the node "d" is $V_{out} + V_d$ and the current through $L2$ decreases with the slope $(V_{out} + V_d)/L2$.

Average voltage on capacitor C is constant (V_{in}) therefore average current through it is zero. Then the average current through inductor $L2$ is equal to the average output current I_o .

$$D := \frac{V_o + V_d}{V_{in} + V_o + V_d}$$

$$D = 0.425$$

$$I_o := \frac{V_o}{R_o}$$

$$I_o = 0.33 A$$

$$\Delta I = \Delta I_1 = \Delta I_2$$

$$\Delta I := \frac{V_{in} \cdot D}{L \cdot f_{sw}}$$

$$\Delta I = 0.17 \text{ A}$$

$$I_2 := I_o$$

$$I_2 = 0.33 \text{ A}$$

Neglecting losses we have:

$$I_1 := \frac{V_o \cdot I_o}{V_{in}}$$

$$I_1 = 0.218 \text{ A}$$

$$I_{1pk} := I_1 + \frac{\Delta I}{2}$$

$$I_{1pk} = 0.303 \text{ A}$$

$$I_{2pk} := I_2 + \frac{\Delta I}{2}$$

$$I_{2pk} = 0.415 \text{ A}$$

$$I_{dpk} := I_{1pk} + I_{2pk}$$


$$I_{dpk} = 0.718 \text{ A}$$

$$\Delta I_d := 2\Delta I$$

$$\Delta I_d = 0.34 \text{ A}$$

$$V_{5max} := V_o + V_d + V_{in}$$

$$V_{5max} = 8.7 \text{ V}$$

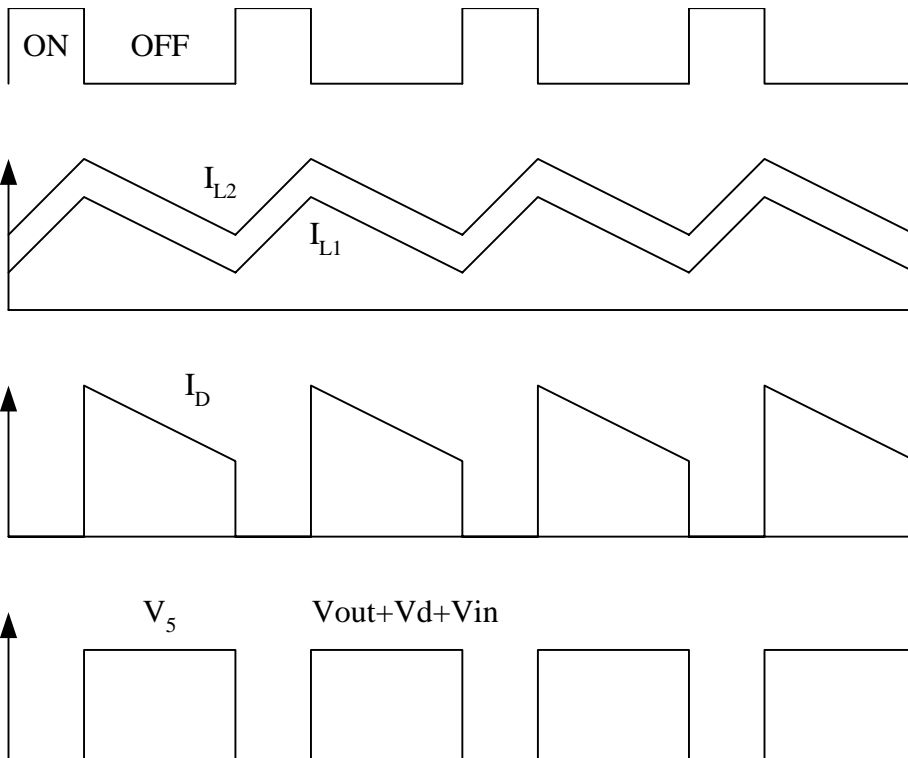

3.2

Give estimation for conduction loss in the switch and diode if $R_{ds_{on}} := 0.3\Omega$

The RMS current through the switch:

$$I_{sw_{rms}} := \sqrt{D \cdot \left(I_I^2 + \frac{\Delta I^2}{12} \right)}$$

$$I_{sw_{rms}} = 0.146 \text{ A}$$

$$P_{sw} := I_{sw_{rms}}^2 \cdot R_{ds_{on}}$$

$$P_{sw} = 6.36 \text{ mW}$$

The average current through the diode (when the diode is conducting):

$$I_{d_{av}} := \frac{I_o}{1 - D}$$

$$I_{d_{av}} = 0.574 \text{ A}$$

$$P_d := I_{d_{av}} \cdot V_d \cdot (1 - D)$$

$$P_d = 132 \text{ mW}$$

3.3

What output power will drive the converter into DCM ?

Input average current is less than the output one, therefore L1 will be in DCM first. This happens when

$$I_I = \frac{\Delta I}{2}$$


$$P_{o_{DCM}} = P_{in_{DCM}} = V_{in} \cdot I_{in} = V_{in} \cdot \frac{\Delta I}{2}$$

$$V_{in} \cdot \frac{\Delta I}{2} = 425 \text{ mW}$$

Problem 4

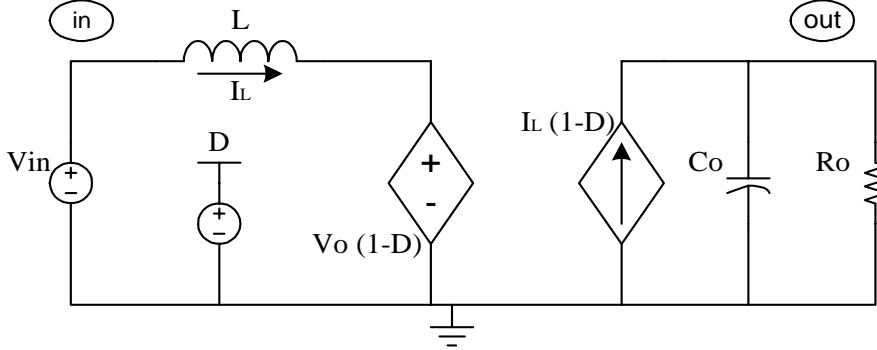4.1


Draw average model for the Boost converter (Fig. 6). $R_o = 50\Omega$, coefficients (like K_s , M_c) are known.



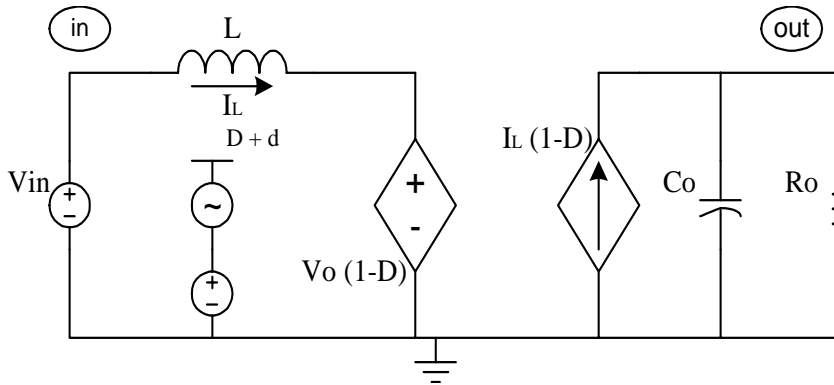
4.2

Explain how to measure transfer function, output impedance and rejection of input AC signal (v_o/v_i).


Insert AC source in series with operating point DC source of D and measure transfer function v_o/d



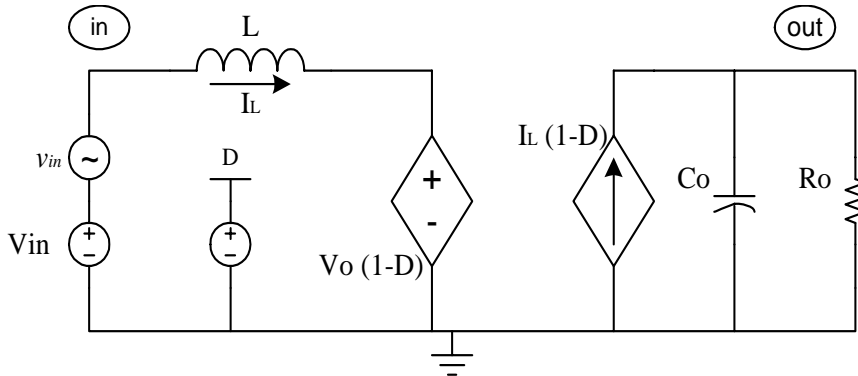Insert AC source in series with operating point DC source of V_{in} and measure rejection of input AC signal v_o/v_i





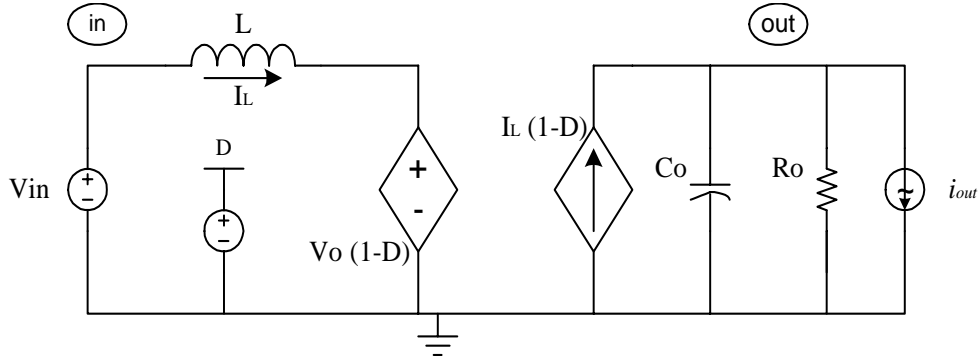Insert AC source in parallel with the DC load and measure output impedance i_o/v_o



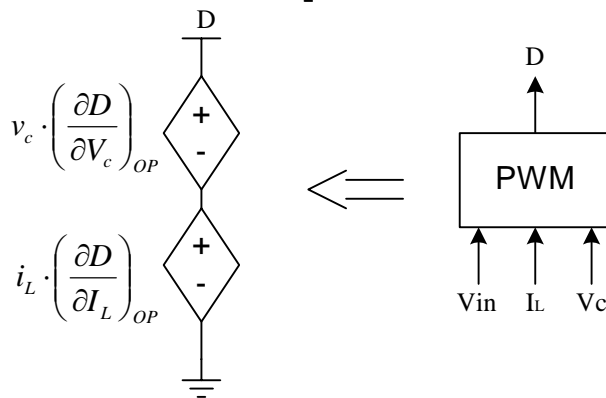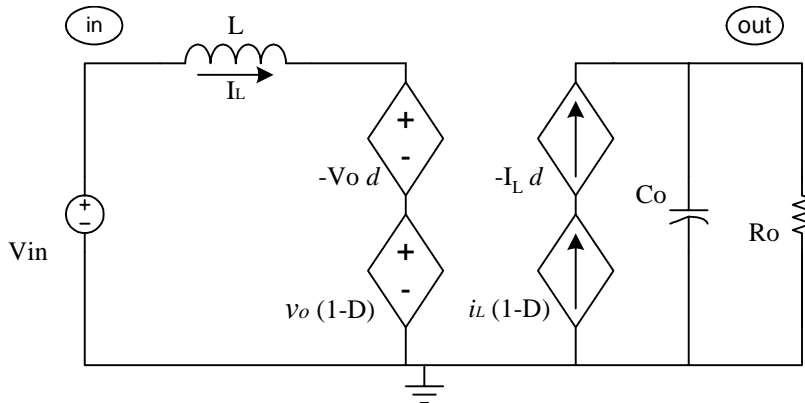4.3

Explain what are the desired steps to derive the analytical expression for transfer function i_L/v_c



Using this circuit with partial derivatives of V_c , I_L , V_L , I_D and V_{in} (equals to zero!) in the operating point it's possible to derive the analytical expression for transfer function i_L/v_c .