

*Training Exercises
to Laboratory Works*

Introduction

Simulation run time is based on the time required to establish the steady state of process under study.

The proposed exercises can start with 10-15 periods (200-300mS)

Maximum step size : 20-30uS for 50Hz..

Figures report should be submitted only 2-3 last period.

Figures report should be kept only major grid.

When printed on a black - white printer, the currents and voltages waves in the figures of the report should be named in the appropriate manner.







Experiment No.1

1. Construct schemes in SPICE: separately for Thyristors, separately for TRIAC's and separately for MOSFET;
2. Spend simulations (Thyristor and TRIAC circuits)at different values of parameters RC - ignition circuit and compare results (6÷8 variants);
3. Compare gate voltage (V_G , V_{G2} and V_{G3} , V_{G4}) at pulse excitation and excitation from RC - ignition circuit;
4. Spend simulations (TRIAC) at different values of parameters L_o , R_o and compare results;
5. Simulation results presents the report on template form for experiment No.1

PARAMETERS:

$R_c = [1k, 2.5k, 5k, 7.5k, 10k]$
 $R_{c1} = 1k$
 $R_{c2} = 1u$
 $ig_deg = 60$
 $ign = (ig_deg/360*20m)$
 $Vp1s = 10$
 $Tw = 3m$
 TRIAC 2N6348
 $V_{drm} = 600v$ $I_{drm} = 10u$ $I_h = 6ma$
 $dVdt = 1000e6$ $I_{on} = 1.5u$
 $I_{gt} = 12ma$ $V_{gt} = 0.9v$ $V_{tm} = 1.3v$ $I_{tm} = 11A$

Ro1, Ro2, Ro3, Ro4 -- [10-70] Ohm

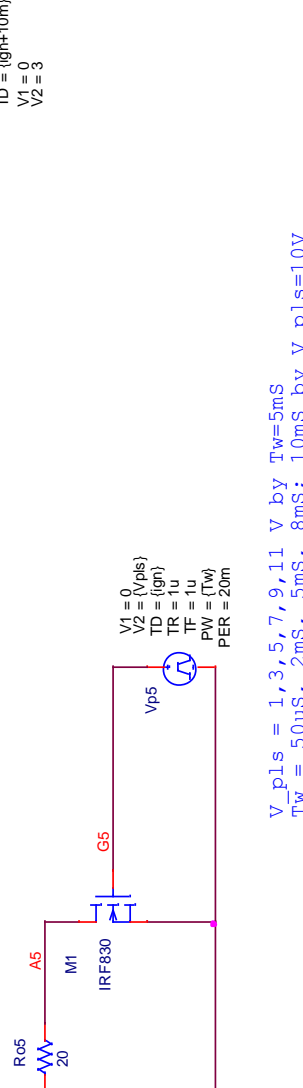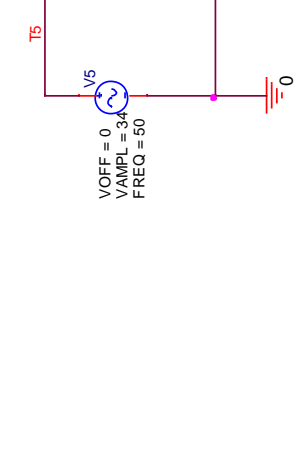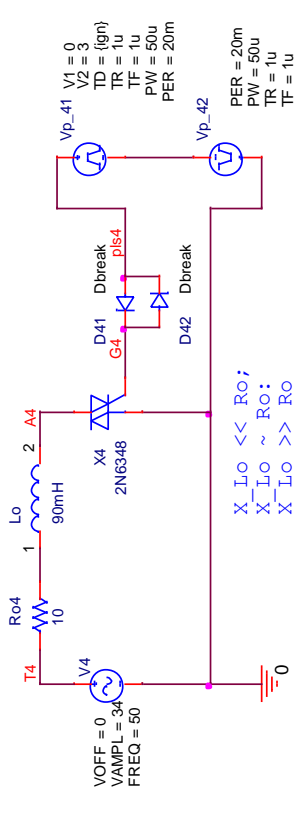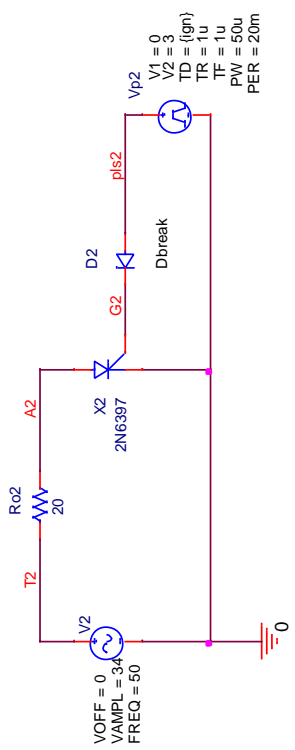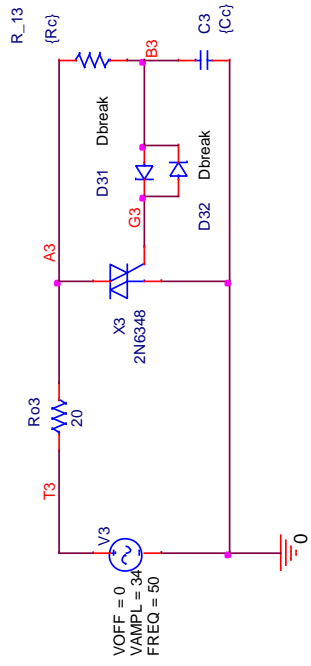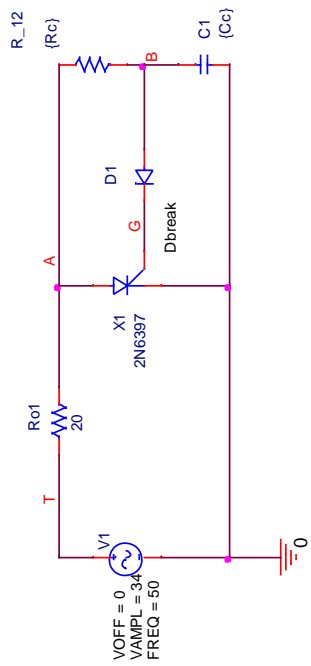

$V_{p1s} = 1, 3, 5, 7, 9, 11$ V by $Tw = 5ms$
 $Tw = 50\mu s, 2ms, 5ms, 8ms, 10ms$ by $V_{p1s} = 10V$

$V1 = 0$
 $V2 = 0$
 $TD = (ign)$
 $TR = 1u$
 $TF = 1u$
 $PW = 50u$
 $PER = 20m$

$X_{Lo} \ll Ro;$
 $X_{Lo} \sim Ro;$
 $X_{Lo} \gg Ro$

$V1 = 0$
 $V2 = 0$
 $TD = (ign)$
 $TR = 1u$
 $TF = 1u$
 $PW = 50u$
 $PER = 20m$


$V1 = 0$
 $V2 = 0$
 $TD = (ign)$
 $TR = 1u$
 $TF = 1u$
 $PW = 50u$
 $PER = 20m$

$V1 = 0$
 $V2 = 0$
 $TD = (ign)$
 $TR = 1u$
 $TF = 1u$
 $PW = 50u$
 $PER = 20m$

$V1 = 0$
 $V2 = 0$
 $TD = (ign)$
 $TR = 1u$
 $TF = 1u$
 $PW = 50u$
 $PER = 20m$


Experiment No. 2

1.

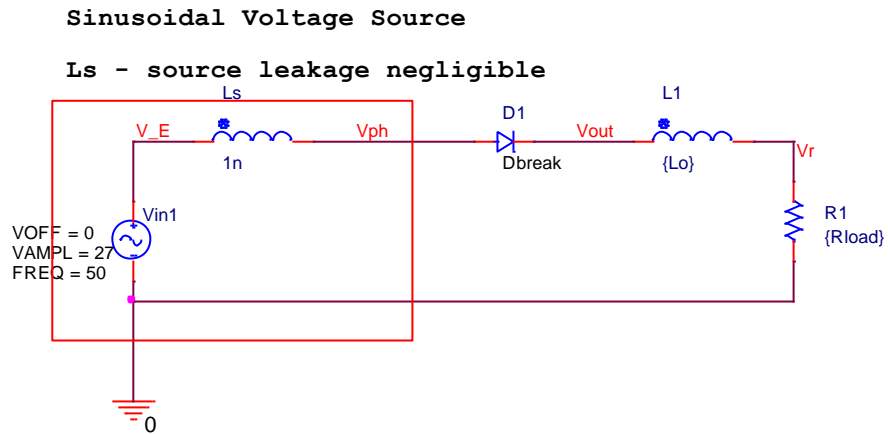

1. Construct schematic;
2. Spend simulations at different values of parameters L_o , R_{load} :
 - a) $L_o = 5\text{nH}$, $R_{load} = 10\ \Omega$;
 - b) $L_o = 50\text{mH}$, $R_{load} = 5\ \Omega$.
3. Submit current $I(R1)$ and voltage V_E waves in one plot

2.

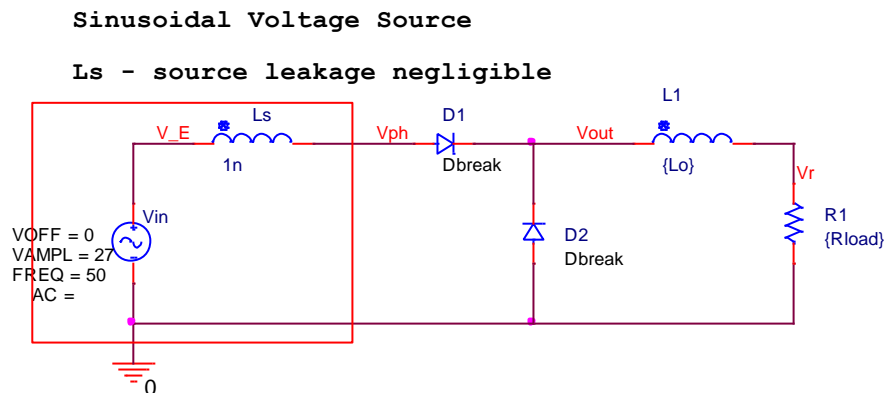


1. Construct schematic;
2. Spend simulations at different values of parameters L_o , R_{load} :
 - $L_o = 5\text{nH}$, $R_{load} = 10\ \Omega$;
 - $L_o = 50\text{mH}$, $R_{load} = 5\ \Omega$.
3. Submit current and voltage waves :
 - V_E , $I(R1)$;
 - $I(D1)$, $I(D2)$.
4. Compare the simulation results for different variants of parameters and evaluate the influence of parameters.
5. Measure and explain the changes diodes $D1, D2$ conduction angles (θ)

3.

Sinusoidal Voltage Source


Is - source leakage negligible

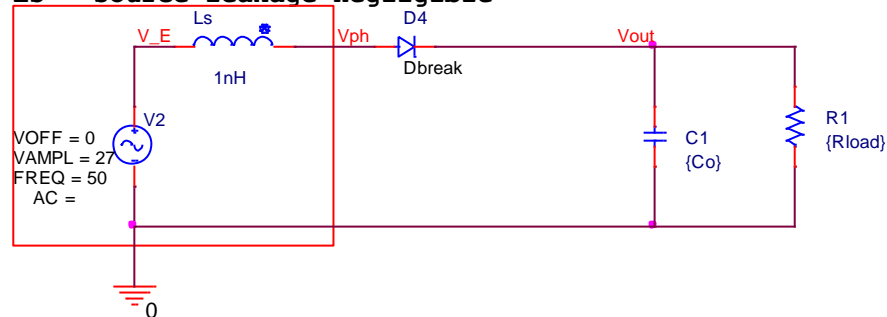

1. Construct schematic;
2. Spend simulations at different values of parameters L_o , R_{load} , C_o :
 $C_o = 5\text{nF}$, $R_{load} = 10\ \Omega$;
 $C_o = 1000\ \mu\text{F}$, $R_{load} = 10\ \Omega$.
3. Submit current and voltage waves :
 V_E , $I(R1)$;
 V_E , $I(D4)$;
 V_E , $I(C1)$;
 $I(D4)$, $I(C1)$.
4. Compare the simulation results for different variants of parameters and evaluate the influence of parameters.
5. Measure and explain the changes diode conduction angle (θ).

4.

Sinusoidal Voltage Source with midpoint

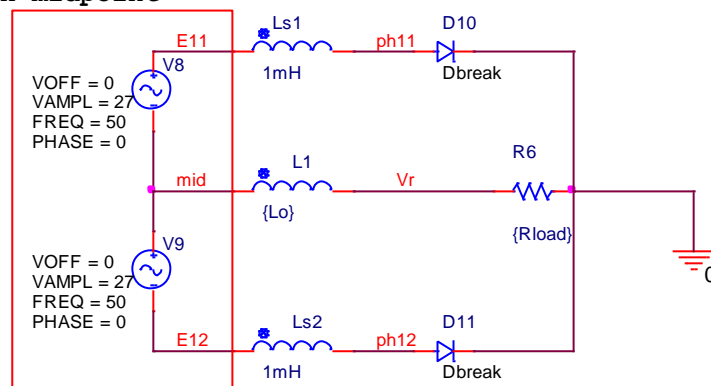

1. Construct schematic;
2. Spend simulations at different values of parameters L_o , R_{load} :
 $L_o = 5\text{nH}$, $R_{load} = 10\ \Omega$;
 $L_o = 10\text{mH}$, $R_{load} = 10\ \Omega$.

3. Submit current and voltage waves :

V_E11 , V_E12, I(R6);


V_E11 , I(D10);

I(D10), I(D11),

4. Compare the simulation results for different variants of parameters and evaluate the influence of parameters.

5. Measure and explain the changes diode ignition angle (α), conduction angle (θ), commutation angle (γ).

5.

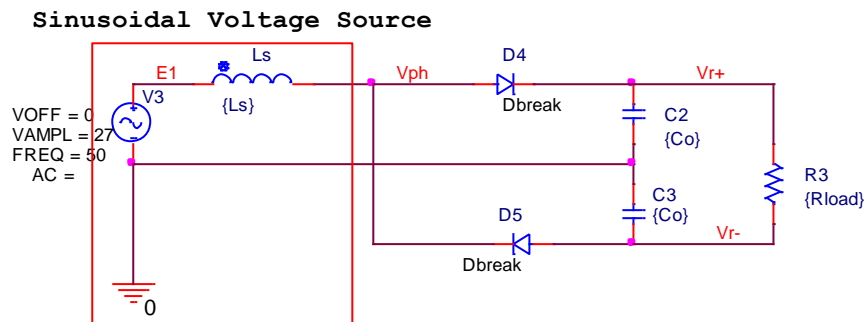

1. Construct schematic;

2. Spend simulations at different values of parameters L_s, C_o, R_{load} :

$L_s = 100\text{nH}, C_o = 1000\mu\text{F}, R_{load} = 10\text{k}\Omega, 100\Omega, 10\Omega$;

$L_s = 100\mu\text{H}, C_o = 1000\mu\text{F}, R_{load} = 10\text{k}\Omega, 100\Omega, 10\Omega$;

3. Submit current and voltage waves :

V_E1 , $(V_{r+}) - (V_{r-})$,

V_E1 , I(R3),

V_E1 , I(D4),


V_E1 , I(D5),

I(D4), I(C2).

4. Compare the simulation results for different variants of parameters and evaluate the influence of parameters.

5. Measure and explain the changes diode ignition angle (α), conduction angle (θ), commutation angle (γ).

6.

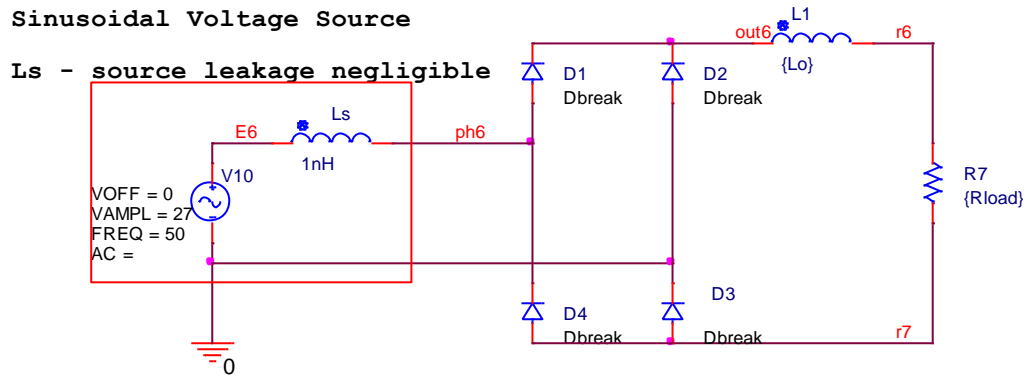

1. Construct schematic;

2. Spend simulations at values of parameters Co, Rload:

Lo = 1nH, Rload = 10 Ω;

3. Submit current and voltage waves :

V_E6, I(R7),


V_E6, I(D1),

V_E6, I(Ls).

4. Compare the simulation results for different variants of parameters and evaluate the influence of parameters.

5. Measure and explain the changes diode D1 ignition angle (α), conduction angle (θ), commutation angle (γ).

7.

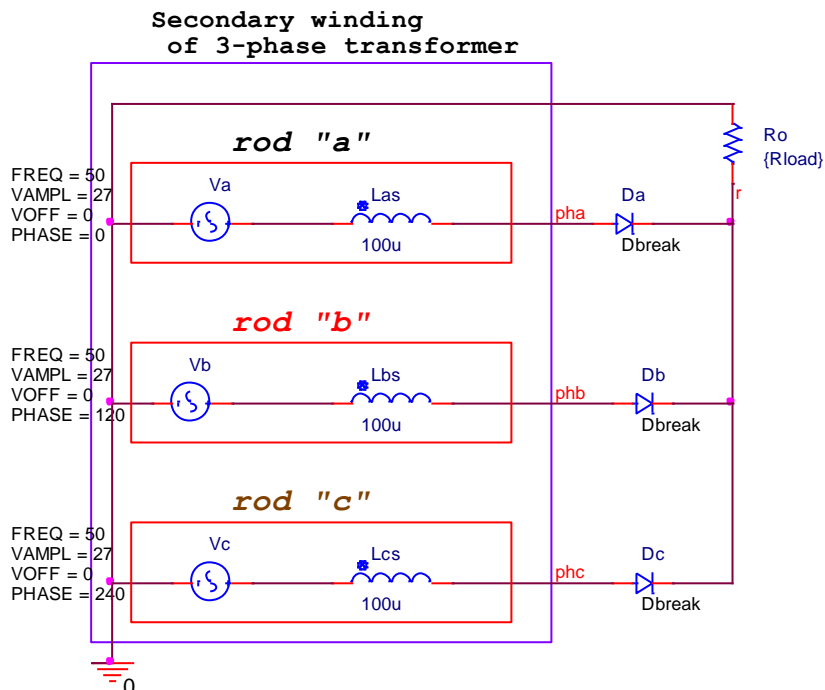


*Each phase contains a single coil, which sits on one of the rod of the 3-phase transformer

1. Construct schematic;
2. Spend simulations at $R_{load}=10 \Omega$.
3. Submit current and voltage waves :
 - V_{Ea} , $V_{(Ea, Eb)}$;
 - V_{Ea} , V_{pha} ;
 - V_{Ea} , V_{Eb} , V_{Ec} ;
 - V_{Ea} , $I(Ro)$;
 - $I(Da)$, $I(Db)$, $I(Dc)$,
 - V_{Ea} , $I(Da)$,
 - Rod current $I(Las)$ and *average* $I(Las)$.

4. Measure diode's D_a ignition angle (α), conduction angle (θ), commutation angle (γ).


8.

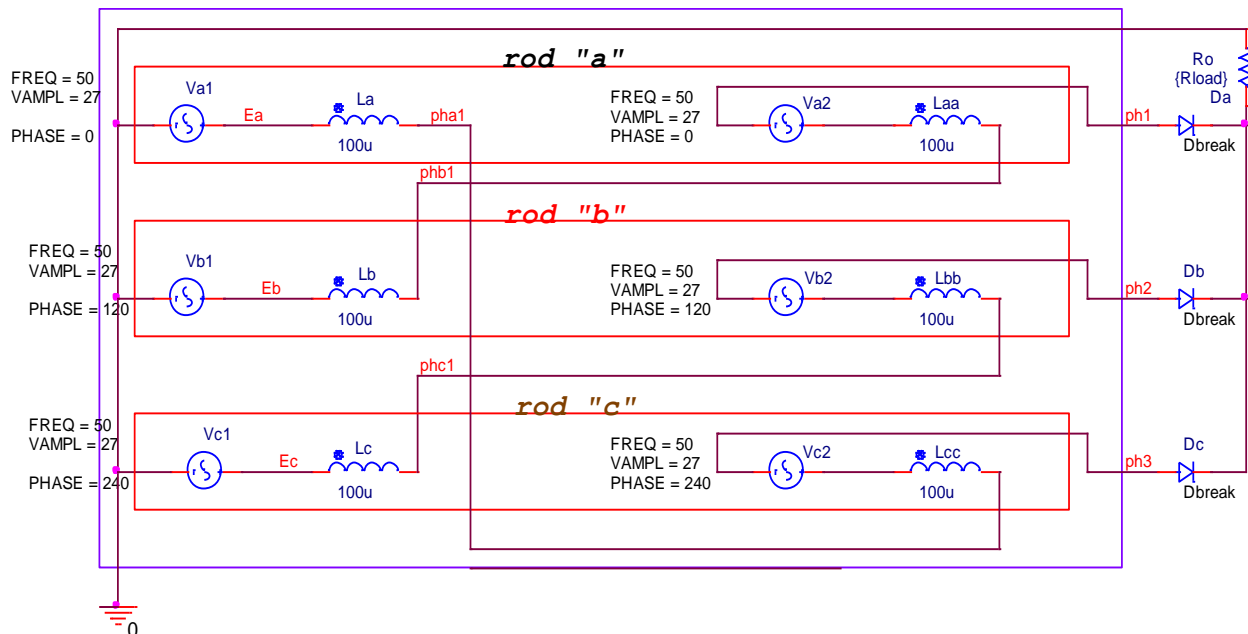

***Every phase contains two identical coils sitting at one rod of the 3-ph transformer*

1. Construct schematic;
2. Spend simulations at $R_{load}=10 \Omega$.
3. Submit current and voltage waves :
 - V_{Ea} , $V_{(ph1, ph2)}$; /single coil EMF and transformer line voltage/
 - V_{Ea} , V_{pha1} ; /single coil EMF and voltage/
 - V_{pha1} , $(V_{ph3}) - V(pha1)$; / coil voltage at rod "a" and coil voltage at rod "c" - components of phase3 /
 - V_{Ea} , $I(La)$;
 - $I(La)$, $I(Laa)$
 - Rod current $I(La) + I(Laa)$ and *average* $I(La) + I(Laa)$;
4. Compare and explain the results of exp.7 and exp.8.

9.

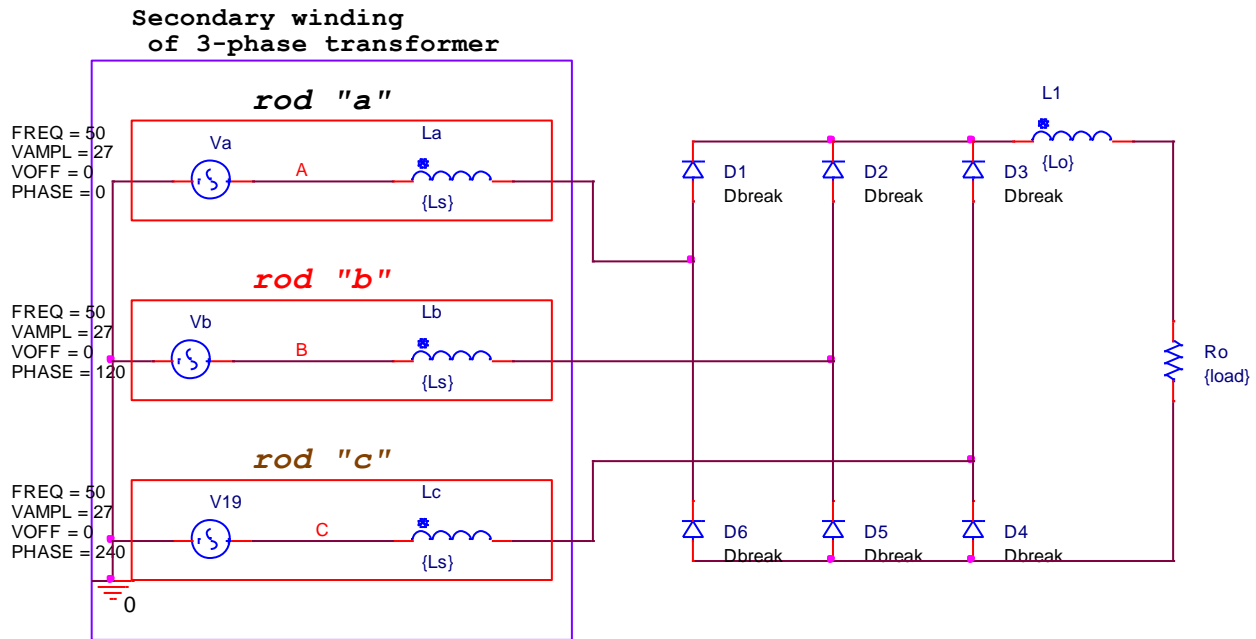

1. Construct schematic;

2. Spend simulations at different values of parameters L_s , R_{load} :

$L_s = 10\text{nH}$, $R_{load} = 10\ \Omega$;

$L_s = 100\ \mu\text{H}$, $R_{load} = 10\ \Omega$;

3. Submit current and voltage waves :

V_A , $V(A,B)$;

V_A , $I(L_a)$;

V_A , $I(R_o)$;

V_A , $I(D_1)$;

Measure and explain the changes diode D1 ignition angle (α), conduction angle (θ), commutation angle (γ).

$I(L_a)$, $I(L_b)$;

Rod "a" current $I(L_a)$ and *average* $I(L_a)$;

Show the sequence of phase operation during one period

4. Compare the simulation results for different variants of parameters and evaluate the influence of parameters.

Experiment No.3

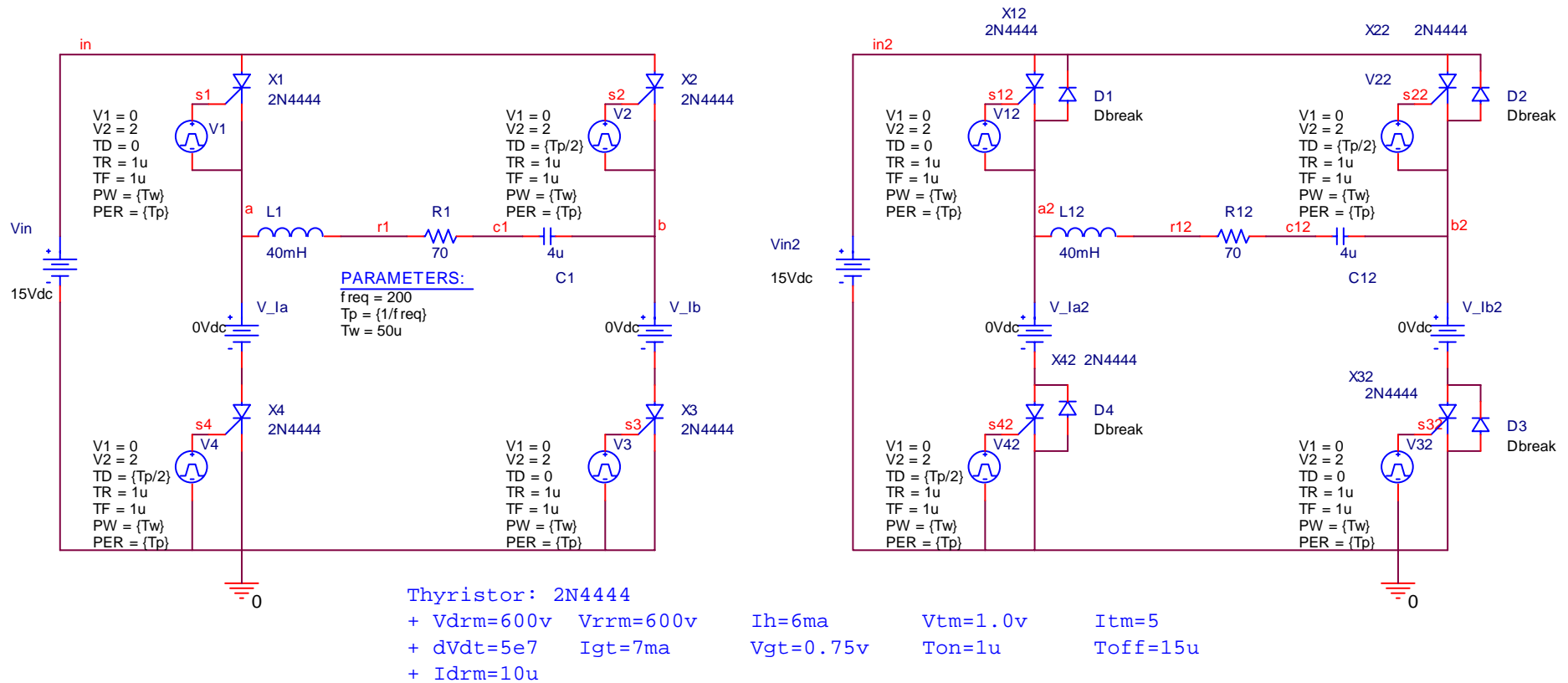


Fig. 3.A1.3. Schematic of bridge Voltage Inverter (without/with clamping diodes)

V_{in} ; $R1$; $C1$; $L1$; V_{in2} ; $R12$; $C12$; $L12$; $freq = var$;

$I_{thyristor}$; $V_{thyristor}$; V_{ab} ; I_{R1} ; V_{ab2} ; $I_{R12} = ??$

Summary

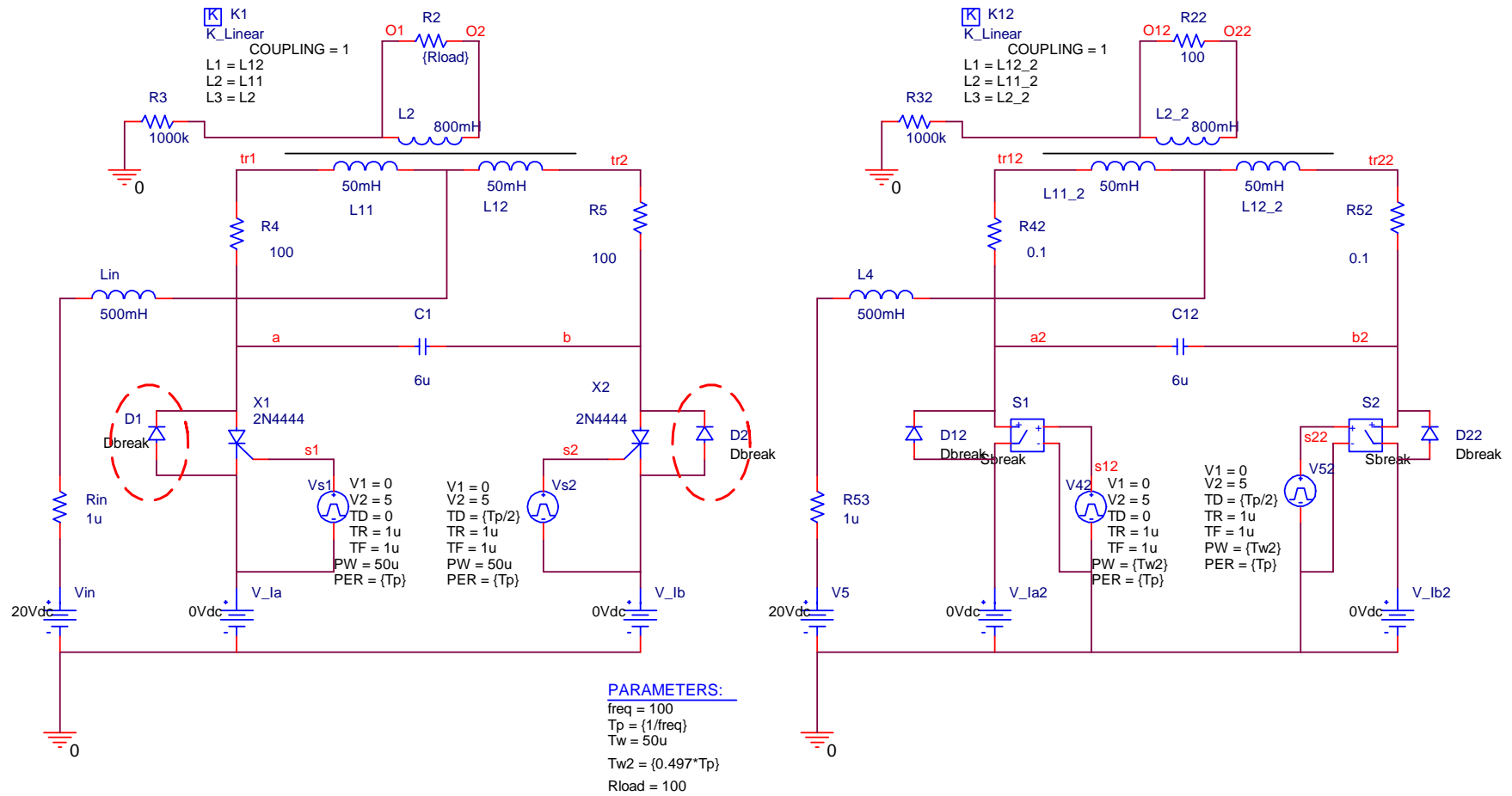


Fig. 3.A1.4. Schematic of Current Inverter (without/with clamping diodes)


V_{in} ; R_{load} ; $C1$; V_{in2} ; $C12$; $freq = var$;

$I_{thyristor}$ ($I(V_{la})$); $V_{thyristor}$; $V_{o1,o2}$; I_{R1} ; V_{ab2} ; $V_{o12,o22} = ??$

Summary

Experiment No.4

Controlled rectifier simulation model

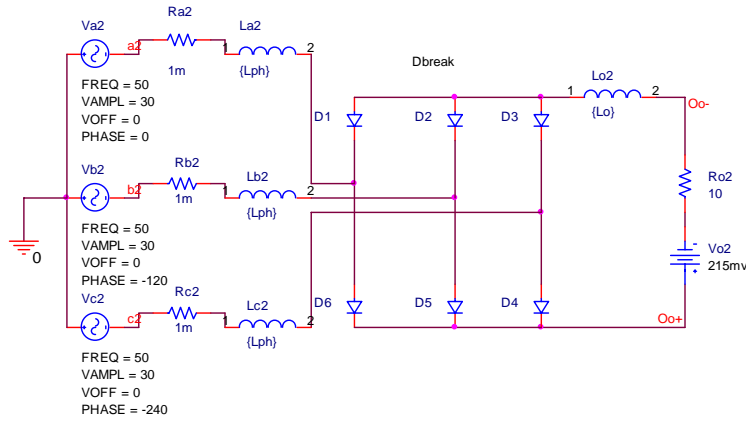

PARAMETERS:



$T_p = 20m$
 $T_{ig} = (K_{ig} \cdot T_p / 3)$
 $K_{ig} = 0$
 $L_{ph} = 0$
 $L_o = 0$

- a) $K_{ig} = 0, 0.1, 0.3; L_{ph} = 0; L_o = 0$
- b) $K_{ig} = 0; L_{ph} = 0.1mH, 0.2mH; L_o = 0$
- c) $K_{ig} = 0; L_{ph} = 0; L_o = 0, 5mH, 15mH$
- d) $K_{ig} = 0.3; L_{ph} = 0.75mH; L_o = 0$
- e) $K_{ig} = 0.3; L_{ph} = 0; L_o = 30m$

2N6405:
 $V_{DRM_RRM} = 800V;$
 $I_T(rms) = 32A;$
 $I_G = 5mA$


Waveforms Study:

$V_{ph}, I_{ph}, I_{th}, V_{pulse}, I_o$

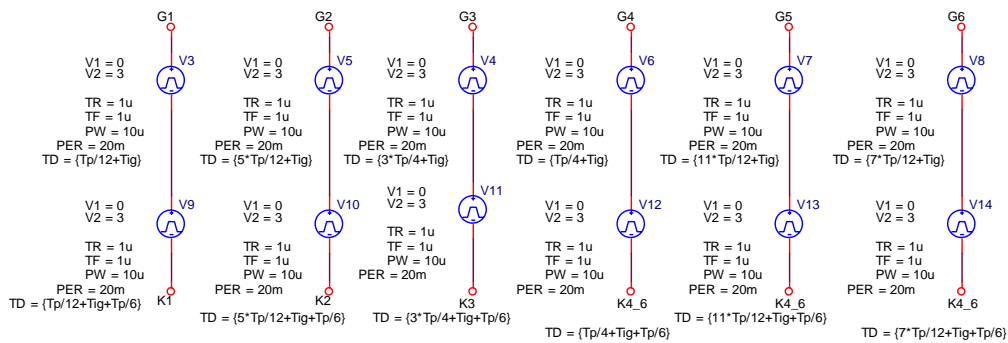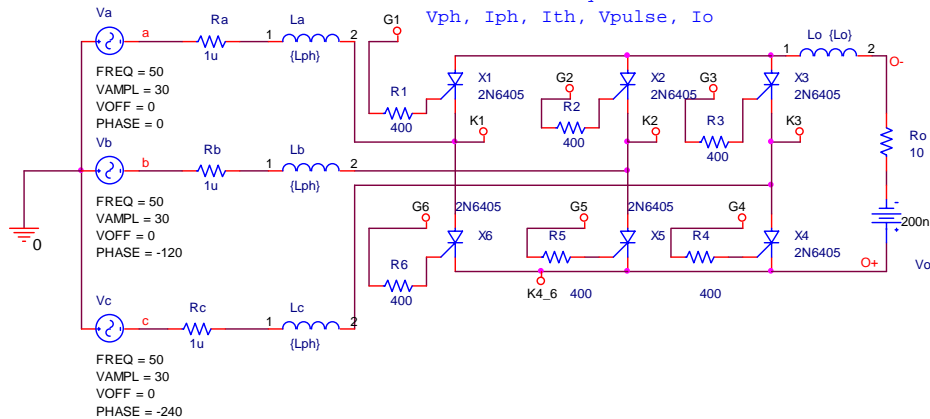


Experiment No.5

1. Introduction in chopper techniques.

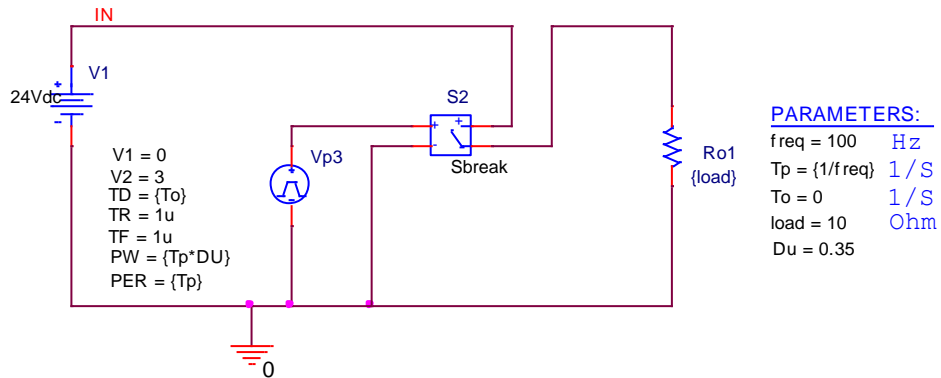

- construct presented schematic in SPICE;
- carry out simulations (transient) for different values (6-8) of parameter Du (0 -1);
- draw the diagram of dependence of average value of loud current from parameter Du

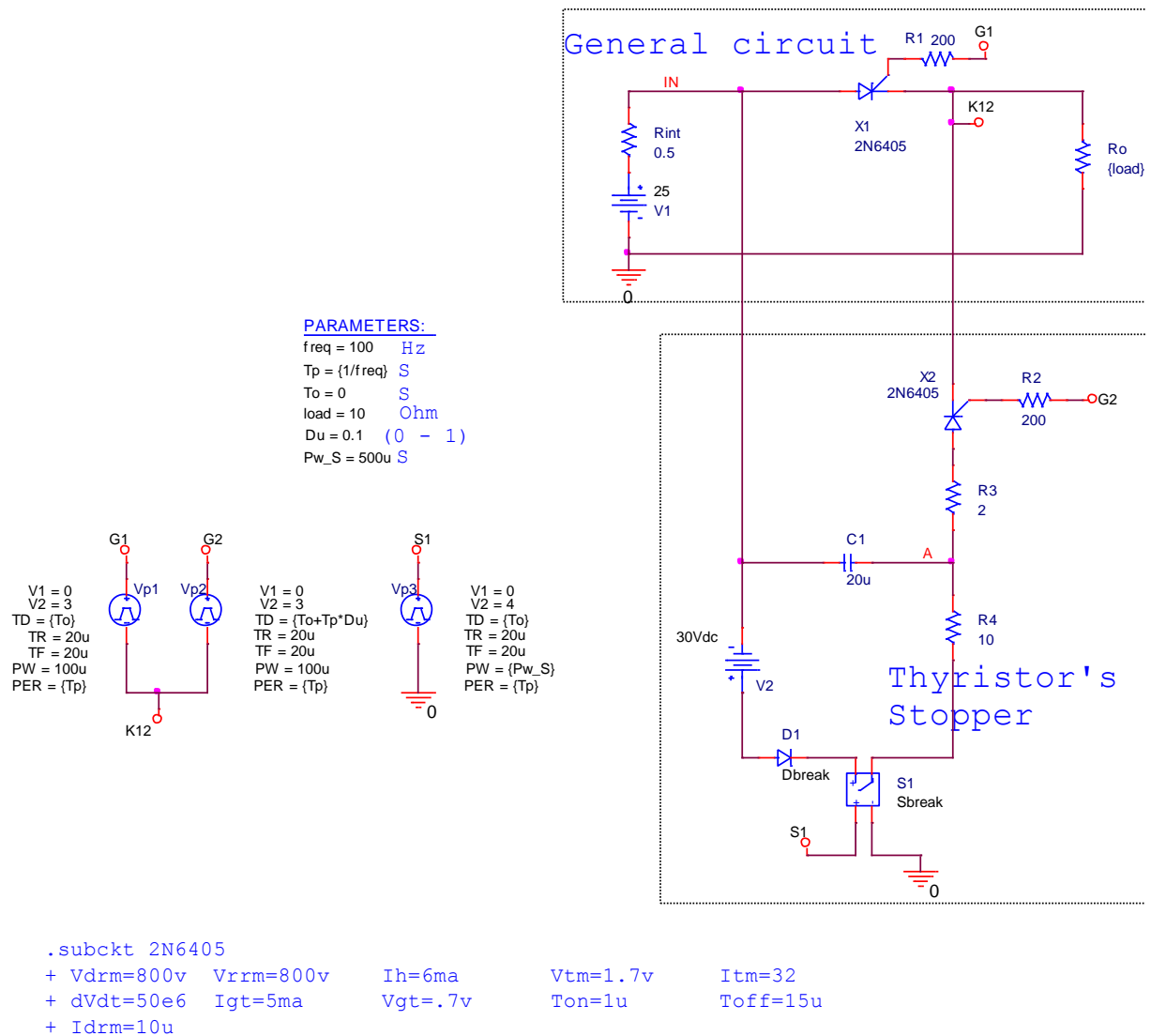2. chopper with external commutation source



- construct schematic in SPICE;
- carry out simulations (transient) for different values of frequencies (20 -800Hz) → find the range of frequencies of working ability of the scheme at the specified parameters;
- draw the current waveform in loud, thyristors, capacitor for one value of frequency;
- explain currents forms.


Device's principle of action:

The pulse on a gate G1 opens the first thyristor X1. The current in load Ro starts to flow. In the same time the switch S1 opens and a source V2 charges the capacitor C1. At the necessary moment the pulse on a gate G2 opens the thyristor X2 and the positive pole A of a capacitor C1 is put to the cathode of the thyristor X1 and the negative pole is put to the its anode. The current through thyristor X1 stops and the Thyristor X1 is closed. The Thyristor X2 will be closed when capacitor C1 will be discharged.

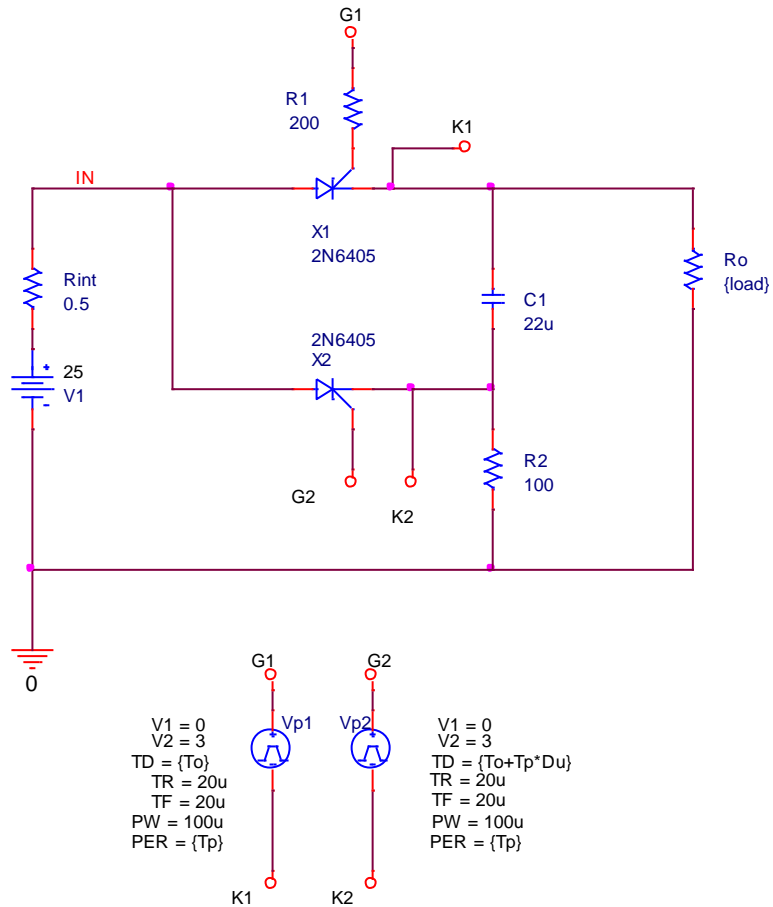3. RC-chopper


PARAMETERS:

freq = 100 Hz
 $T_p = \{1/freq\}$ S
 $T_o = 0$ S
 load = 10 Ohm
 $D_u = 0.35$ (0 - 1)




- construct schematic in SPICE;
- execute simulations (transient) for different values of frequencies (20 -800Hz) → find the range of frequencies of working ability of the scheme at the specified parameters;
- draw the current waveform in loud, thyristors, capacitor for one value of frequency;
- explain currents forms.

4. LC - chopper

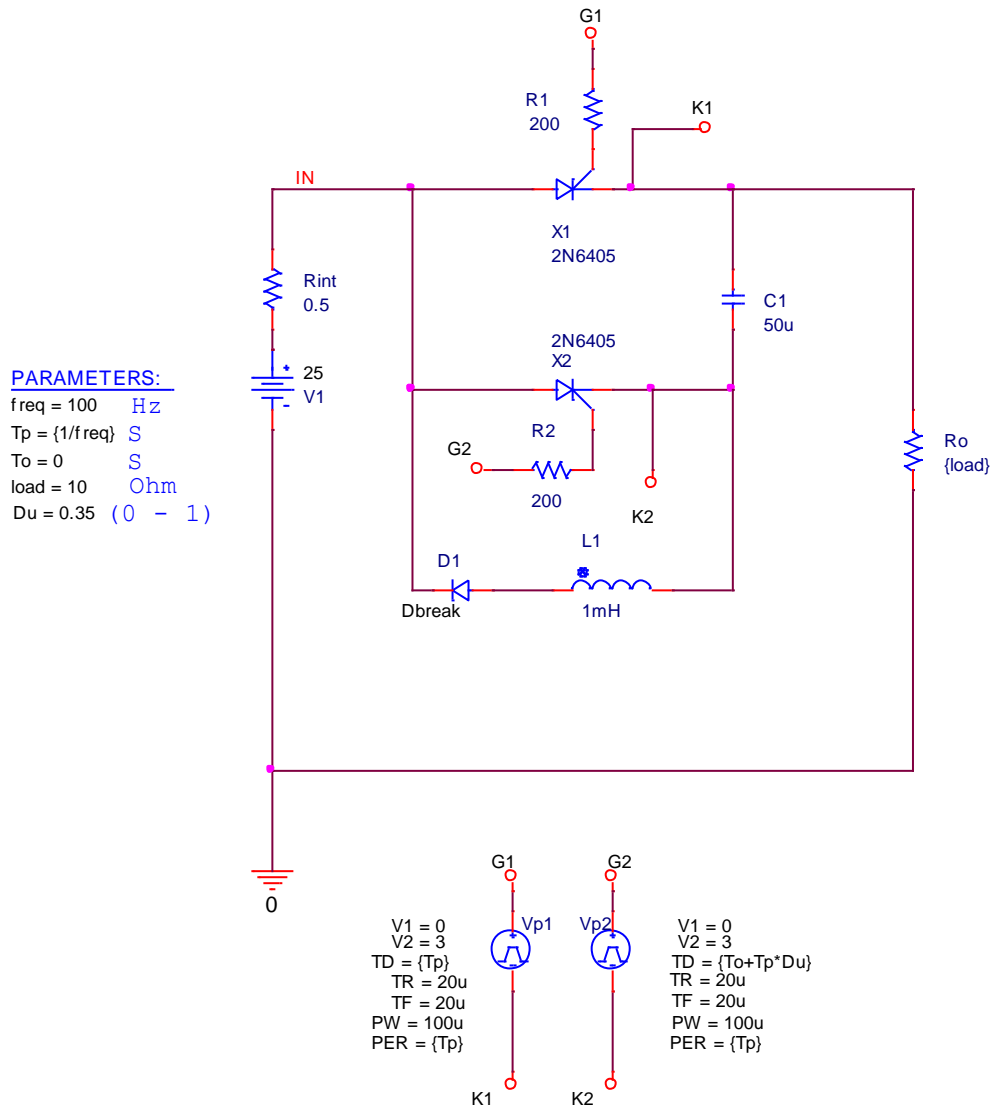


- construct schematic in SPICE;
- carry out simulations (transient) for different values of frequencies (20 -800Hz) → find the range of frequencies of working ability of the scheme at the specified parameters;
- draw the current waveform in loud, thyristors, capacitor for one value of frequency;
- explain currents forms.

Experiment No.6

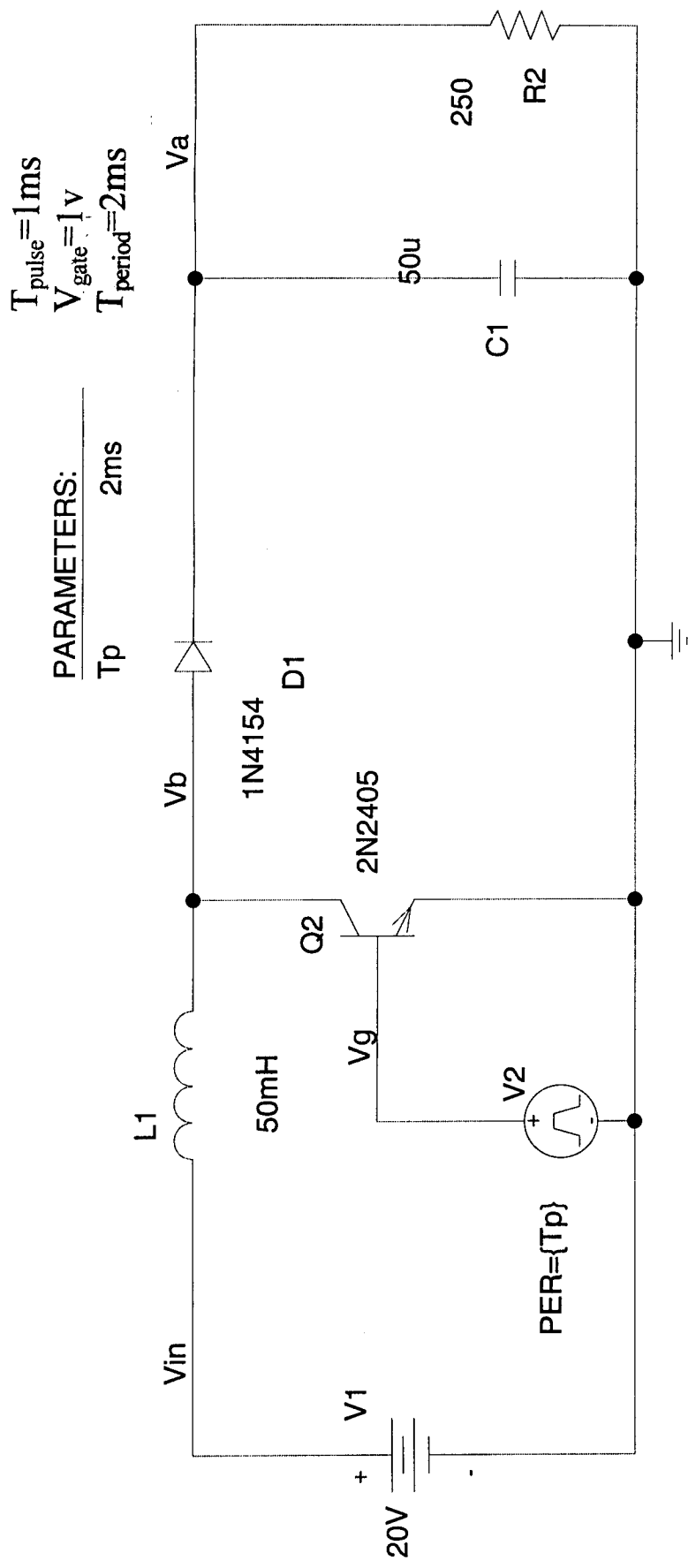

סכימה לסמולציה לניסוי מס' 6 - Boost converter

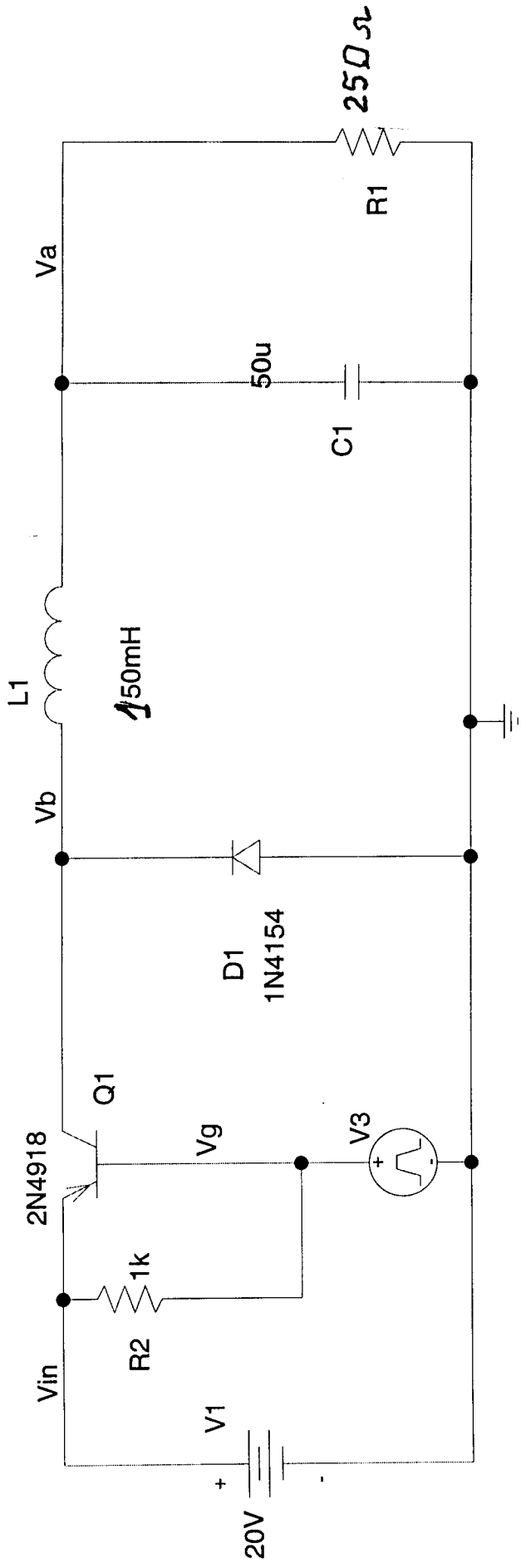$T_{\text{pulse}}=1\text{ms}$
 $T_{\text{period}}=2\text{ms}$




סכימה לסמולציה לניסוי מס' 6 - Buck converter

$T_{pulse} = 1ms$
 $T_{period} = 2ms$

PARAMETERS:

T_p 2ms

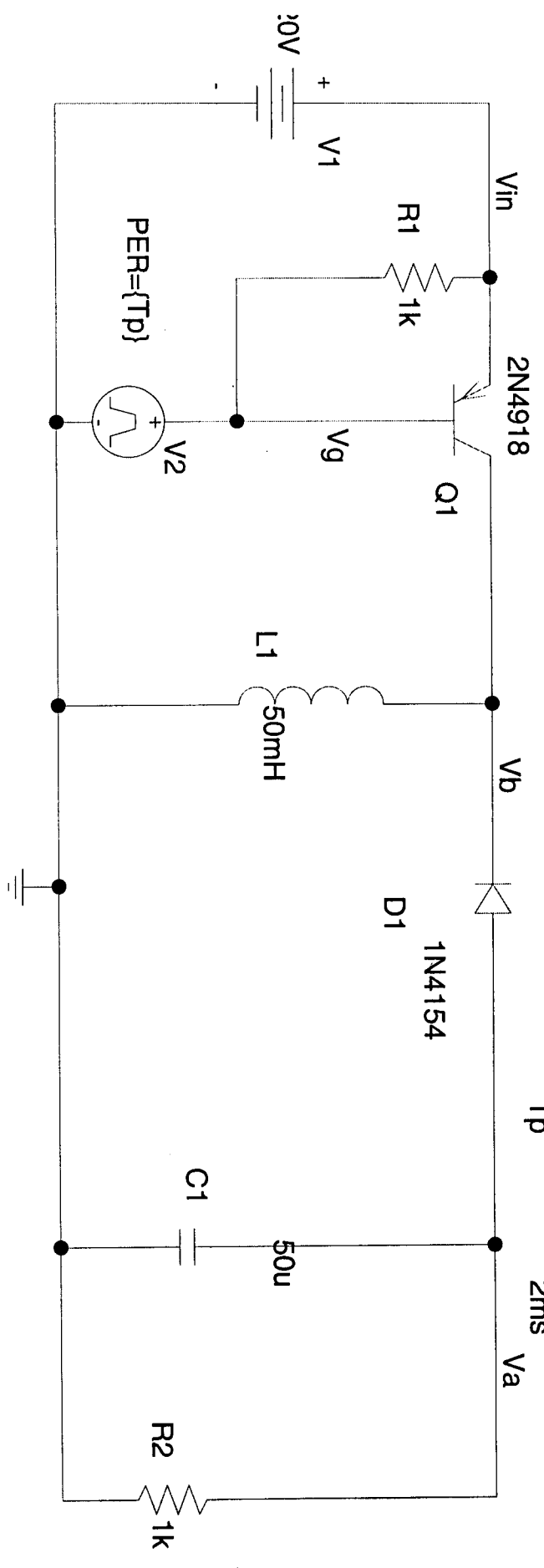


סכימה לסמולציה לניסוי בט' - Buck-Boost converter 6

Experiment No. 7

Exercise 1

6-step inverter

Running time ~ >15-20 periodes

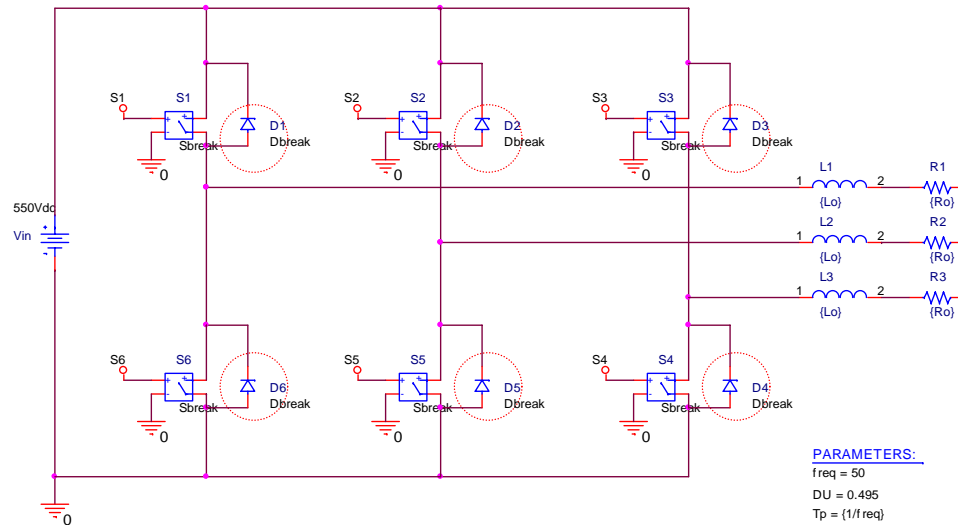

$$X_L = 2 * \pi * f * L = 6.28 * 50 * 0.1 = 31.4 \text{ Ohm}$$

PARAMETERS:

freq = 50

DU = 0.495

$T_p = \{1/\text{freq}\}$


$T_w = \{DU * T_p\}$

$T_D = \{T_p/3\}$

$R_o = 15$

$R_o = 15$ (30, ... 30n) Ohm

$L_o = 500u$ (10n, ... 0.1m) H

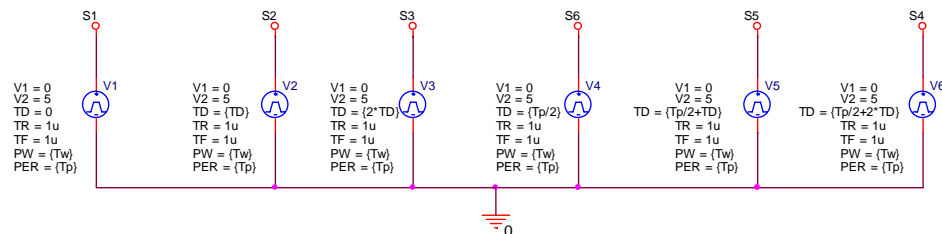

Result voltages and currents of switch and load in the scheme without diodes:
(Z~30 Ohm)

1. for active load ;
2. for active-inductive load;
3. for mainly inductive load.

The same in the scheme with diodes

PWM forming


Exercise 2

PWM are created at comparison of a signal of carrier frequency with a signal of reference frequency

Carrier saw-tooth
voltage generator

Reference frequency
generator


Comparator

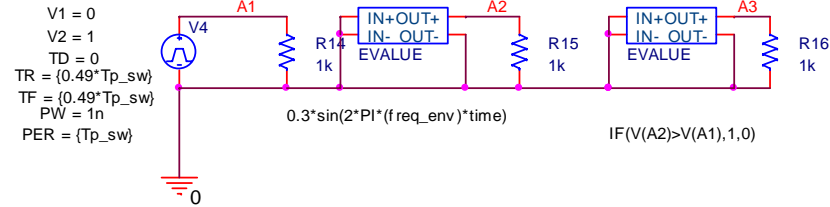


PARAMETERS:


$\text{freq_env} = 25$
 $\text{freq_switch} = 1000$
 $Tp_sw = \{1/\text{freq_switch}\}$
 $PI = 3.141592654$

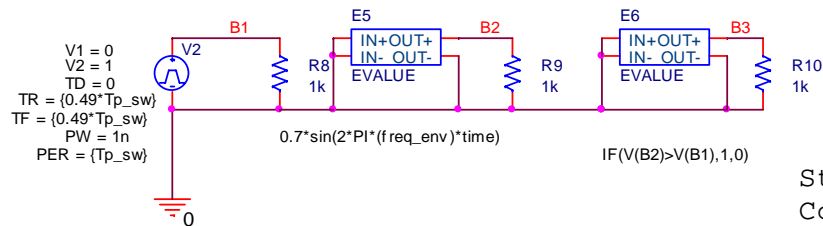
freq_env - output frequency (reference);
 freq_switch - internal switching frequency
 (carrier frequency)



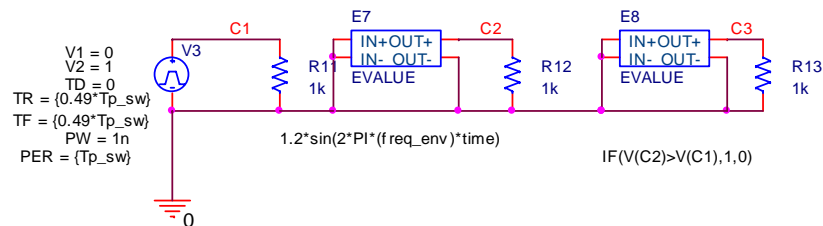Study process of pulses formation on the specified schemes;
 Compare spectra of output signals;
 Draw spectra curves




For calculation of spectra use *SPICE* option : 
 Simulation Setting\Output File Options\
 Center frequency - freq_env ;
 Number of harmonics - 45;
 Output variables - $V(A3)$, $V(B3)$, --- $V(D3)$

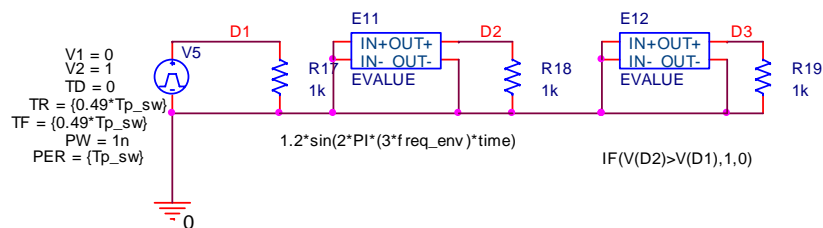

PWM 3-phase inveter

Exercise 3

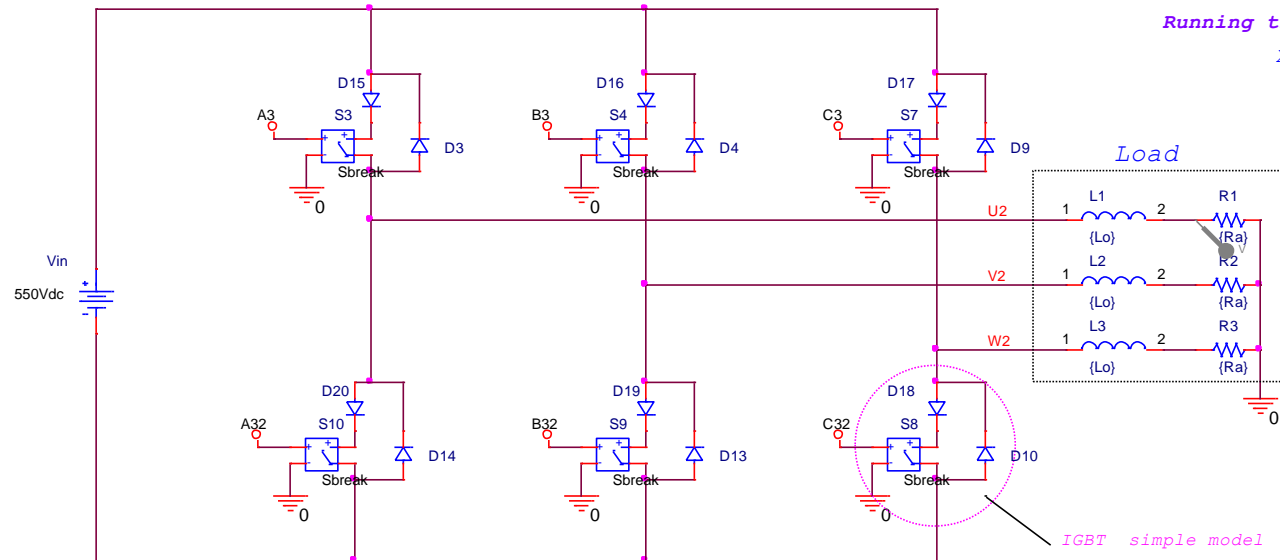

Running time ~ >15-20 periodes of envelope curve

$$X_L = 2 * \pi * f * L = 6.28 * 50 * 0.01H = 3.14 \text{ Ohm}$$

PARAMETERS:

freq = 50 envelope frequency
 Tp = {1/freq}
 TD = (Tp/3)
 freq_car = 1000 carrier frequency
 DU_car = 0.495
 Tw_car = (DU_car * Tp_car)
 Tp_car = {1/freq_car}

Lo = 10nH (10mH)
 Ra = 30.14 (30.14n)
 V_du = 0.8
 (Pi=3.141592654)

Result voltages and currents of switch and load
 1. for active load (Z~30 Ohm);
 2. for active-inductive load (Z~30 Ohm)

Pulse Generator

