

## Project: Incandescent lamps dimmer

Students	Asaf Abraham ID: 032824526	
	Ran Yehiely ID: 034359505	

Supervisor: Prof. Sam Ben-Yaakov

Year: 2005


### Abstract

Line current harmonics is one of the major issues in the design of a dimmer. The harmonics problem increases when attempting to achieve a modulation frequency at a "low" frequency (up to 20 KHz). The objective of this project was to design and build a dimmer that complies with the line harmonic standard but with low switching frequency.

The problem of eliminating harmonics in a switching converter at a given desired fundamental output voltage was to find the switching times (angles) that produce the optimum switching angles for the converter. This optimization eliminated some higher order harmonics while maintaining the required fundamental voltage.


The control circuit we built eliminates up to the tenth harmonic with exact switching angles. The switching frequency is 1.3 KHz.


The final circuit

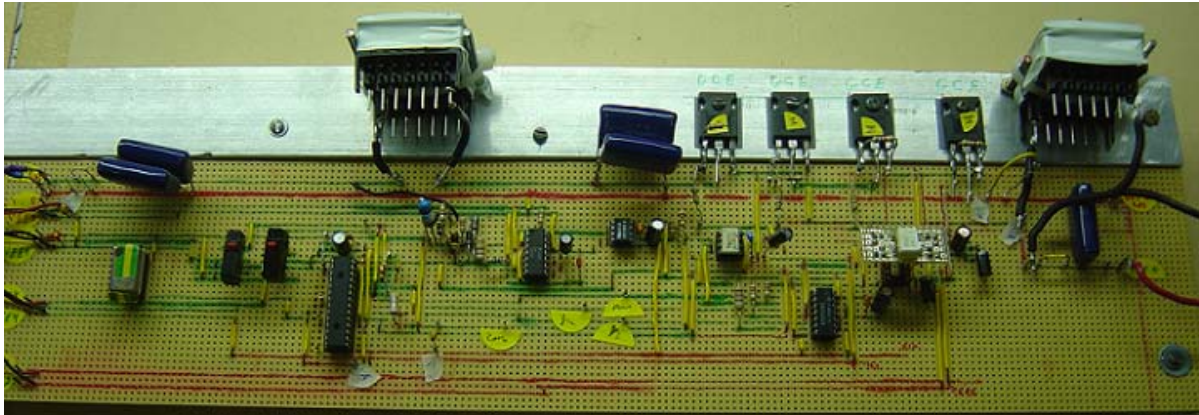

Some of the measurements we took:

1) Measurements of the line current harmonics

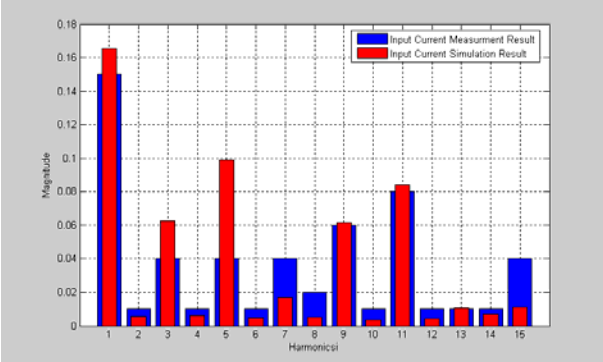
Line current harmonics	Planned Output Power $\left(\frac{P_{out}}{P_{out_{max}}} \mid P_{out_{max}} = 500w\right)$	Input voltage $V_{in}$ [V]
 <p data-bbox="311 1545 550 1601"><math>I_{rms_{measured}} = 0.19[A]</math></p> <p data-bbox="311 1601 550 1646"><math>I_{rms_{simulation}} = 0.23[A]</math></p>	23%	30

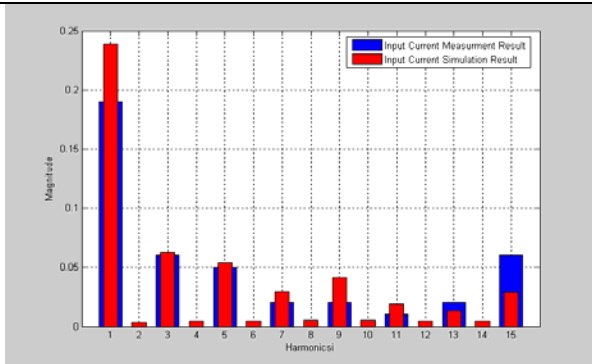

45%

$$I_{rms_{measured}} = 0.21[A]$$

$$I_{rms_{simulation}} = 0.27[A]$$

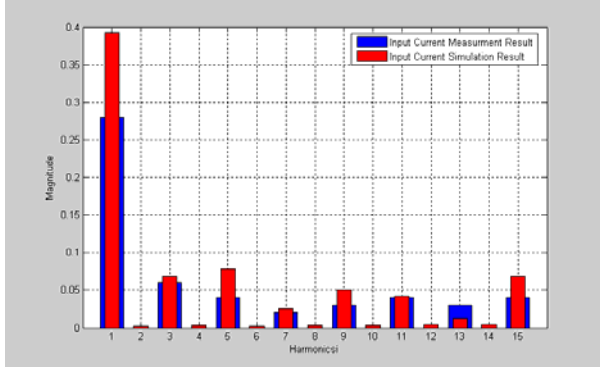




85%

$$I_{rms_{measured}} = 0.29[A]$$

$$I_{rms_{simulation}} = 0.41[A]$$

2) Wave forms with input voltage of 30Vrms

Graph	Channels	Output power
	<p><b>Upper channel</b> Control signal for Q3 Vs. time</p>	<p>Switching for 23% of the max planned output</p>
<p><b>Lower channel</b> Control signal for Q4 Vs. time</p>	<p><b>(115W)</b></p>	
	<p><b>Upper channel</b> PWM Signal Vs. time</p>	
<p><b>Lower channel</b> Line current Vs. time</p>		
	<p><b>Upper channel</b> PWM Signal Vs. time</p>	
<p><b>Lower channel</b> Coil current Vs. time</p>		

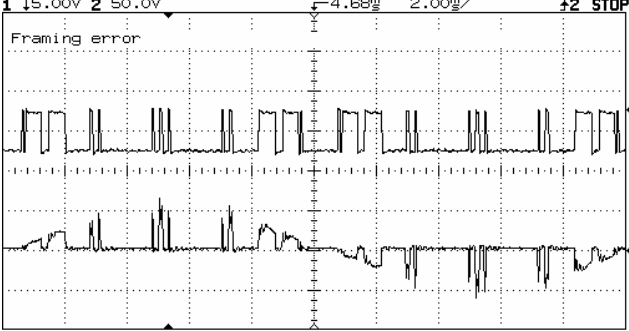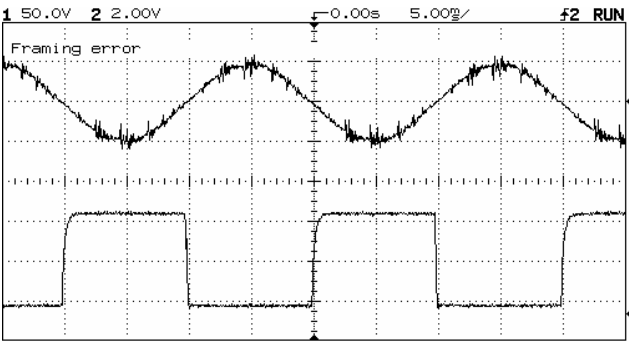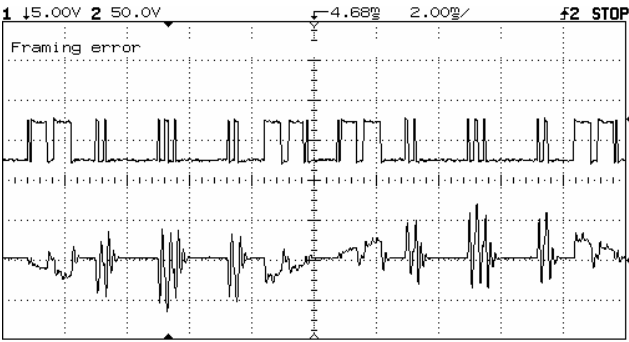Graph	Channels	Output power
 <p>1 15.00V 2 50.0V 4.68µs 2.00µs / f2 STOP</p> <p>Framing error</p>	<p><b>Upper channel</b> PWM signal Vs. time</p>	<p>Switching for 23% of the max planned output  <b>(115W)</b></p>
<p><b>Lower channel</b> Coil voltage Vs. time</p>		
 <p>1 50.0V 2 2.00V 0.00s 5.00µs / f2 RUN</p> <p>Framing error</p>	<p><b>Upper channel</b> Vin Vs. time</p>	
<p><b>Lower channel</b> Zerocross detector signal Vs. time</p>		
 <p>1 15.00V 2 50.0V 4.68µs 2.00µs / f2 STOP</p> <p>Framing error</p>	<p><b>Upper channel</b> PWM signal Vs. time</p>	
<p><b>Lower channel</b> Output voltage Vs. time</p>		