
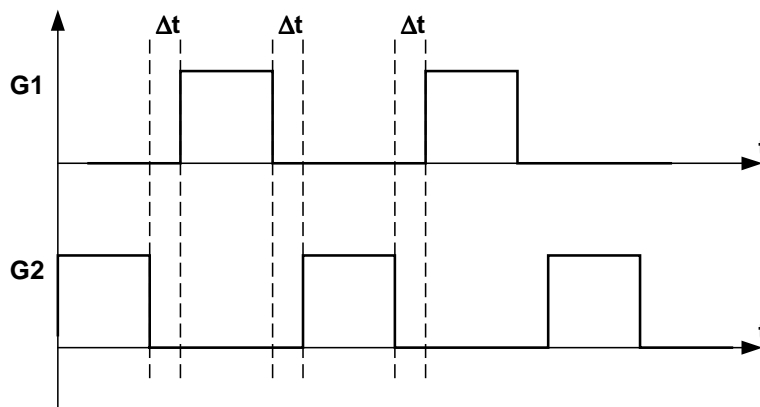


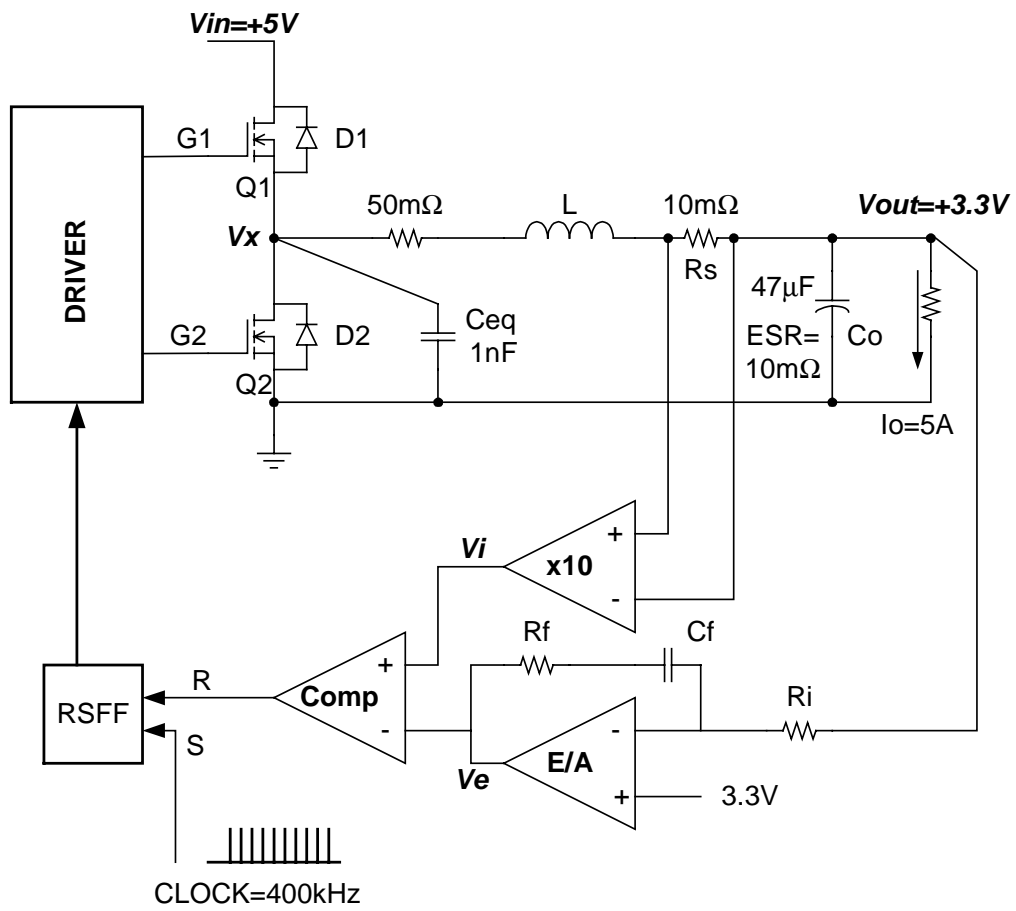- כל חומר עזר מותר
- אין להעביר חומר בין הנבחנים
- שימוש במחשבוניס כולל מחשב מטלטל מותר



כל השאלות מתייחסות לשרטוט המצורף.
יש לענות על 3 מתוך 4 השאלות הנתונות.

נתון: תדר המיתוג 400kHz
זמן מת בין פולסי השער (dead time Δt) 100ns
 $V_{D1}=V_{D2}=0.3V$, $R_{DSon}=0.1\Omega$, $Q_{gate}=30nC$

שאלה מס' 1

1.1 (20%)

חשב ערכו של L כך שאדוות הזרם $\Delta I=1A$ בעומס הנומינלי בהזנחת Δt dead time ומפלי המתח במעגל (R_{DSon} , מתחי דיודות).

1.2 (40%)

חשב ושרטט את המתח בנקודה V_x והזרמים דרך הדיודות והטרנזיסטורים בהנחה שזמני המיתוג של הטרנזיסטורים מוזנחים (יש להתחשב ב-dead time). החישוב עבור $\Delta I=1A$.

1.3 (40%)

חשב את הפסדי ההולכה של הטרנזיסטורים בהזנחת Δt . פרט את ההפסדים הנוספים של כל אחד מהטרנזיסטורים בהנחה שהם זהים. איזה יתחמם יותר?

שאלה מס' 2

2.1 (33%)

חשב את האדווה במוצא במצב היציב אם $\Delta I=2A$ (בגין ESR ובגין טעינת הקבל).

2.2 (33%)

חשב את הפסדי "ההולכה" של קבל מוצא.

2.3 (34%)

חשב את הזרם הדרוש בשערי הטרנזיסטורים (בהנחה שהוא קבוע בזמן הטעינת השער) כך שזמן העליה יהיה 50ns.

שאלה מס' 3

3.1 (30%)

חשב AP של הסליל אם $\Delta I=1A$, $K=0.5$, $B_{max}=0.3T$, $J=4A/mm^2$.

3.2 (30%)

הסבר כיצד ניתן לחשב התנגדות DC של חוט הסליל שחושב בסעיף 3.1 בהנחה שהגוף נבחר מהקטלוג והמוליכות הסגולית של חומר החוט ידועה.

3.3 (40%)

חשב את הפסדי הסליל אם התנגדות החוט $50m\Omega$ והפסדי הגרעין :

$$P_{core}=10(\Delta B_{pp})^2 \text{ Watt/cm}^3$$

ונפח הגרעין $2cm^3$.

שאלה מס' 4

מניחים $L=5\mu H$

4.1 (25%)

חשב ושרטט את המתחים V_e, V_i (ראה שרטוט) במצב היציב.

4.2 (35%)

בהנחה שמשווא הזרם גורם לסליל להתנהג כמקור זרם, שרטט את פונקציית התמסורת $\frac{v_o}{v_e}(f)$.

רמז: הנח $V_e=1V$ ובדוק איזה זרם יזרום בסליל, זה שווה מספרית ל- $\frac{i_L}{v_e}$ של מקור הזרם.

4.3 (40%)

על בסיס פונקציית התמסורת שהתקבלה ב-4.2 הצע רשת משוב וחשב R_f, R_i, C_f .

DC-DC Switch-Mode Converters

"moed Aleph"

$$nC := 10^{-9}C \quad ns := 10^{-9}s \quad mW := 10^{-3}W \quad m\Omega := 10^{-3}\Omega \quad mT := 10^{-3}T$$

Problem 1

1.1)

$$\Delta I := 1A \quad I_{load} := 5A$$

$$D = \frac{V_o}{V_{in}}$$

$$\frac{3.3V}{5V} = 0.66$$

$$L = \frac{V_o \cdot (1 - D)}{\Delta I \cdot f_{sw}} = \frac{V_o \cdot \left(1 - \frac{V_o}{V_{in}}\right)}{\Delta I \cdot f_{sw}}$$

$$\frac{3.3V \cdot \left(1 - \frac{3.3V}{5V}\right)}{1A \cdot 400kHz} = 2.81 \mu H$$

1.2)

$$\Delta t := 100ns \quad \Delta I := 1A$$

$$I_{Lav} = I_{load} = 5A$$

$$I_p = I_{Lav} + \frac{\Delta I}{2}$$

$$5A + \frac{1A}{2} = 5.5A$$

$$I_m = I_{Lav} - \frac{\Delta I}{2}$$

$$5A - \frac{1A}{2} = 4.5A$$

When Q1 switches OFF, the current through the inductor L continues to flow and discharges the equivalent capacitance C_{eq} in resonant manner. Supposing inductor current constant, let's check the discharge rate:

$$\frac{dV}{dt} = \frac{I_L(\text{peak})}{C_{eq}}$$

$$\frac{5.5A}{1nF} = 5.5 \frac{V}{ns}$$

Time needed to discharge this capacitor from 5V to zero:

$$\frac{5V}{5.5 \frac{V}{ns}} = 0.91 ns \quad (\ll \Delta t !!)$$

The resonant frequency of L- C_{eq} circuit:

$$\frac{1}{2 \cdot \pi \cdot \sqrt{2.81 \mu H \cdot 1nF}} = 3 MHz$$


$$\frac{1}{3MHz} = 333 ns$$

The possible voltage amplitude:

$$V = I \cdot \rho = I_p \cdot \sqrt{\frac{L}{C_{eq}}}$$

$$5.5A \cdot \sqrt{\frac{2.81\mu H}{1nF}} = 291.55V$$

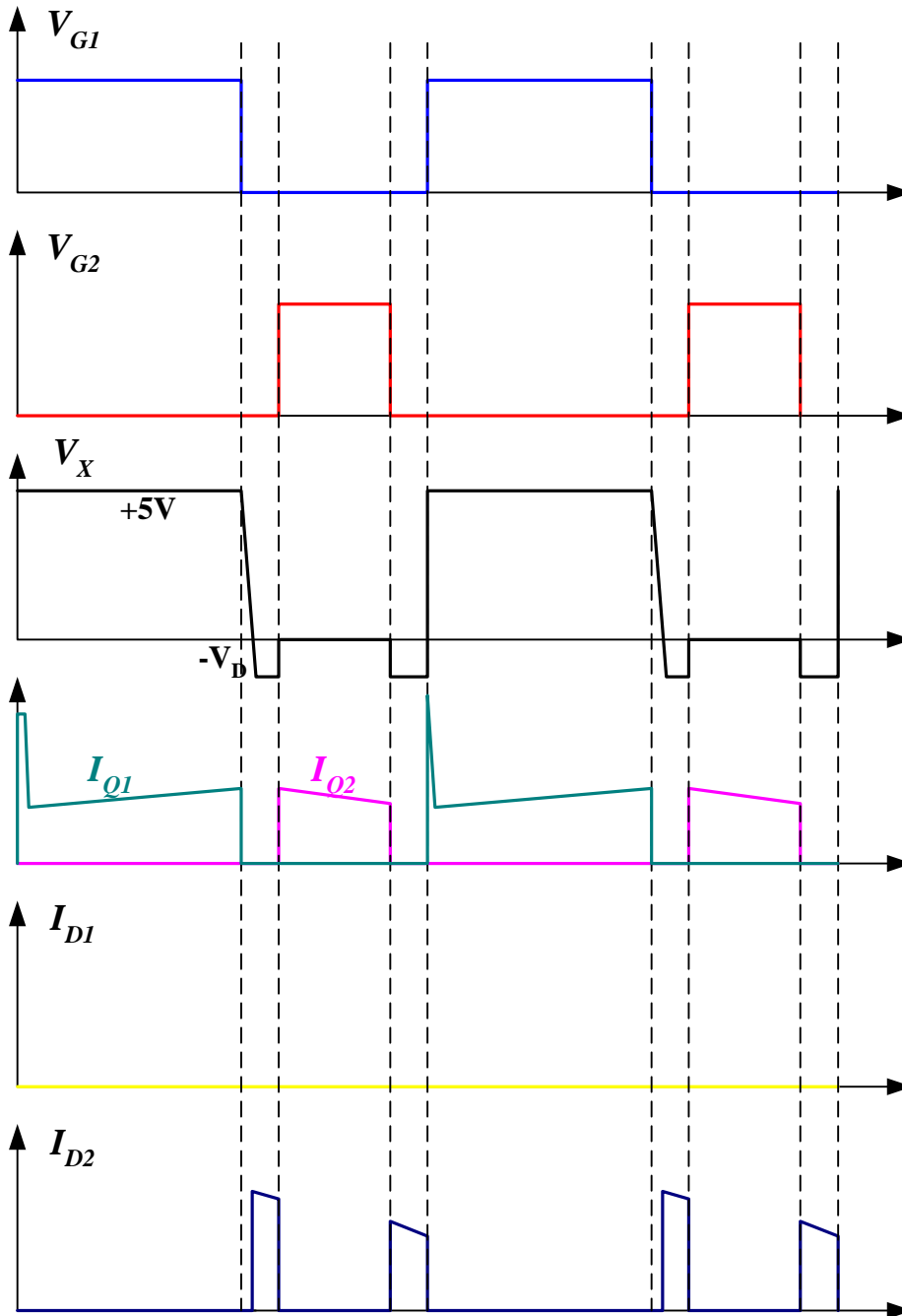From these calculations it can be concluded that capacitor voltage will be clamped by D2 diode and inductor current will flow through this diode until Q2 turns ON.



1.3)

$$P_{conduction} = I_{RMS}^2 \cdot R_{DS_{on}}$$

Conduction losses for Q1:

$$I_{RMS} = \sqrt{D \cdot \left(I_p \cdot I_m + \frac{\Delta I^2}{3} \right)} \quad \sqrt{0.66 \cdot \left[5.5A \cdot 4.5A + \frac{(1A)^2}{3} \right]} = 4.07A$$

$$(4.07A)^2 \cdot 0.1\Omega = 1.66W$$

Conduction losses for Q2:

$$I_{RMS} = \sqrt{(1-D) \cdot \left(I_p \cdot I_m + \frac{\Delta I^2}{3} \right)} \quad \sqrt{(1-0.66) \cdot \left[5.5A \cdot 4.5A + \frac{(1A)^2}{3} \right]} = 2.92A$$

$$(2.92A)^2 \cdot 0.1\Omega = 0.85W$$

Additional losses are switching losses.

Q1: hard switching turn-on, hard switching turn-off;

Q2: zero-voltage switching turn-on, zero-voltage switching turn-off.

(Q1 charges C_{eq} every turn-on cycle):

$$P_{C_{eq}} = \frac{C_{eq} \cdot V^2}{2} \cdot f_{sw} \quad \frac{1nF \cdot (5V)^2}{2} \cdot 400kHz = 5mW$$

Q1 will be hotter than Q2

Problem 2

2.1)

$$\Delta I := 2A$$

The ripple due the ESR:

$$V_{ESR_{p-p}} = \Delta I \cdot ESR \quad 2A \cdot 10m\Omega = 20mV$$

The ripple due the output capacitor charge-discharge:

$$V_{Co} = \frac{\Delta I}{8 \cdot C_o \cdot f_{sw}} \quad \frac{2A}{8 \cdot 47\mu F \cdot 400kHz} = 13.3mV$$

2.2)

$$P_{Co} = (I_{Co_{RMS}})^2 \cdot ESR = \left(\frac{\Delta I}{\sqrt{12}} \right)^2 \cdot ESR \quad \left(\frac{2A}{\sqrt{12}} \right)^2 \cdot 10m\Omega = 3.33mW$$

2.3)

$$Q_{gate} := 30nC$$

$$I_{drive} = \frac{\Delta Q}{\Delta t}$$

$$\frac{30nC}{50ns} = 0.6A$$

Problem 3

3.1)

$$\Delta I := 1A \quad K := 0.5 \quad B_{max} := 0.3T \quad J := 4 \frac{A}{mm^2}$$

$$L := 2.81\mu H$$

$$AP = \frac{L \cdot I_p \cdot I_{L_{RMS}}}{J \cdot K \cdot B_{max}}$$

$$I_{L_{RMS}} = \sqrt{I_{Lav}^2 + \frac{\Delta I^2}{12}}$$

$$\sqrt{(5A)^2 + \frac{(1A)^2}{12}} = 5.01A$$

$$\frac{2.81\mu H \cdot 5.5A \cdot 5.01A}{4 \cdot 10^6 \frac{A}{m^2} \cdot 0.5 \cdot 0.3T} = 129.05 mm^4$$

3.2)

The conductivity of the copper wire is known: $\sigma_{cu_1} = x \left(\frac{\Omega^{-1}}{m} \right)$ (for specific wire diameter)

or $\sigma_{cu_2} = x \left(\Omega^{-1} \cdot m \right)$ (for any generic wire).

The effective core area A_e and other geometric parameters can be taken from the datasheet.


The Mean Length of Turn (MLT) can be taken from the datasheet too or calculated:

$$MLT = 2\pi r$$

$$R_L = \frac{MLT \cdot N}{\sigma_{cu_1}} = \frac{MLT}{\sigma_{cu_1}} \cdot \frac{L \cdot I_p}{B_{max} \cdot A_e}$$

or:
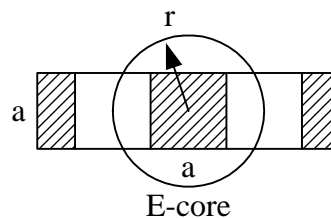
$$R_L = \frac{MLT \cdot N}{\sigma_{cu_2} \cdot A_{wire}} = \frac{MLT}{\sigma_{cu_2} \cdot A_{wire}} \cdot \frac{L \cdot I_p}{B_{max} \cdot A_e}$$



(supposing the wire area A_{wire} is given)

3.3)

$$R_L := 50m\Omega \quad P_{core} = 10 \cdot (\Delta B_{pp})^2 \frac{W}{cm^3} \quad V_e := 2cm^3$$

$$P_L = P_{core} + P_{cu}$$

$$P_{cu} = (I_{L_{RMS}})^2 \cdot R_L \quad (5.01A)^2 \cdot 50m\Omega = 1.26W$$

$$\frac{\Delta B}{B_{max}} = \frac{\mu \cdot \Delta H}{\mu \cdot H_{max}} = \frac{\frac{N \cdot \Delta I}{l}}{\frac{N \cdot I_p}{l}} = \frac{\Delta I}{I_p}$$

$$\Delta B = B_{max} \cdot \frac{\Delta I}{I_p} \quad 0.3T \cdot \frac{1A}{5.5A} = 54.5mT$$

$$P_{core} = 10 \cdot (\Delta B_{pp})^2 \cdot \frac{W}{cm^3} \cdot V_e \quad 10 \cdot (54.5 \cdot 10^{-3})^2 \cdot \frac{W}{cm^3} \cdot 2cm^3 = 59.4mW$$

$$1.26W + 59.4mW = 1.32W$$

Problem 4

$$L := 5\mu H$$

4.1)

$$\Delta I = \frac{V_o \cdot (1 - D)}{L \cdot f_{sw}} \quad \frac{3.3V \cdot (1 - 0.66)}{5\mu H \cdot 400kHz} = 0.56A$$

$$I_p = I_{Lav} + \frac{\Delta I}{2} \quad 5A + \frac{0.56A}{2} = 5.28A$$


$$I_m = I_{Lav} - \frac{\Delta I}{2} \quad 5A - \frac{0.56A}{2} = 4.72A$$

$$V_{Rs} = I_L \cdot R_s$$

$$\Delta V_{Rs} = \Delta I \cdot R_s \quad 0.56A \cdot 10m\Omega = 5.6mV$$


$$V_{Rs(peak)} = I_p \cdot R_s \quad 5.28A \cdot 10m\Omega = 52.8mV$$

$$V_i = 10 \cdot V_{Rs}$$

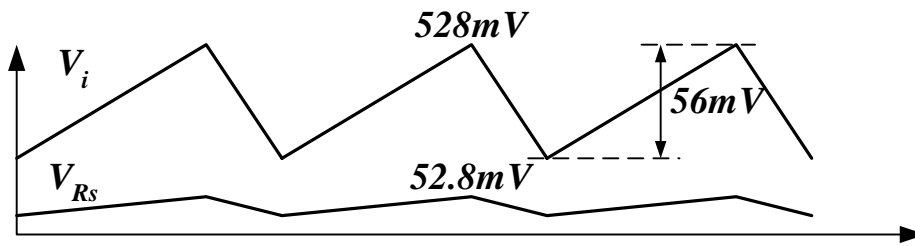

$$V_e = V_i(\text{peak}) = 528\text{mV}$$

4.2)

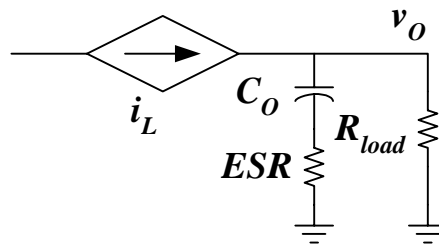

$$\frac{v_o}{v_e} = \frac{i_L \cdot Z_o}{v_e} = \frac{\frac{v_{Rs}}{R_s} \cdot Z_o}{v_e} = \frac{\frac{v_i}{10} \cdot \frac{Z_o}{R_s}}{v_e} = \frac{v_i}{v_e} \cdot \frac{Z_o}{10 \cdot R_s} = \frac{Z_o}{10 \cdot R_s} \quad \left(\frac{v_i}{v_e} = 1 \right)$$

$$Z_o = \frac{1}{\frac{1}{R_{load}} + \frac{1}{ESR + \frac{1}{j\omega \cdot C_o}}} = \frac{1}{\frac{1}{R_{load}} + \frac{j\omega \cdot C_o}{1 + j\omega \cdot C_o \cdot ESR}} = \frac{R_{load} \cdot (1 + j\omega \cdot C_o \cdot ESR)}{1 + j\omega \cdot C_o \cdot (ESR + R_{load})} = \dots$$

$$ESR \ll R_{load}$$

$$\dots = \frac{R_{load} \cdot (1 + j\omega \cdot C_o \cdot ESR)}{1 + j\omega \cdot C_o \cdot R_{load}}$$

$$\frac{v_o}{v_e} = \frac{R_{load}}{10 \cdot R_s} \cdot \frac{1 + j\omega \cdot C_o \cdot ESR}{1 + j\omega \cdot C_o \cdot R_{load}} \quad \frac{v_o}{v_e}(f) = \frac{R_{load}}{10 \cdot R_s} \cdot \frac{1 + j \cdot \frac{f}{f_z}}{1 + j \cdot \frac{f}{f_p}}$$

$$\frac{R_{load}}{10 \cdot R_s}$$

$$\frac{0.66\Omega}{10 \cdot 10\text{m}\Omega} = 6.6$$


$$20 \cdot \log(6.6) = 16.4$$

$$f_z = \frac{1}{2\pi \cdot C_o \cdot ESR}$$


$$\frac{1}{2\pi \cdot 47\mu\text{F} \cdot 10\text{m}\Omega} = 339\text{kHz}$$

$$f_p = \frac{1}{2\pi \cdot C_o \cdot R_{load}}$$
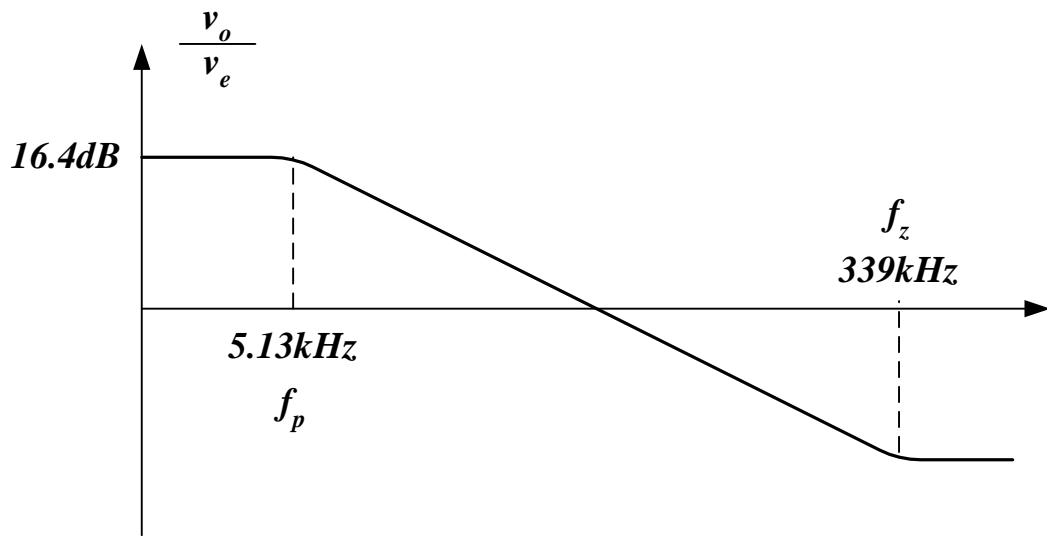
$$\frac{1}{2\pi \cdot 47\mu\text{F} \cdot 0.66\Omega} = 5.13\text{kHz}$$



4.3)

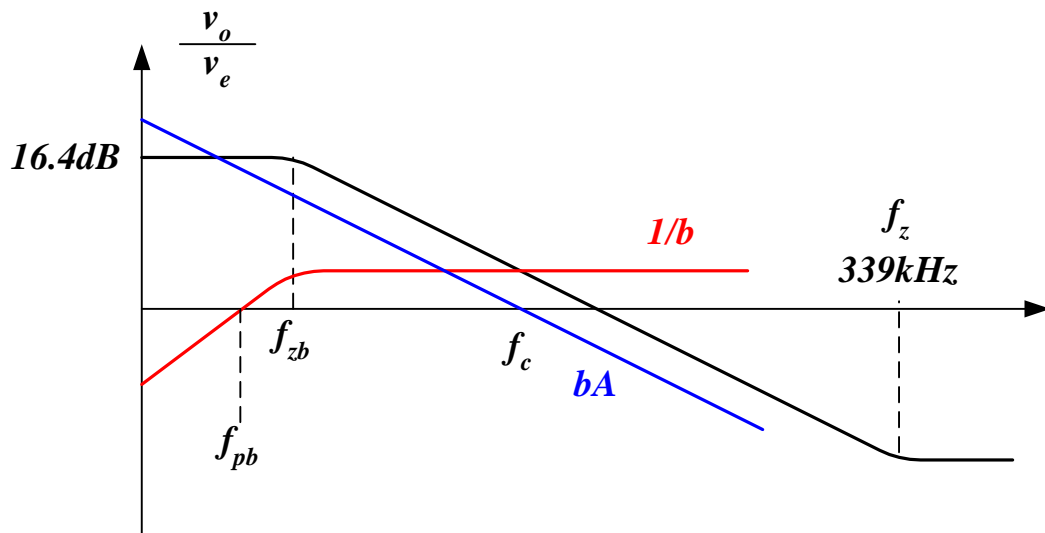

$$\beta = \frac{1 + j \cdot \frac{f}{f_z \beta}}{j \cdot \frac{f}{f_p \beta}} \quad f_z \beta = f_p = 5.13 \text{ kHz}$$

Open loop gain equals 0dB at: $5.13 \text{ kHz} \cdot 10^{\frac{16.4}{20}} = 33.9 \text{ kHz}$

Take crossover frequency at 20kHz: $f_c = 20 \text{ kHz}$

Then A_{OL} crosses $1/\beta$ at: $20 \cdot \log\left(\frac{33.9 \text{ kHz}}{20 \text{ kHz}}\right) = 4.58 \text{ dB}$

The β pole frequency: $5.13 \text{ kHz} \cdot 10^{\frac{-4.58}{20}} = 3.03 \text{ kHz}$

$$f_{p\beta} = 3.03\text{kHz} = \frac{1}{2\pi C_f \cdot R_i}$$

$$f_{z\beta} = 5.13\text{kHz} = \frac{1}{2\pi C_f \cdot R_f}$$

Take $C_f = 10\text{nF}$.

$$R_i = \frac{1}{2\pi C_f \cdot f_{p\beta}}$$

$$\frac{1}{2\pi 10\text{nF} \cdot 3.03\text{kHz}} = 5.25\text{k}\Omega$$

$$R_f = \frac{1}{2\pi C_f \cdot f_{z\beta}}$$

$$\frac{1}{2\pi 10\text{nF} \cdot 5.13\text{kHz}} = 3.1\text{k}\Omega$$