

Power Converters Control Technique

- 10.1 The Dynamic Problem
- 10.2 Control
 - 10.2.1 Modulator
 - 10.2.2 Oscillator
 - 10.2.3 Isolation
- 10.3 Design of feedback system
- 10.4 Frequency response of power converter
 - 10.4.1 Average Model – AC Analysis
 - 10.4.2 SPICE Linearization
 - 10.4.3 Example: Frequency response of the BUCK converter
- 10.5 Voltage Mode
- 10.6 Current Mode
 - 10.6.1 Current feedback
 - 10.6.2 Peak Current Mode (PCM) and Average Current Mode (ACM)
- 10.7 Parasitic Effects
 - 10.7.1 PCB trace resistance
 - 10.7.2 Correct layout
 - 10.7.3 Interfering signal injection
 - 10.7.4 Inductive coupling
 - 10.7.5 Stray inductance


The Dynamic Problem

A closed loop converter is a feedback system

Issues:

- Stability
- Rejection of input voltage variations (audio susceptibility)
- Resistance to load changes
- Quick response to reference change - good tracking. Important for variable output voltage working in close loop.


The Dynamic Problem

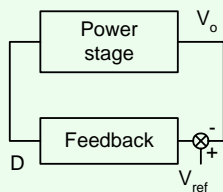

Power stage is a Switching system

Feedback is analog (or digital) control


Closed Loop

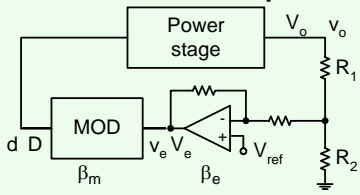

$\frac{v_o}{v_e}(f)$ – Analog Function


Feedback factor v_e (small signal) into d (small signal)

The Concept of d

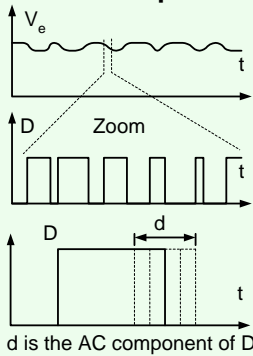


d is the AC component of D


Control

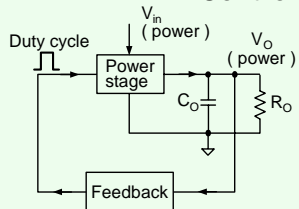

The power conversion system

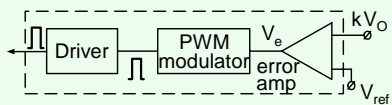


Modulator

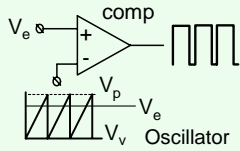

$$V_t = \frac{(V_p - V_v)t}{T_s} + V_v$$

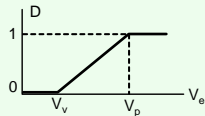
$$V_t = V_e = \frac{(V_p - V_v)t_{on}}{T_s} + V_v$$




$$\frac{t_{on}}{T_s} = D_{on} = \frac{(V_e - V_v)}{V_p - V_v}$$

Practical $D_{on\ max} \approx 0.8 \div 0.9$

Oscillator

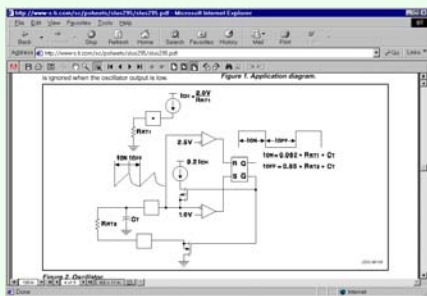


Complete controller - Voltage Mode (VM)

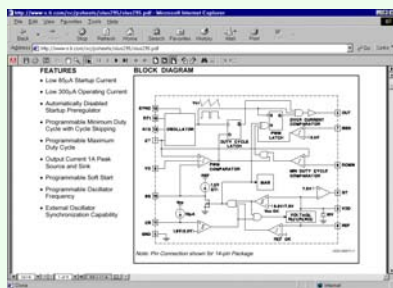


- This controller does not include an error amplifier

Primary to secondary isolation


The problem :

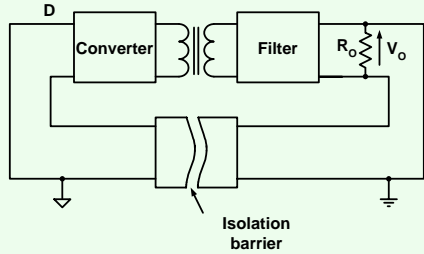

Feedback Alternatives

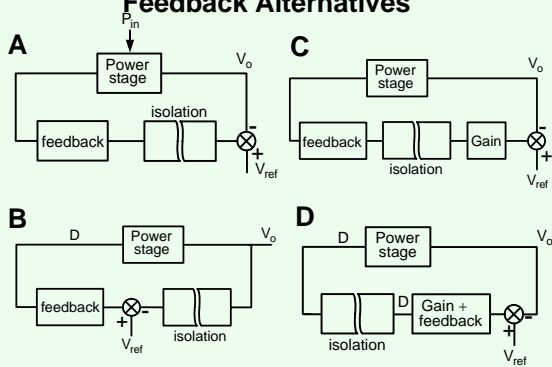

Output Voltage Sampler

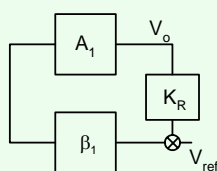


$$\left(\frac{V_o}{V_{ref}} \right) = \frac{\beta_1 A_1}{1 + \beta_1 A_1 K_R}$$

$$\beta_1 A_1 K_R > 1$$

$$\left(\frac{V_o}{V_{ref}} \right) = \frac{1}{K_R}$$

LoopGain

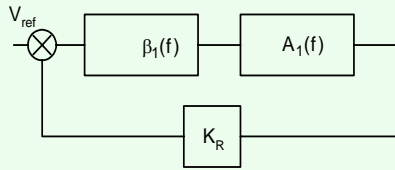


Stability and dynamic response depend on Loop Gain (LG)

$$LG = K_R \beta_1(f) A_1(f)$$

General representation

$$LG = A(f) \beta(f)$$

Bode Plot

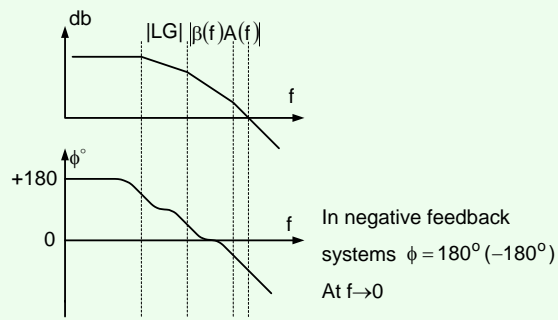


Nyquist Criterion

$$A_{CL} = \frac{A(s)}{1+LG(s)}$$


- The system is unstable if $\{1+LG(s)\}$ has roots in the right half of the complex plane.
- Nyquist criterium is a test for location of $\{1+LG(s)\}$ roots.
- Nyquist criterium is normally translated into the Bode plane (frequency domain)

Bode Presentation

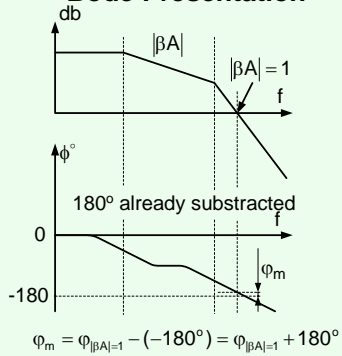


The design problem

Given $A(f)$
Find $\beta(f)$

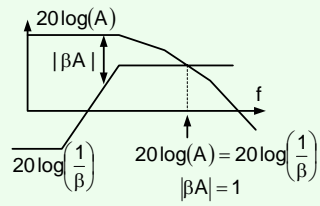


$$20\log(A) - 20\log\left(\frac{1}{\beta}\right) = 20\log(\beta A)$$


LG=1

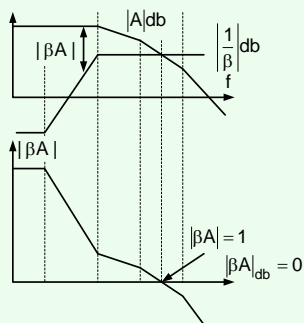


Rate of Closure

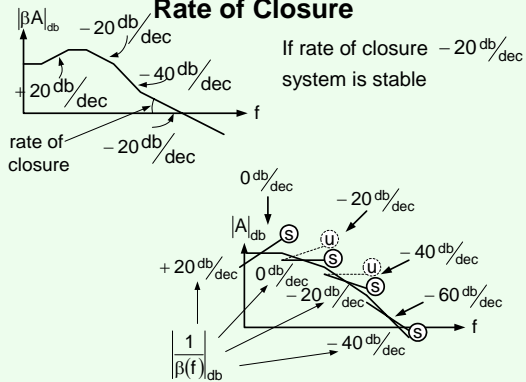



Bandwidth

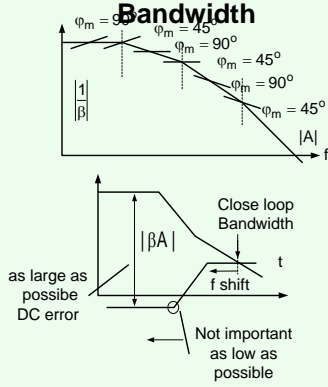


Phase Margin Effects

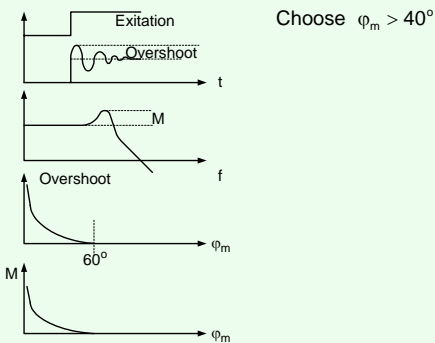

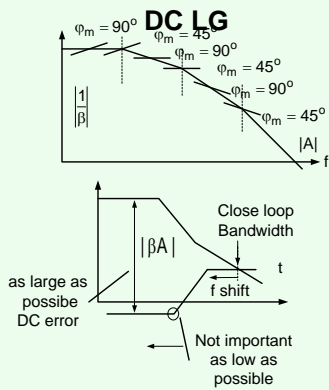

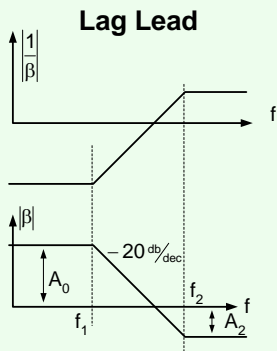


Average Model – AC Analysis

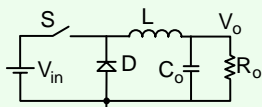

$$E_{in} = V_{in} \cdot D_{on}$$


$$G_b = \bar{I}_L \cdot D_{on}$$

$$E_{in} - V_o \rightarrow \bar{V}_L$$

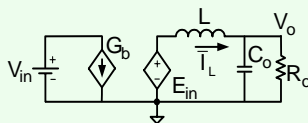

Polarity: (voltage and current sources) selected by inspection

Linearization


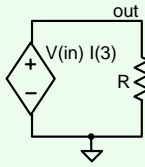


$$V(out) = V(in) * I(3)$$

$$d(V(out)) = \frac{\partial(V(out))}{\partial(V(in))} v(in) + \frac{\partial(V(out))}{\partial(I(3))} i(3)$$

$$V(out) = \frac{\Delta V(out)}{\Delta V(in)} v(in) + \frac{\Delta V(out)}{\Delta I(3)} i(3)$$


SPICE Linearization (AC Analysis)

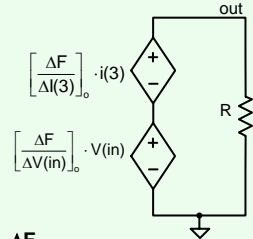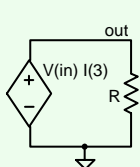

$$\frac{\Delta F}{\Delta V(in)} = I(3)_0$$


$$\frac{\Delta F}{\Delta I(3)} = V(in)_0$$

Buck linearization

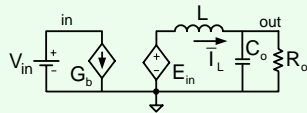


$$E_{in} = V_{in} D$$


$$G_b = \bar{I}_L D$$

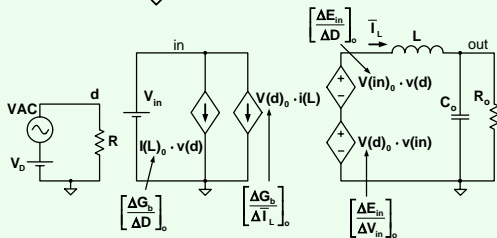


Example: Buck Average Model Simulations

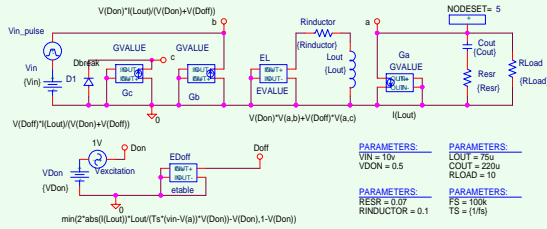

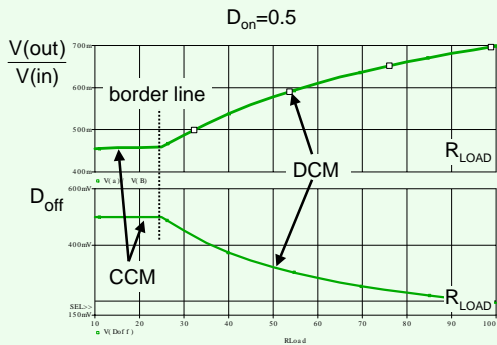Example: Buck DC Sweep Analysis (CCM/DCM)



Example: Buck AC Analysis (CCM/DCM)

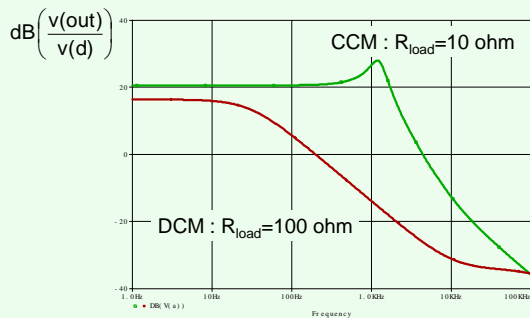

Buck AC Analysis (CCM/DCM) file .out


```

**** SMALL SIGNAL BIAS SOLUTION   TEMPERATURE = 27.000 DEG C
**** CURRENT STEP                 PARAM RLOAD = 10
-----
NODE VOLTAGE  NODE VOLTAGE  NODE VOLTAGE  NODE VOLTAGE
( a) 4.5455   ( B) 10.0000   ( C) -0.8182   ( DCM) .5000
(DcM) .5000 (N000069) -.0455 (N00141) 0.0000 (N000071) .5000 (N000230) 0.0000

VOLTAGE SOURCE CURRENTS
NAME      CURRENT
V_Vestabtn  0.000E+00
V_VDcm      0.000E+00
V_Vin       -2.273E-01

**** CURRENT STEP                 PARAM RLOAD = 100
-----
NODE VOLTAGE  NODE VOLTAGE  NODE VOLTAGE  NODE VOLTAGE
( a) 6.9835   ( B) 10.0000   ( C) -7.340   ( DCM) .5000
(DcM) .1945 (N000069) -.0070 (N00141) 0.0000 (N000071) .5000 (N000230) 0.0000

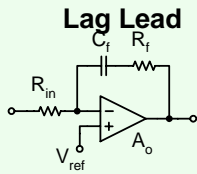VOLTAGE SOURCE CURRENTS
NAME      CURRENT
V_Vestabtn  0.000E+00
V_VDcm      0.000E+00
V_Vin       -5.029E-02
    
```




$$A_o = A_{OL} \text{ (ampl.)}$$

$$f_L = \frac{1}{2\pi C_f R_f}$$


$$A_2 = \frac{R_f}{R_{in}}$$

Exercise

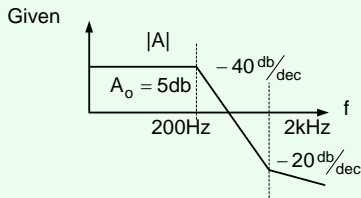

Design β and feedback circuit for $f_{cl}=5\text{kHz}$

Power Stage Example

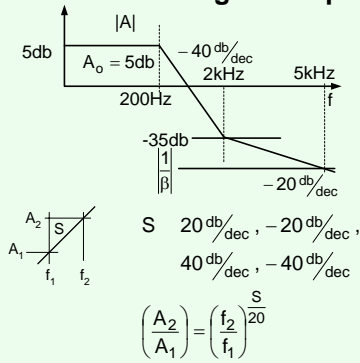

Pole Zero

$$\frac{A_1}{A_2} = \left(\frac{5}{2}\right)^{-1}$$



$$A_2 = A_1 \left(\frac{2}{5}\right)^1$$

$$A_{2_{\text{db}}} = A_{1_{\text{db}}} + 20 \lg\left(\frac{2}{5}\right)$$


$$A_{2_{\text{db}}} = 35 + (-7.5) = -42.5\text{db}$$

$$C = \frac{1}{2\pi R 1\text{kHz}} = 0.59\text{nF}$$

$$\frac{1}{2\pi RC} = 1\text{kHz}$$

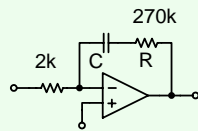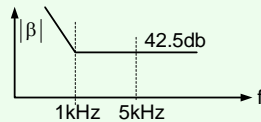


Problem?

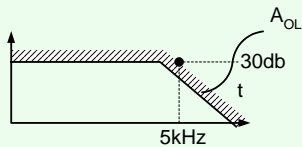


Operational amplifier limitation

Buck

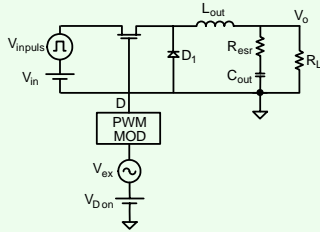

File: Buck_cy_by_cy.SCH

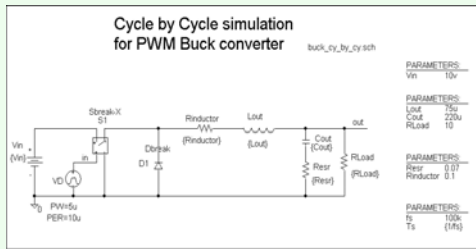


Current Feedback

- The problem: transfer function is second order
- Solution: Add current Feedback


System order is reduced for each state variable feedback

Current Feedback

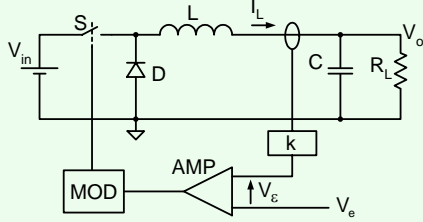


- For strong feedback ($A_{OL} \gg 1$):
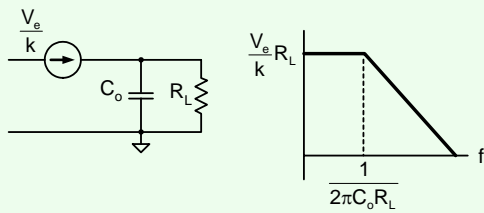
$$I_L = \frac{1}{k} V_e \quad (V_e \rightarrow 0)$$




- First order system !

PCM & ACM

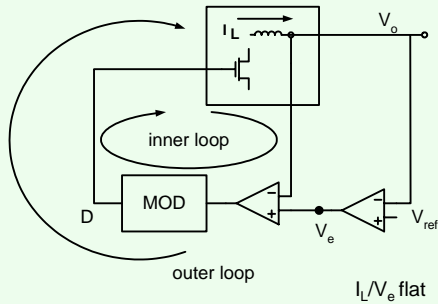


Current mode (CM) control

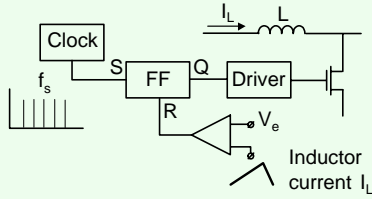


$$\frac{V_o}{V_{in}} = f(D_{on}) \text{ is the same !}$$

Implementation CM Boost

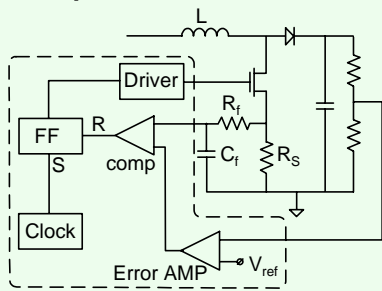

Some controllers have amplifiers for sensed current

CM Controller

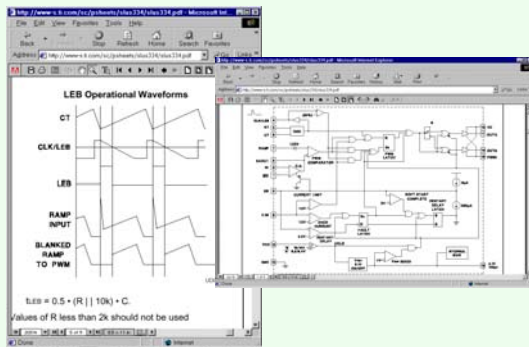


Advantages of peak CM (PCM)

- * Cycle by cycle protection
- * Better dynamics


Disadvantages

- * Loading edge spike
- * Subharmonic oscillation


The nature of Subharmonic Oscillations

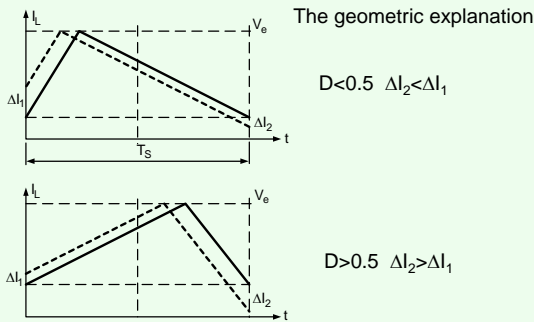

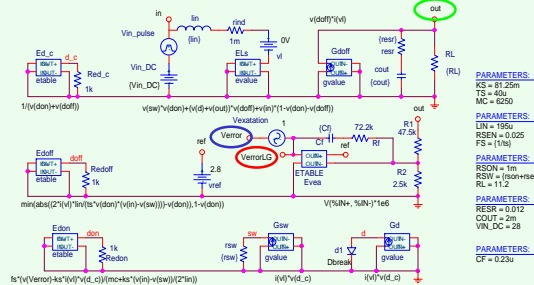
BOOST Average Model AC analysis PCM (CCM & DCM)




BOOST Average Model Simulation

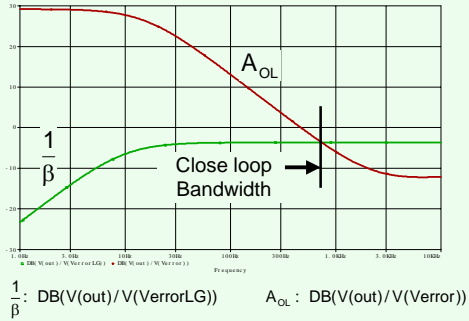

BOOST Average Model Simulation

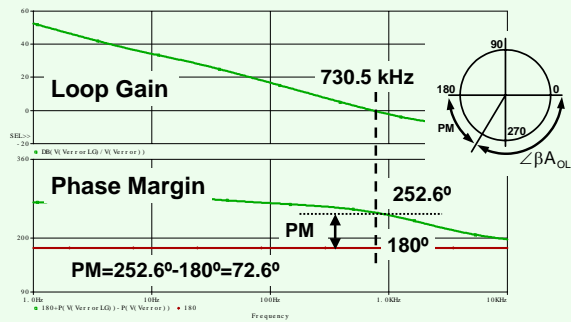


Average Current Mode (ACM) Control

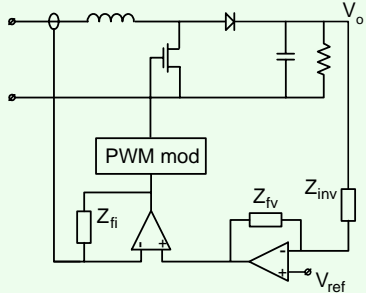

Current is filtered first to take out high frequency (f_s)

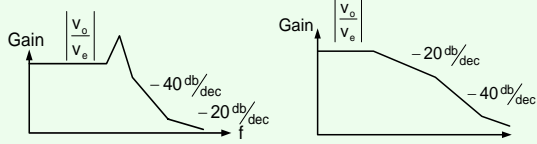
The advantages of current feedback (PCM or ACM)



Typical power stage VM

Same power stage (outer loop) with CM


Parasitic effects: PCB trace resistance

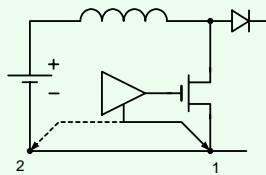

$$V_1 \neq V_2$$


Ground Noise

Separate power ground from signal ground

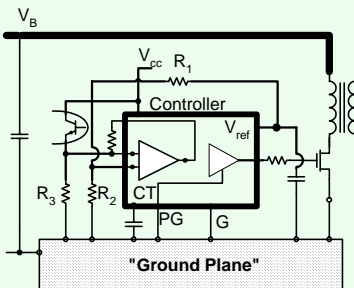


This circuit will probably not work. Why ?

Correct layout

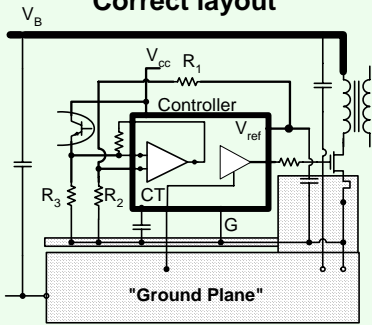


Do not rely on "Ground Plane"


Schottky Diodes

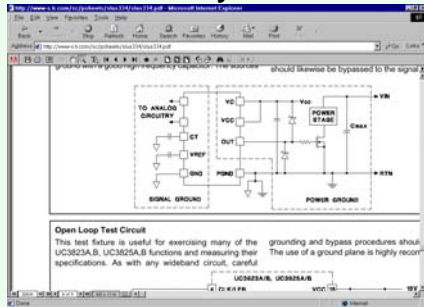

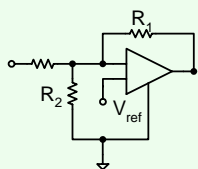
Parasitic effects: Interfering signal injection



Sensitive Part-Capacitive coupling

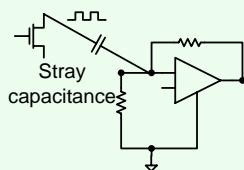


Parasitic effects: Inductive coupling

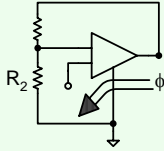

Do not put sensitive elements close to high voltage pulses or close to magnetic elements


Current Loop Area

Avoid wide power line loops

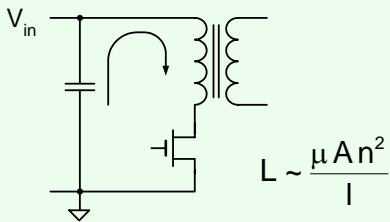


Stray inductance is proportional to area. So is the radiated wave.

Loop Area

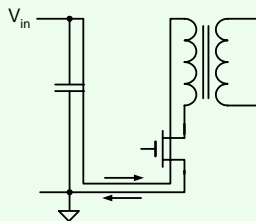

Best way is to run the forward-return paths on two sides of the PCB

Parasitic effects: Stray inductance

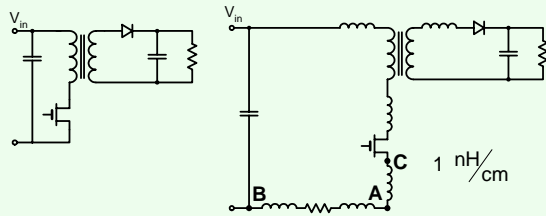

Two points on power PCB trace will never have same potential $V_A \neq V_B \neq V_C$
