

## BUCK, BOOST, BUCK-BOOST, DCM

- 2.1 Buck converter
  - 2.1.1 Operation modes
  - 2.1.2 Voltage transfer function
  - 2.1.3 Current modes (CCM, DCM)
  - 2.1.4 Capacitor current
- 2.2 Boost converter
  - 2.2.1 Operation modes
  - 2.2.2 Voltage transfer function
- 2.3 Buck-Boost converter
- 2.4 Comparison between topologies
- 2.5 Simulation of SMPS
  - 2.5.1 The simulations problem
  - 2.5.2 Basics of average model of SMPS
  - 2.5.3 Example: Boost average model simulations

---

---

---

---

---

---



---

---

---

---
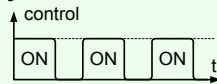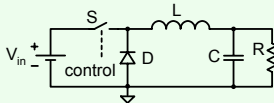
## Buck Converter Constant Switching Frequency




Switch frequency:  $f_s = \frac{1}{T_s}$

Duty Cycle:

$$\frac{t_{on}}{T_s} = D_{on} \quad \text{or} \rightarrow D$$
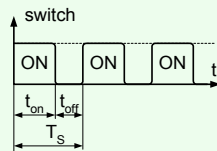
$$\frac{t_{off}}{T_s} = D_{off} \quad \rightarrow 1 - D$$




---

---

---

---

---

---

---



---

---



---

## Operation modes

**On**

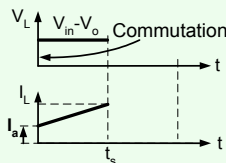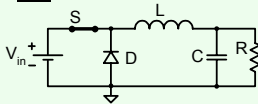

**Off**

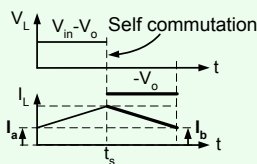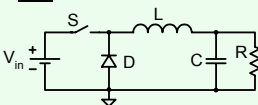

At steady state  $I_a = I_b$

---

---

---

---

---

---

---


---

---


---

**Buck**

In this case

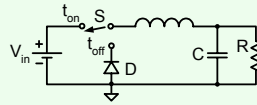

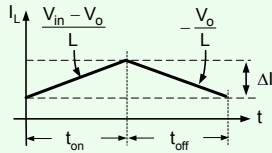Inductor current waveform at steady state




---

---

---

---

---

---


---

---

---

---

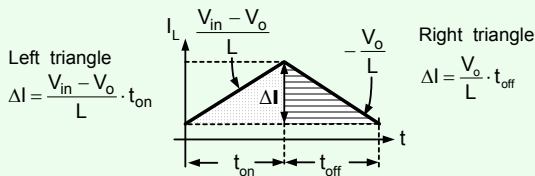**Voltage transfer function**  
The ΔI method



Left triangle  
$$\Delta I = \frac{V_{in} - V_o}{L} \cdot t_{on}$$

Right triangle  
$$\Delta I = \frac{V_o}{L} \cdot t_{off}$$

$$\left( \frac{V_{in} - V_o}{L} \right) t_{on} = \frac{V_o}{L} t_{off}$$

$$\frac{V_o}{V_{in}} = \frac{t_{on}}{t_{on} + t_{off}} = \frac{t_{on}}{T_s} = D_{on} \quad \text{Independent of L !}$$

---

---

---

---

---

---


---

---

---

---

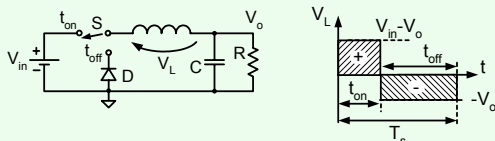**Voltage transfer function**  
The average voltage method



At steady state, over one switching cycle:

- $\bar{V}_L = 0;$
- $S_+ = (V_{in} - V_o) \cdot t_{on};$
- $S_- = (-V_o) \cdot t_{off};$
- $S_+ + S_- = 0 \Rightarrow \frac{V_o}{V_{in}} = D_{on}$

---

---

---

---

---

---


---

---

---

---

### Load Change with Fixed D

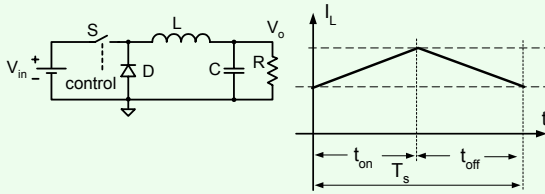

How will  $I_L$  change if R is getting smaller?

---

---

---

---

---

---


---

---

---

---

### Load Change

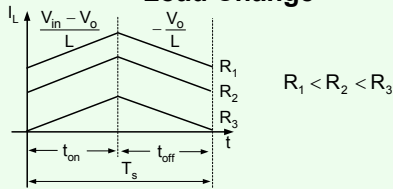

CCM - Continues Conductor Current Mode  
DCM - Discontinues Conductor Current Mode

---

---

---

---

---

---


---

---

---

---
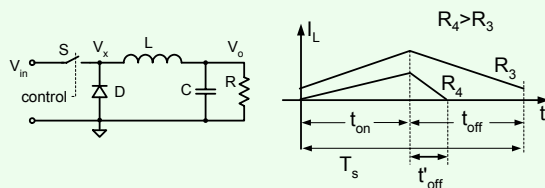
### Discontinuous Inductor Current Mode (DCM)



- Different voltage transfer ratio  $\neq D_{on}$
- Higher ripple current

---

---

---

---

---

---


---

---

---

---

### Voltage transfer function (DCM)

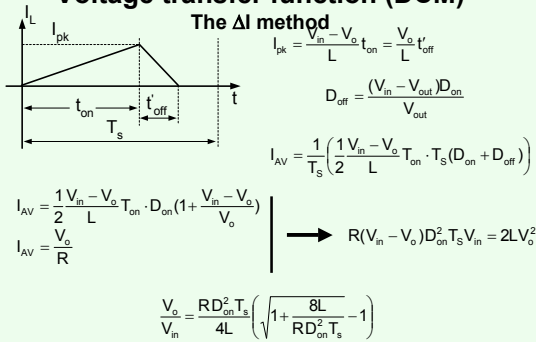


---

---

---

---

---

---


---

---

---

---

### Boundary of CCM and DCM

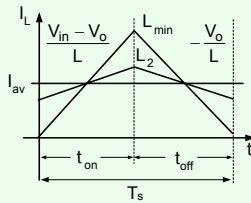

- For CCM  $L > L_{min}$
- In Buck  $\frac{V_o}{L_{min}} t_{off} = I_{pk} = 2I_{av}$   $L_{min} = \frac{V_o D_{off}}{2I_{av} f_s} = \frac{RD_{off}}{2f_s}$

---

---

---

---

---

---

---

---

---

---

### Example

A BUCK converter has a following characteristics:  
 Output voltage:  $V_o = 5V$     Output current:  $I_{out} = I_{av} = 10A$   
 Input voltage:  $V_{in} = 10V$     Frequency:  $f_s = 100kHz$   
 Current mode: CCM

Find:  $L_{min}$

$$\frac{V_o}{V_{in}} = D_{on} = 0.5 \quad \xrightarrow{\text{CCM}} \quad D_{off} = 1 - D_{on} = 0.5$$

$$L_{min} = \frac{V_o D_{off}}{2I_{av} f_s} = \frac{5 \cdot 0.5}{2 \cdot 10 \cdot 10^5} = 1.2 \mu H$$

---

---

---

---

---

---



---

---

---


---

### Capacitor current

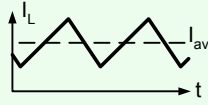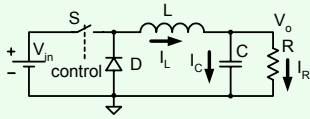


- Assumption:

$V_o$  has small ripple

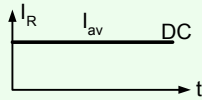

$$I_C = I_L - I_R$$

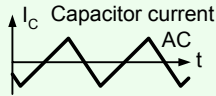


---

---

---

---


---

---

---

---

### BOOST Step-Up

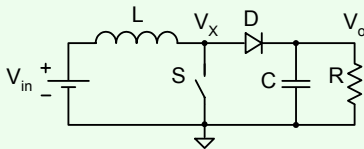

- $V_o > V_{in}$  Why ??

---

---

---

---

---



---

---



---

### Operational Modes

**ON**  $V_L = V_{in}$

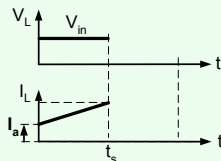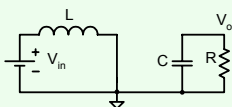

**OFF**  $V_L = V_{in} - V_o$

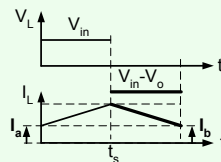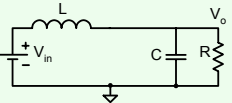


---

---

---

---


---

---

---

---
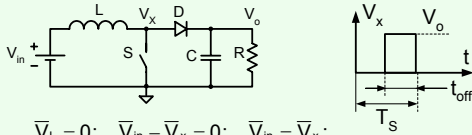
### Voltage transfer function The average voltage method



$$\bar{V}_L = 0; \quad \bar{V}_{in} - \bar{V}_x = 0; \quad \bar{V}_{in} = \bar{V}_x;$$

$$V_{in} = \bar{V}_{in};$$

$$\bar{V}_x = \frac{V_o t_{off}}{T_s} = V_o D_{off};$$

$$V_{in} = V_o D_{off} \rightarrow \frac{V_o}{V_{in}} = \frac{1}{D_{off}}$$

---

---

---

---


---

---

---

---
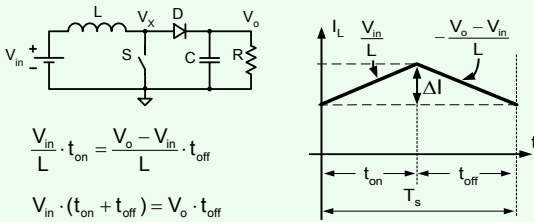
### Voltage transfer function The $\Delta I$ method



$$\frac{V_{in}}{L} \cdot t_{on} = \frac{V_o - V_{in}}{L} \cdot t_{off}$$

$$V_{in} \cdot (t_{on} + t_{off}) = V_o \cdot t_{off}$$

$$\frac{V_o}{V_{in}} = \frac{1}{D_{off}}$$

---

---

---

---


---

---

---

---

### BUCK-BOOST Step-Up Step-Down

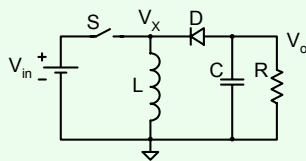

- Find  $V_o/V_{in}$   
Hint: Average of  $V_x$  ?

---

---

---

---


---

---

---

---

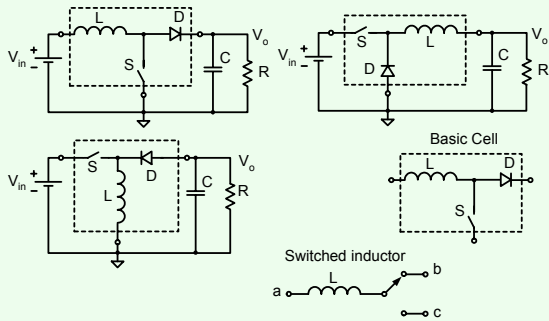**Comparison between basic topologies CCM**




---

---

---

---


---

---

---

---

**Input and Output Currents**

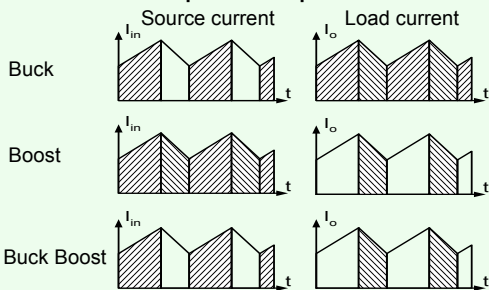

Continues current -> Low ripple component  
 Discontinues current -> High ripple component

---

---

---

---


---

---

---

---

**The simulation problem**

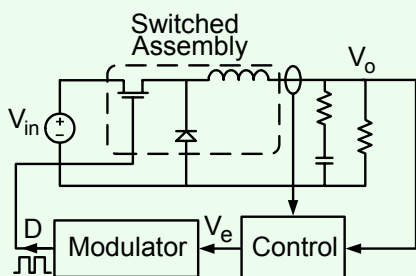


---

---

---

---


---

---

---

---

### The simulation problem

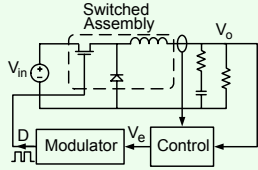

- The problematic part : Switched Assembly
- Rest of the circuit continuous - SPICE compatible
- Only possible simulation :  
Time domain (cycle-by-cycle) - Transient
- The objective : translate the  
Switched Assembly into an equivalent  
circuit which is SPICE compatible

---

---

---

---

---

---


---

---

---

---

### Average Simulation of PWM Converters

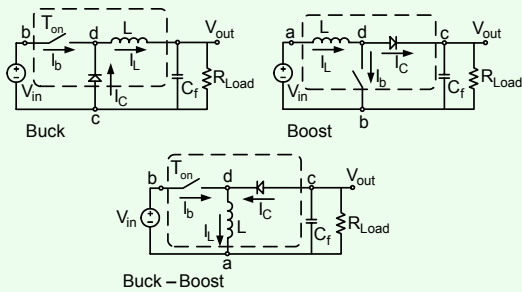


---

---

---

---

---

---


---

---

---

---

### The Switched Inductor Model

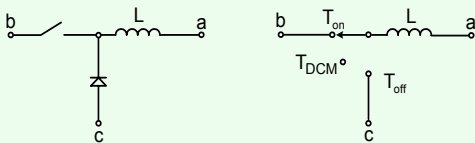

- $T_{on}$  - switch conduction time
- $T_{off}$  - diode conduction time
- $T_{DCM}$  - no current time (in DCM)

---

---

---

---

---

---

---

---


---

---



### The Switched Inductor Model (SIM) (CCM)

The concept of average signals

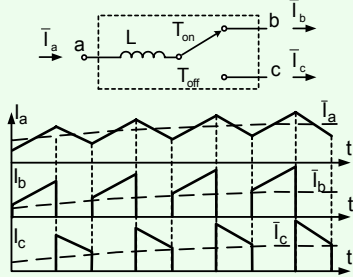


---

---

---

---

---


---

---

---
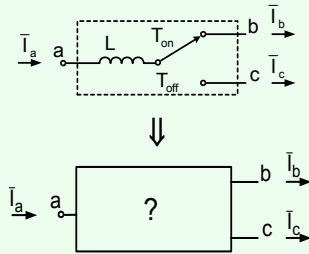
### The SIM

Objective : To replace the switched part by a continuous network




---

---

---

---


---

---

---

---

### Average current

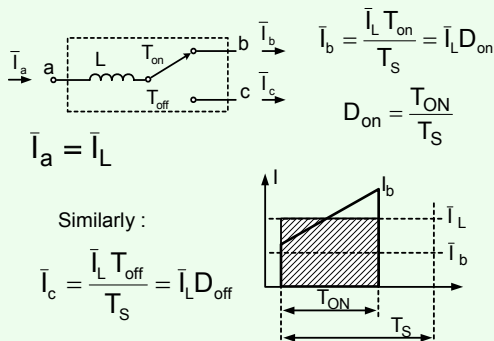


---

---

---

---


---

---

---

---

**Toward a continuous model**

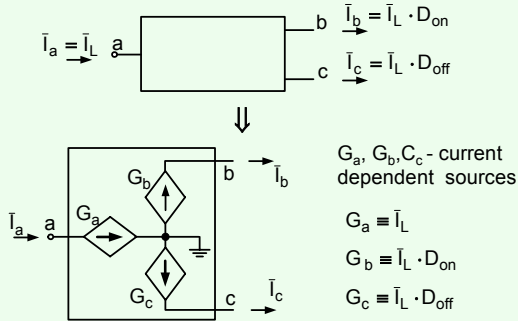


---

---

---

---

---

---


---

---

**Average inductor current**

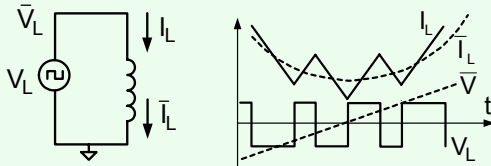**Deriving  $\bar{I}_L$**

$$\frac{dI_L}{dt} = \frac{V_L}{L} \Rightarrow \frac{d\bar{I}_L}{dt} = \frac{\bar{V}_L}{L}$$




---

---

---

---


---

---

---

---

**Average inductor current**

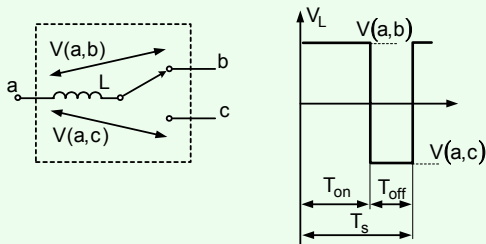

$$\bar{V}_L = \frac{V(a,b) \cdot T_{on} + V(a,c) \cdot T_{off}}{T_s} = V(a,b) \cdot D_{on} + V(a,c) \cdot D_{off}$$

---

---

---

---


---

---

---

---
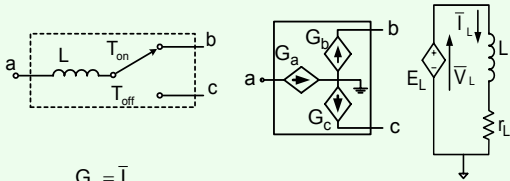
### The Generalized Switched Inductor Model (GSIM)



$$G_a = \bar{I}_L$$

$$G_b = \bar{I}_L \cdot D_{on}$$

$$G_c = \bar{I}_L \cdot D_{off}$$

$$E_L = V(a,b) \cdot D_{on} + V(a,c) \cdot D_{off}$$

Topology independent !

---

---

---

---

---


---

---

---

### Example Implementation in Buck Topology

1. The formal approach

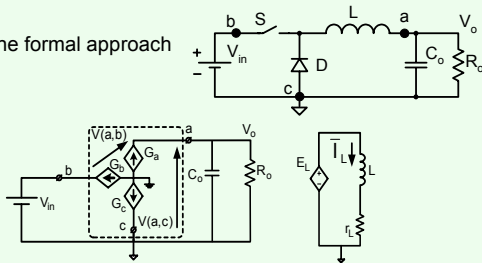

$$G_a = \bar{I}(L) \quad G_b = \bar{I}(L) \cdot D_{on} \quad G_c = \bar{I}(L) \cdot D_{off}$$

$$E_L = [V_o - V_{in}] \cdot D_{on} + [0 - V_o] \cdot D_{off}$$

---

---

---

---

---


---

---

---

### Implementation in Buck Topology

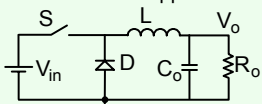
2. The intuitive approach - by inspection



$$E_{in} = V_{in} \cdot D_{on}$$

$$G_b = \bar{I}_L \cdot D_{on}$$

$$E_{in} - V_o \rightarrow \bar{V}_L$$

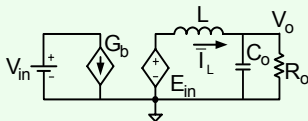

Polarity: (voltage and current sources) selected by inspection

---

---

---

---


---

---

---

---

**Boost**

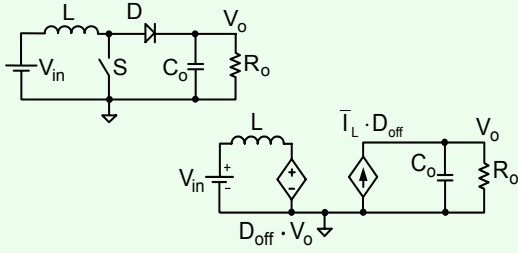

- Emulate average voltage on inductor
- Create  $\bar{I}_L$  dependent current sources

---

---

---

---


---

---

---

---

**Buck-Boost**

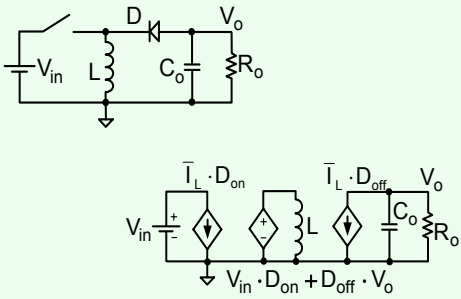


---

---

---

---


---

---

---

---

**Partially accounting for parasitics**

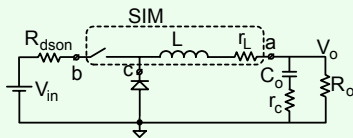


---

---

---

---


---

---

---

---

### Modified Average Model

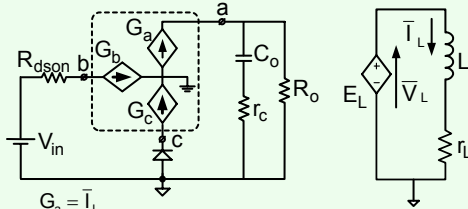

$$G_a = \bar{I}_L$$

$$G_b = \bar{I}_L \cdot D_{on}$$

$$G_c = \bar{I}_L \cdot D_{off}$$

$$E_L = (V_a - V_b) \cdot D_{on} + (V_a - V_c) \cdot D_{off}$$

---

---

---

---


---

---

---

---

### Making the model SPICE compatible

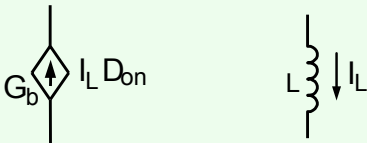

$I_L$  and  $D_{on}$  are time dependent variables  $\{I_L(t), D_{on}(t)\}$   
 $D_{on}$  is not an electrical variable

---

---

---

---


---

---

---

---

### In SPICE environment

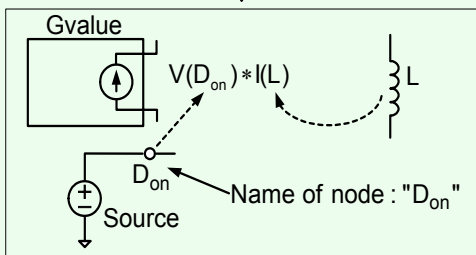

$D_{on}$  is coded into voltage

---

---

---

---

---

---

---

---

### Simulation

Running SPICE simulation

DC (steady state points) - as is

TRAN (time domain) - as is

AC ( small signal) - as is

\* Linearization is done by simulator !

---

---

---

---


---

---

---

---

### Discontinuous Model (DCM)

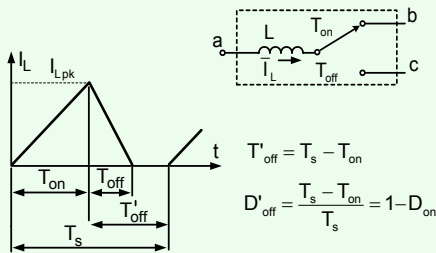


---

---

---

---

---


---

---

---

### Combining CCM / DCM

1. The average inductor current in DCM

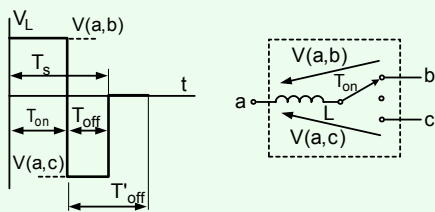

$\bar{V}_L = V(a,b)D_{on} + V(a,c)D_{off}$  as in CCM

---

---

---

---



---

---

---

---

### Combining CCM / DCM

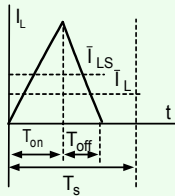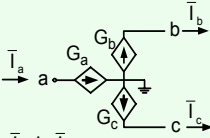

- \*  $\bar{I}_a$  is  $\bar{I}_L$
- \*  $\bar{I}_b$  is sampled during  $T_{on}$
- \*  $\bar{I}_c$  is sampled during  $T_{off}$
- \*  $\bar{I}_b$  is  $\bar{I}_c$  are sampling  $\bar{I}_{LS}$

$$\bar{I}_{LS} = \frac{\bar{I}_L T_s}{T_{on} + T_{off}} = \frac{\bar{I}_L}{D_{on} + D_{off}}$$

---

---

---

---

---

---



---

---

---

---

### Combining CCM / DCM

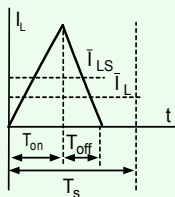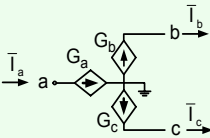

$$G_a = \bar{I}_L$$

$$G_b = \frac{\bar{I}_L D_{on}}{D_{on} + D_{off}}$$

$$G_c = \frac{\bar{I}_L D_{off}}{D_{on} + D_{off}}$$

in CCM:  $(D_{on} + D_{off}) = 1$

---

---

---

---

---

---

---

---

---

---

### Doff in DCM

$$I_{pk} = \frac{V(a,b)T_{on}}{L}$$


$$\bar{I}_L = \frac{1}{2} \left( \frac{V(a,b)T_{on}}{L} \right) \frac{(T_{on} + T_{off})}{T_s}$$

$$\bar{I}_L = \frac{V(a,b)D_{on}}{2Lf_s} (D_{on} + D_{off})$$

$$D_{off} = \frac{2\bar{I}_L L f_s}{V(a,b)D_{on}} - D_{on}$$

$$D'_{off} = 1 - D_{on}$$

$$D_{off} \leq 1 - D_{on}$$

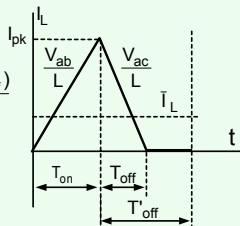


---

---

---

---

---

---


---

---

---

---

### The combined DCM / CCM mode

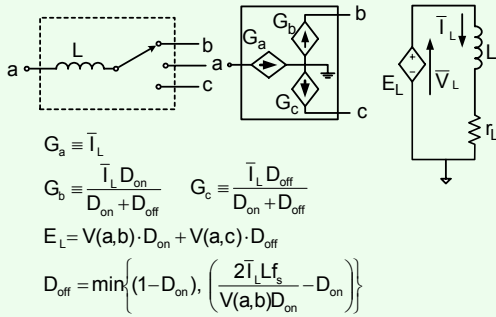


---

---

---

---

---

---


---

---


---

---
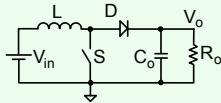
### Example: Boost average model simulation



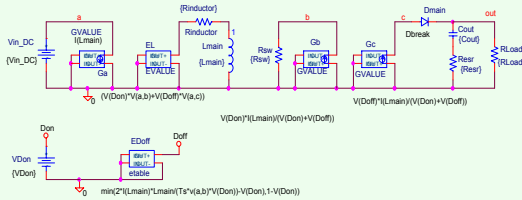**PARAMETERS:**  
 VIN\_DC = 15v  
 VDON = 0.5  
 LMAIN = 75u  
 COUT = 220u  
 RLOAD = 10  
 RESR = 0.07  
 RINDUCTOR = 0.1  
 RSW = 0.1  
 FS = 100k  
 TS = (1/FS)




---

---

---

---

---

---


---

---

---

---
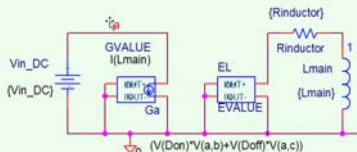
### Example: Boost average model simulation




---

---

---

---

---

---

---



---

---

---


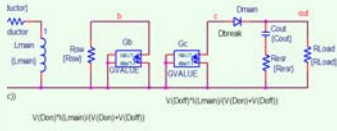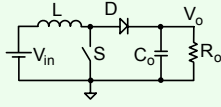
### Example: Boost average model simulation



---

---

---

---



---

---

---

---
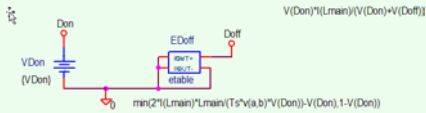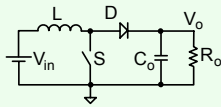
### Example: Boost average model simulation



---

---

---

---


---

---

---

---
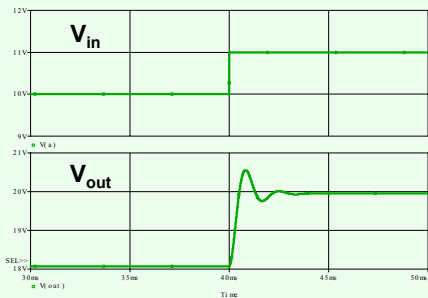
### Boost: Response to step of input voltage (average model simulation)



---

---

---

---


---

---

---

---
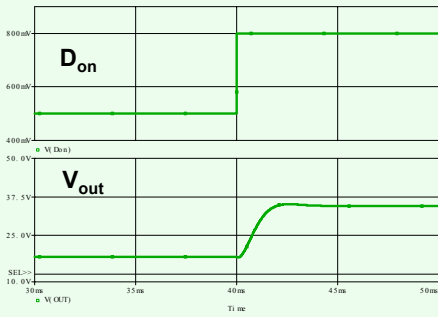
### Boost: Response to step of duty cycle




---

---

---

---

---

---

---


---

---

---

### Boost transfer function (CCM)

DC Sweep simulation

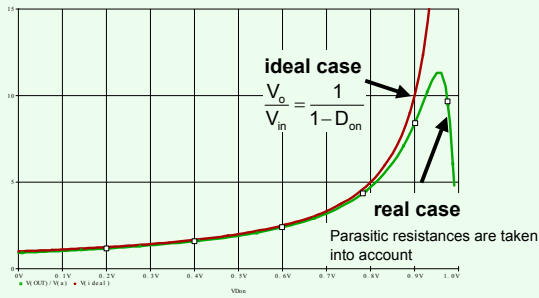


---

---

---

---

---

---

---

---

---

---