

BUCK, BOOST, BUCK-BOOST, DCM

2.1 Buck converter

- 2.1.1 Operation modes
- 2.1.2 Voltage transfer function
- 2.1.3 Current modes (CCM, DCM)
- 2.1.4 Capacitor current

2.2 Boost converter

- 2.2.1 Operation modes
- 2.2.2 Voltage transfer function


2.3 Buck-Boost converter

2.4 Comparison between topologies

2.5 Simulation of SMPS

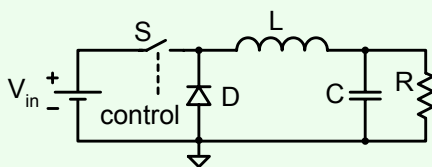- 2.5.1 The simulations problem
- 2.5.2 Basics of average model of SMPS
- 2.5.3 Example: Boost average model simulations

Buck Converter Constant Switching Frequency





Switch frequency: $f_s = \frac{1}{T_s}$

Duty Cycle:



$$\frac{t_{on}}{T_s} = D_{on} \quad \text{or} \rightarrow D$$
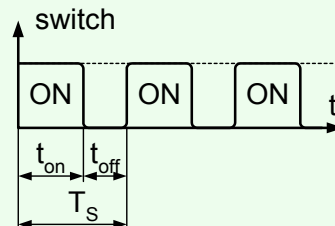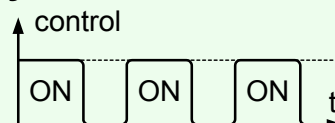
$$\frac{t_{off}}{T_s} = D_{off} \quad \rightarrow 1 - D$$





Operation modes

On

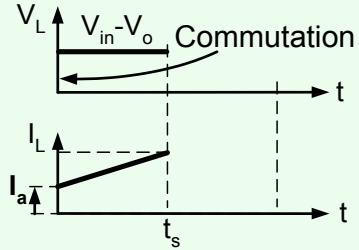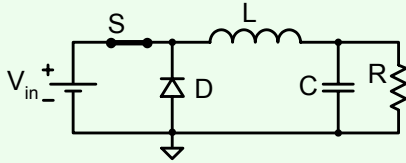


Off

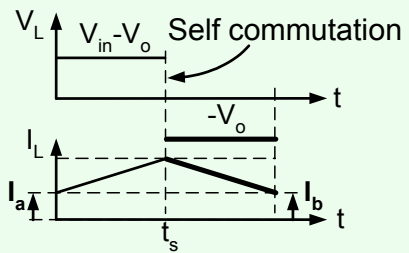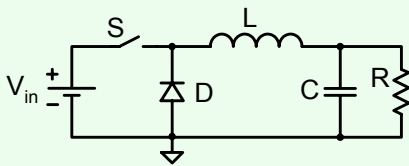


At steady state $I_a = I_b$

Buck

In this case

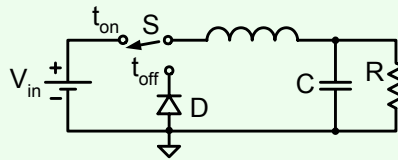

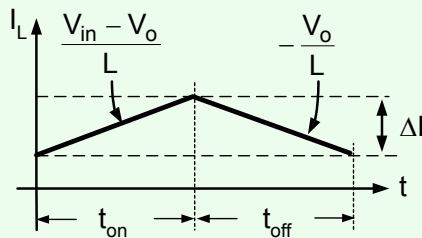
Inductor current waveform at steady state



Voltage transfer function The ΔI method

Left triangle
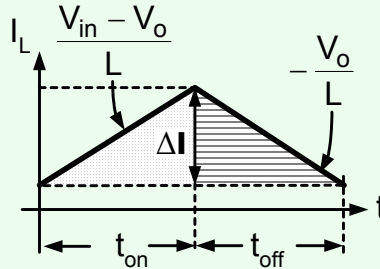
$$\Delta I = \frac{V_{in} - V_o}{L} \cdot t_{on}$$



Right triangle



$$\Delta I = \frac{V_o}{L} \cdot t_{off}$$

$$\left(\frac{V_{in} - V_o}{L} \right) t_{on} = \frac{V_o}{L} t_{off}$$

$$\frac{V_o}{V_{in}} = \frac{t_{on}}{t_{on} + t_{off}} = \frac{t_{on}}{T_s} = D_{on}$$

Independent of L !

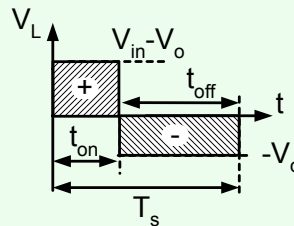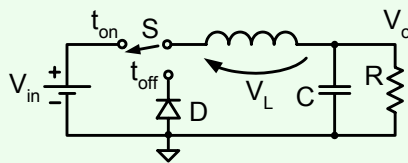
Voltage transfer function The average voltage method



At steady state, over one switching cycle:


$$\begin{aligned} \bar{V}_L &= 0; \\ S_+ &= (V_{in} - V_o) \cdot t_{on}; \\ S_- &= (-V_o) \cdot t_{off}; \\ S_+ + S_- &= 0 \Rightarrow \frac{V_o}{V_{in}} = D_{on} \end{aligned}$$

Load Change with Fixed D

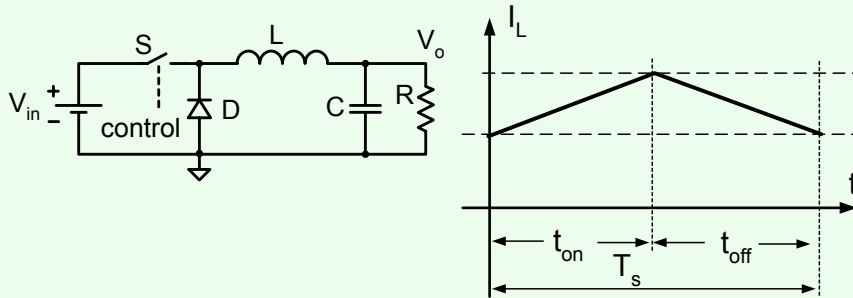

How will I_L change if R is getting smaller?


Load Change

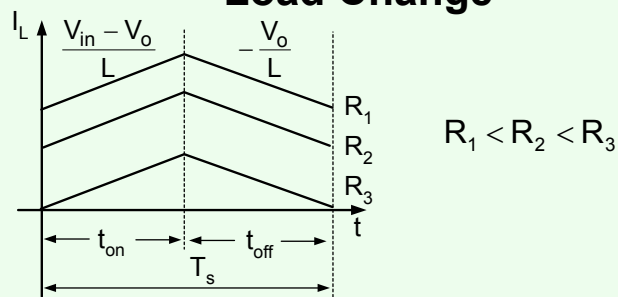

CCM - Continues Conductor Current Mode


DCM - Discontinues Conductor Current Mode

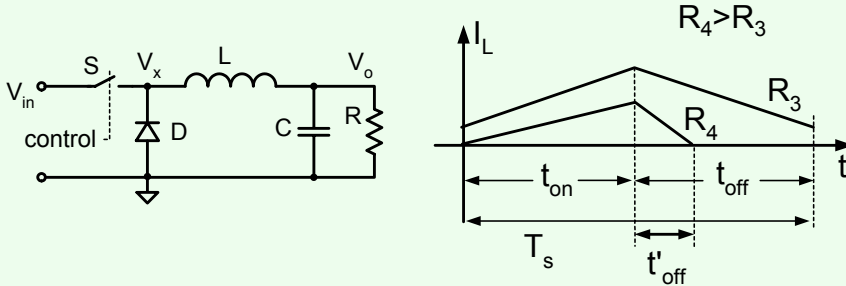Discontinuous Inductor Current Mode (DCM)



- Different voltage transfer ratio $\neq D_{on}$
- Higher ripple current

Voltage transfer function (DCM)

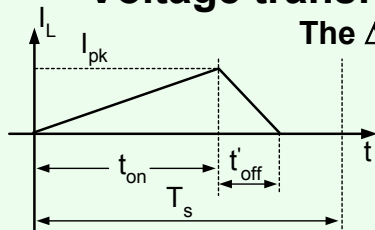

The ΔI method

$$I_{pk} = \frac{V_{in} - V_o}{L} t_{on} = \frac{V_o}{L} t'_{off}$$

$$D_{off} = \frac{(V_{in} - V_o) D_{on}}{V_o}$$

$$I_{AV} = \frac{1}{T_s} \left(\frac{1}{2} \frac{V_{in} - V_o}{L} T_{on} \cdot T_s (D_{on} + D_{off}) \right)$$


$$I_{AV} = \frac{1}{2} \frac{V_{in} - V_o}{L} T_{on} \cdot D_{on} \left(1 + \frac{V_{in} - V_o}{V_o} \right)$$

$$I_{AV} = \frac{V_o}{R}$$

$$\longrightarrow R(V_{in} - V_o) D_{on}^2 T_s V_{in} = 2L V_o^2$$

$$\frac{V_o}{V_{in}} = \frac{R D_{on}^2 T_s}{4L} \left(\sqrt{1 + \frac{8L}{R D_{on}^2 T_s}} - 1 \right)$$

Boundary of CCM and DCM

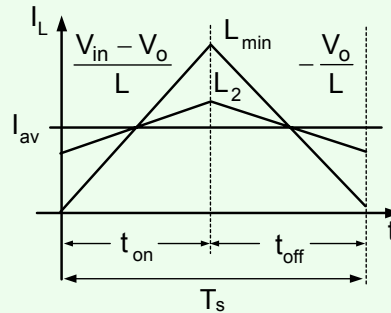

- For CCM $L > L_{min}$

- In Buck $\frac{V_o}{L_{min}} t_{off} = I_{pk} = 2I_{av}$ $L_{min} = \frac{V_o D_{off}}{2I_{av} f_s} = \frac{RD_{off}}{2f_s}$

Example

A BUCK converter has a following characteristics:

Output voltage: $V_o = 5V$ Output current: $I_{out} = I_{av} = 10A$

Input voltage: $V_{in} = 10V$ Frequency: $f_s = 100kHz$



Current mode: CCM

Find: L_{min}


$$\frac{V_o}{V_{in}} = D_{on} = 0.5 \quad \xrightarrow{\text{CCM}} \quad D_{off} = 1 - D_{on} = 0.5$$

$$L_{min} = \frac{V_o D_{off}}{2I_{av} f_s} = \frac{5 \cdot 0.5}{2 \cdot 10 \cdot 10^5} = 1.2 \mu H$$


Capacitor current

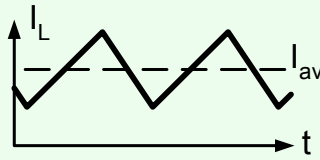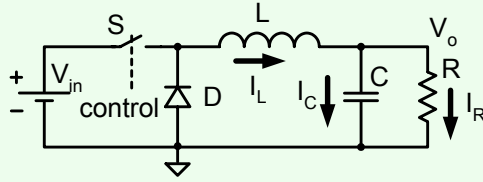


- Assumption:
 V_o has small ripple

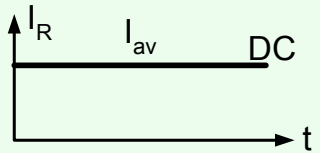

$$I_C = I_L - I_R$$

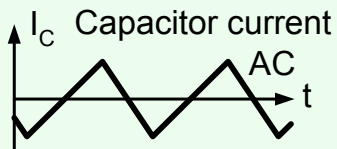



BOOST Step-Up

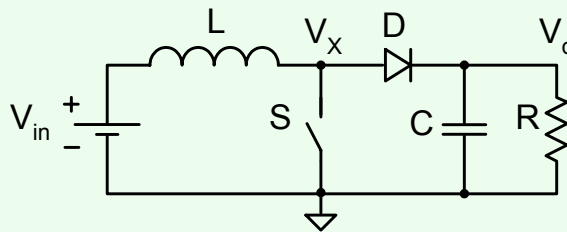



- $V_o > V_{in}$ Why ??

OperaBoostodes

ON $V_L = V_{in}$

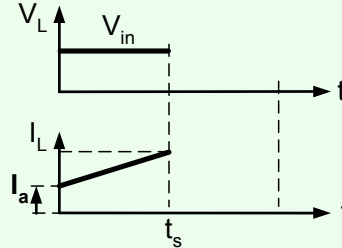
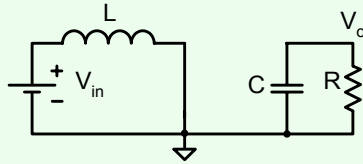


OFF $V_L = V_{in} - V_o$

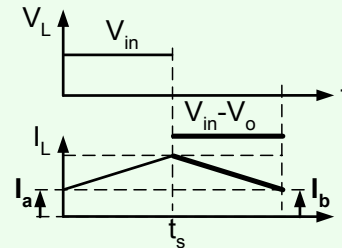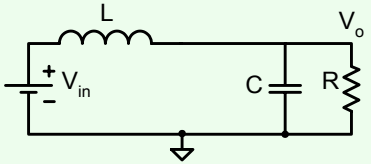

Voltage transfer function

The average voltage method

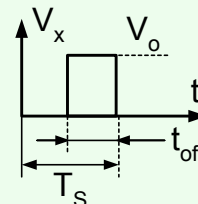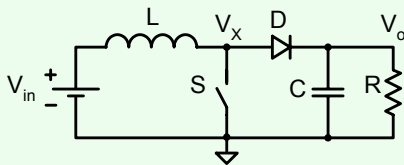

$$\bar{V}_L = 0; \quad \bar{V}_{in} - \bar{V}_x = 0; \quad \bar{V}_{in} = \bar{V}_x;$$



$$V_{in} = \bar{V}_{in};$$

$$\bar{V}_x = \frac{V_o t_{off}}{T_s} = V_o D_{off};$$

$$V_{in} = V_o D_{off} \rightarrow \frac{V_o}{V_{in}} = \frac{1}{D_{off}}$$

Voltage transfer function

The ΔI method

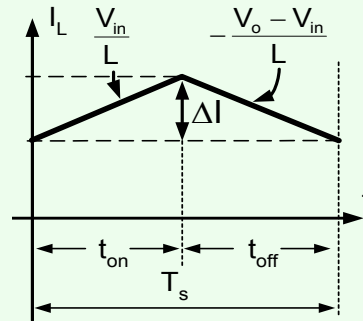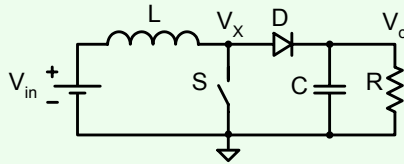


$$\frac{V_{in}}{L} \cdot t_{on} = \frac{V_o - V_{in}}{L} \cdot t_{off}$$

$$V_{in} \cdot (t_{on} + t_{off}) = V_o \cdot t_{off}$$

$$\frac{V_o}{V_{in}} = \frac{1}{D_{off}}$$


BUCK-BOOST

Step-Up Step-Down

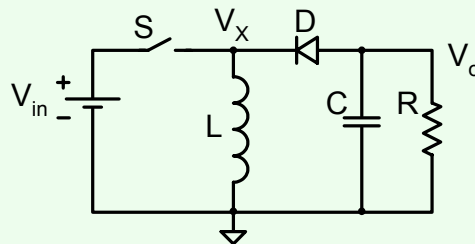


- Find V_o/V_{in}
Hint: Average of V_x ?

Comparison between basic topologies CCM

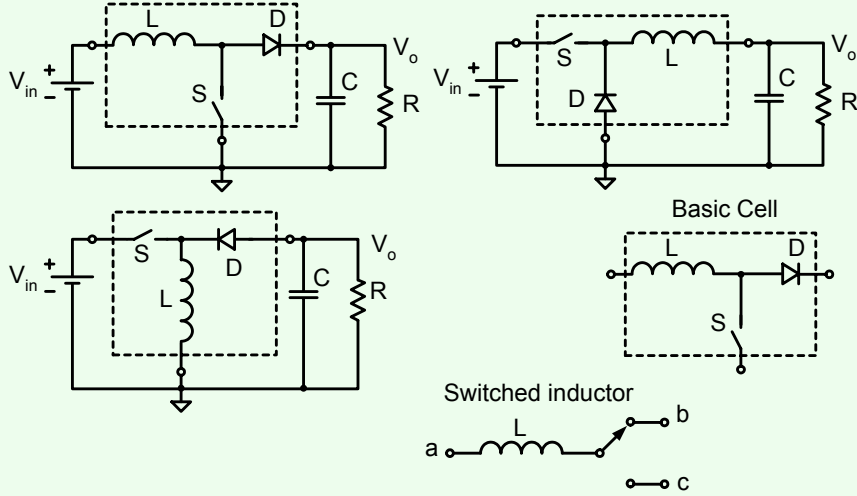


Input and Output Currents

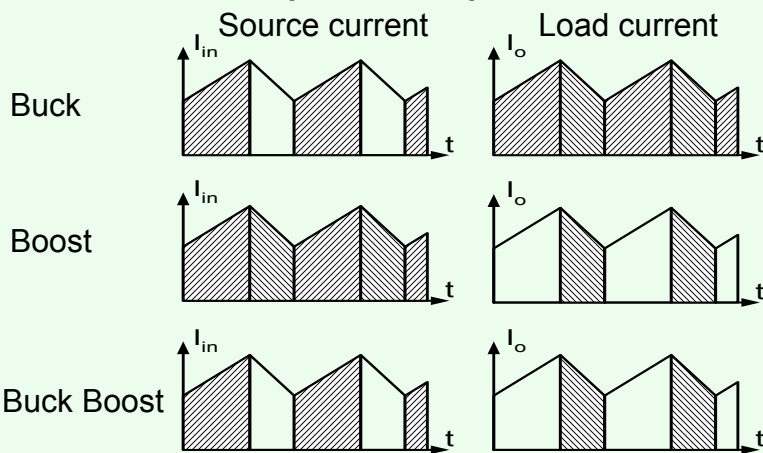


Continues current -> Low ripple component

Discontinues current -> High ripple component

The simulation problem

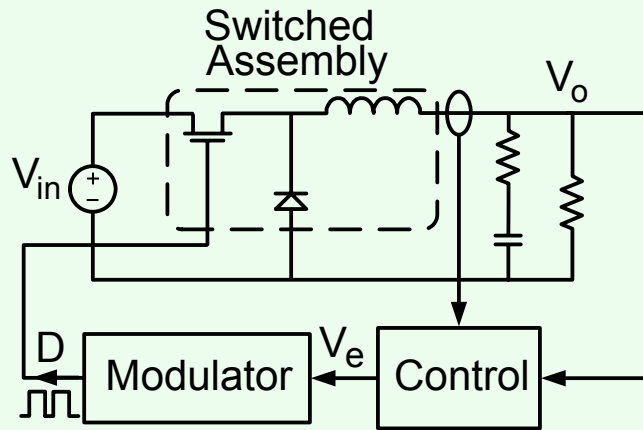


The simulation problem

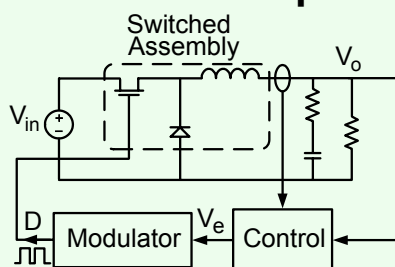


- The problematic part : Switched Assembly
- Rest of the circuit continuous - SPICE compatible
- Only possible simulation :
Time domain (cycle-by-cycle) - Transient
- The objective : translate the
Switched Assembly into an equivalent
circuit which is SPICE compatible

Average Simulation of PWM Converters

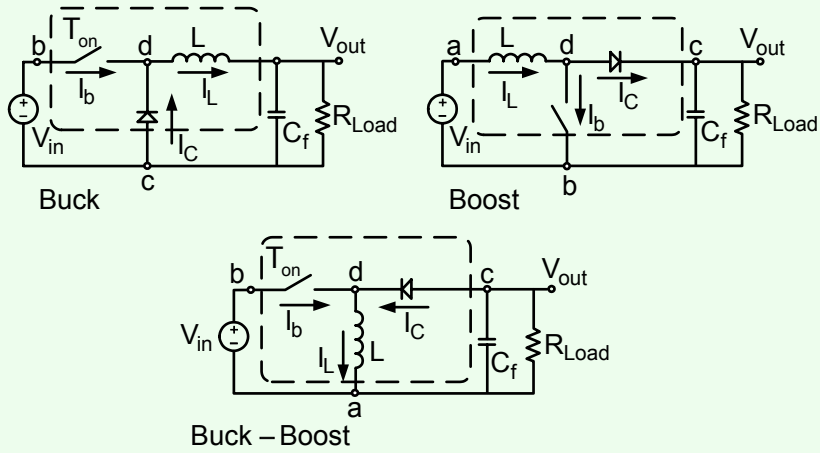


The Switched Inductor Model

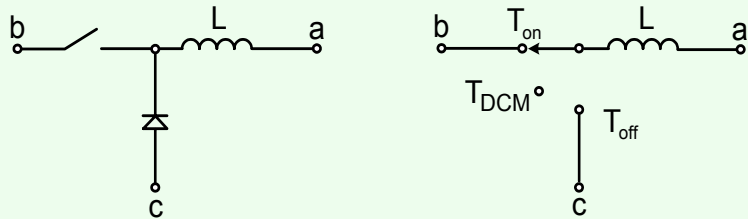

T_{on} - switch conduction time
 T_{off} - diode conduction time
 T_{DCM} - no current time (in DCM)


The Switched Inductor Model (SIM) (CCM)

The concept of average signals

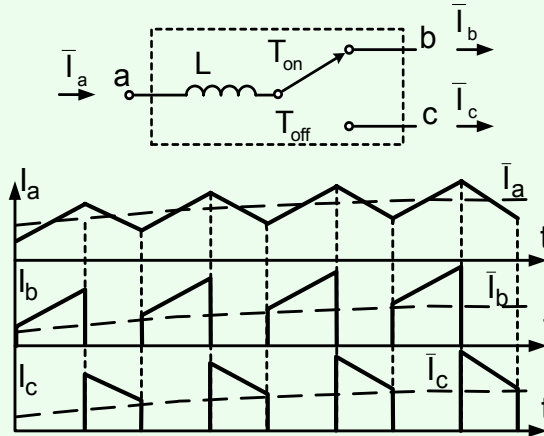


The SIM

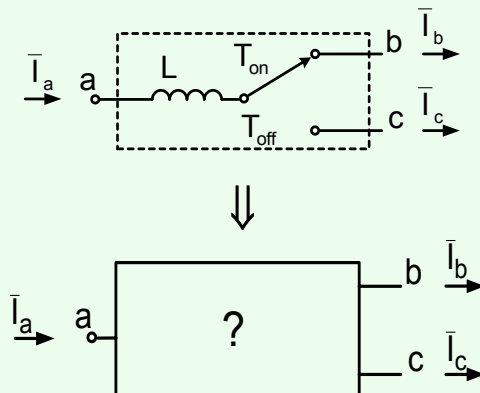Objective : To replace the switched part by a continuous network




Average current


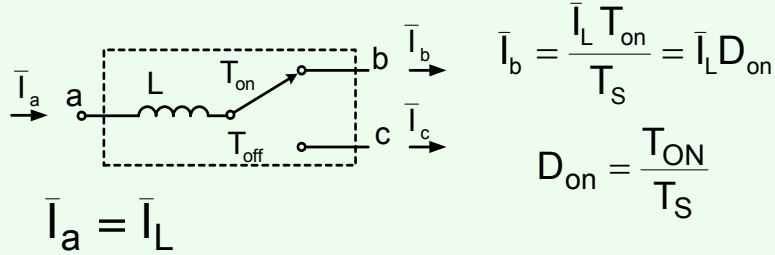


Similarly :
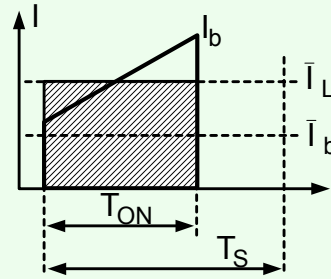
$$\bar{I}_c = \frac{\bar{I}_L T_{off}}{T_S} = \bar{I}_L D_{off}$$



Toward a continuous model

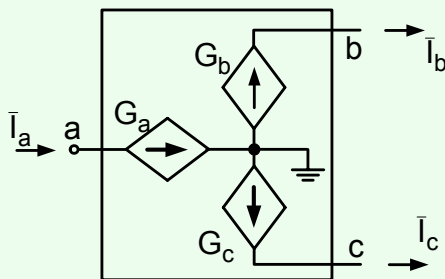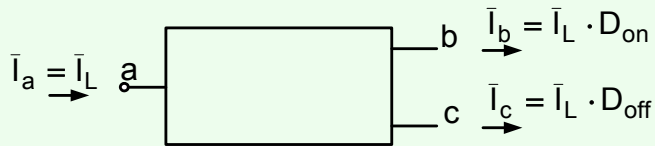

G_a, G_b, G_c - current dependent sources

$$G_a \equiv \bar{I}_L$$


$$G_b \equiv \bar{I}_L \cdot D_{on}$$

$$G_c \equiv \bar{I}_L \cdot D_{off}$$


Average inductor current

Deriving \bar{I}_L
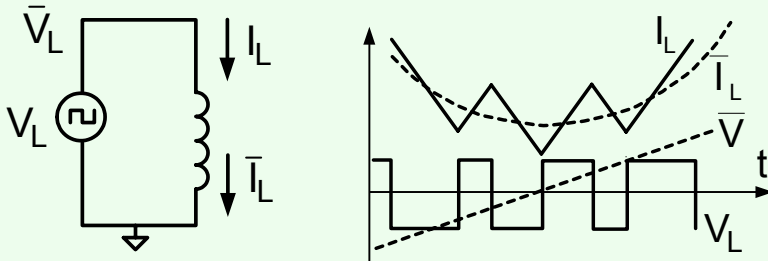
$$\frac{di_L}{dt} = \frac{V_L}{L} \Rightarrow \frac{d\bar{I}_L}{dt} = \frac{\bar{V}_L}{L}$$




Average inductor current

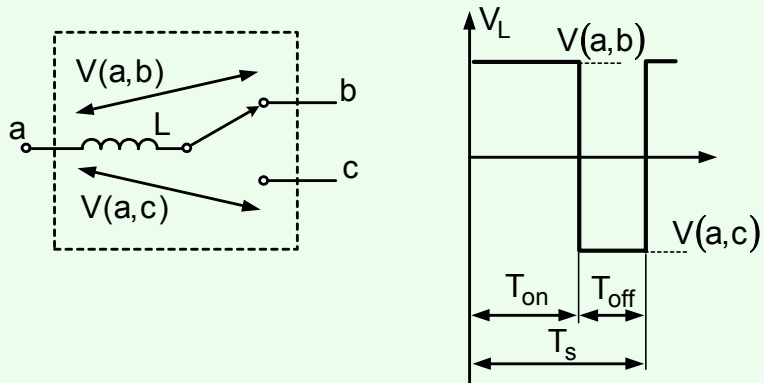

$$\begin{aligned} \bar{V}_L &= \frac{V(a,b) \cdot T_{on} + V(a,c) \cdot T_{off}}{T_s} = \\ &= V(a,b) \cdot D_{on} + V(a,c) \cdot D_{off} \end{aligned}$$

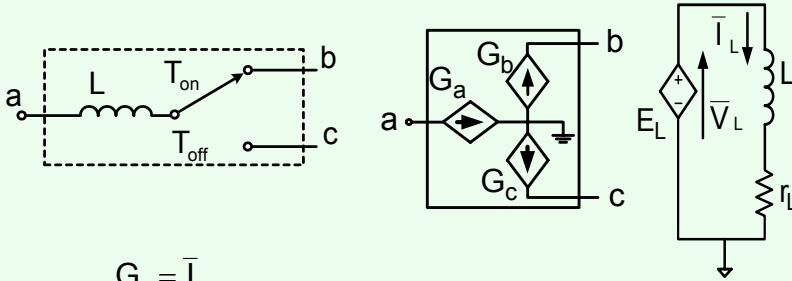The Generalized Switched Inductor Model (GSIM)



$$G_a = \bar{I}_L$$

$$G_b = \bar{I}_L \cdot D_{on}$$


$$G_c = \bar{I}_L \cdot D_{off}$$

$$E_L = V(a,b) \cdot D_{on} + V(a,c) \cdot D_{off}$$

Topology independent !

Example Implementation in Buck Topology

1. The formal approach

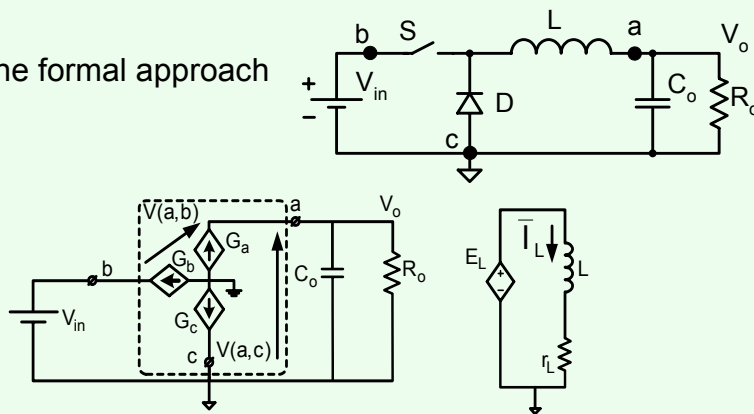


$$G_a = \bar{I}(L) \quad G_b = \bar{I}(L) \cdot D_{on} \quad G_c = \bar{I}(L) \cdot D_{off}$$

$$E_L = [V_o - V_{in}] \cdot D_{on} + [0 - V_o] \cdot D_{off}$$

Implementation in Buck Topology

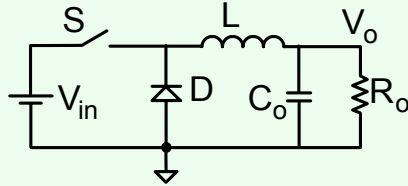
2. The intuitive approach - by inspection



$$E_{in} = V_{in} \cdot D_{on}$$



$$G_b = \bar{I}_L \cdot D_{on}$$

$$E_{in} - V_o \rightarrow \bar{V}_L$$

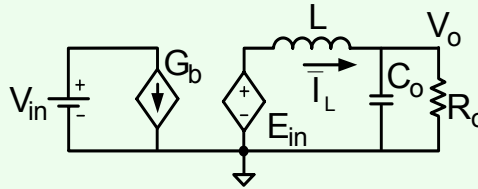



Polarity: (voltage and current sources) selected by inspection

Boost

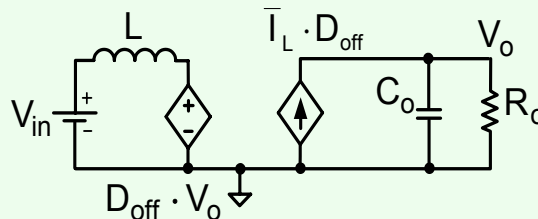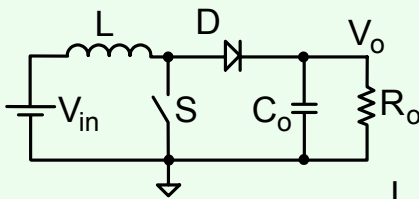


- Emulate average voltage on inductor
- Create \bar{I}_L dependent current sources


Buck-Boost

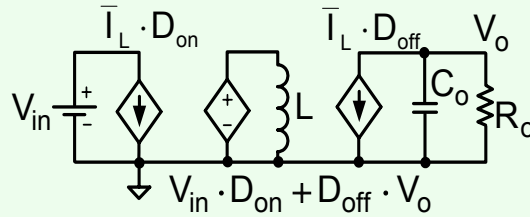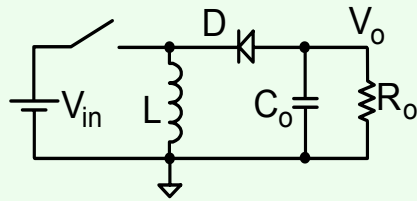

Partially accounting for parasitics

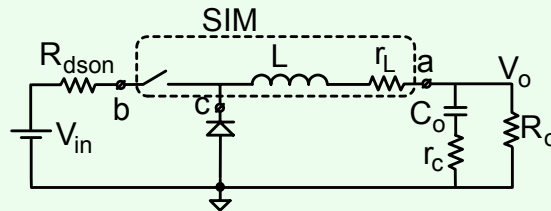

Modified Average Model

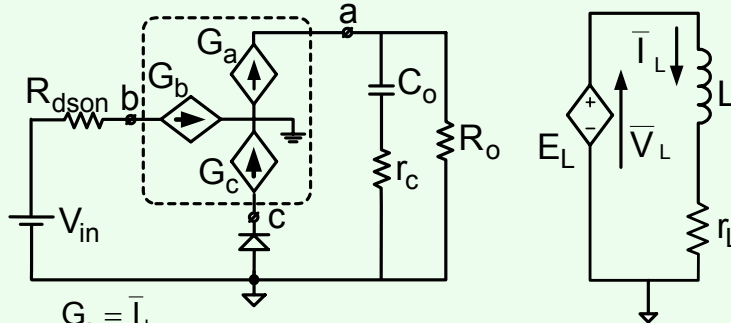

$$G_a = \bar{I}_L$$

$$G_b = \bar{I}_L \cdot D_{on}$$

$$G_c = \bar{I}_L \cdot D_{off}$$


$$E_L = (V_a - V_b) \cdot D_{on} + (V_a - V_c) \cdot D_{off}$$

Making the model SPICE compatible



I_L and D_{on} are time dependent variables $\{I_L(t), D_{on}(t)\}$
 D_{on} is not an electrical variable

In SPICE environment

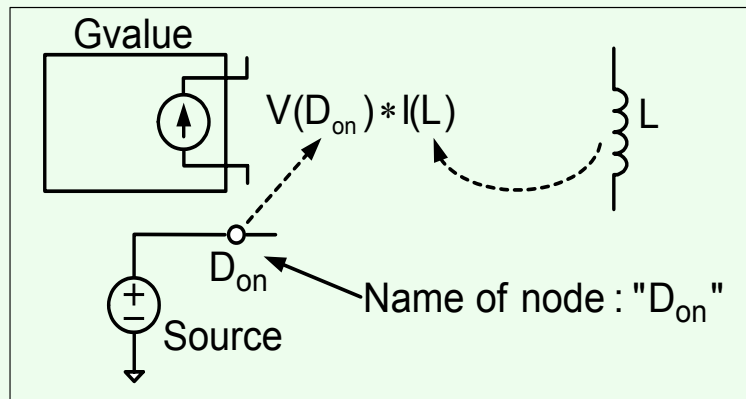

D_{on} is coded into voltage

Simulation

Running SPICE simulation


DC (steady state points) - as is

TRAN (time domain) - as is

AC (small signal) - as is


* Linearization is done by simulator !

Discontinuous Model (DCM)

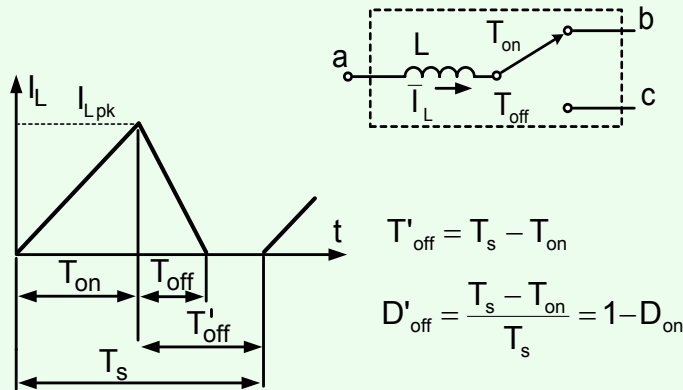



Combining CCM / DCM

1. The average inductor current in DCM

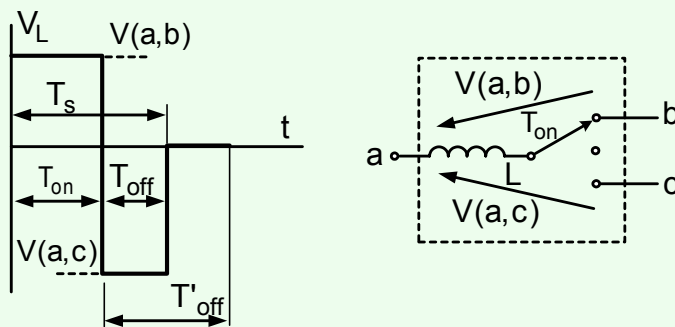

$$\bar{V}_L = V(a,b)D_{on} + V(a,c)D_{off} \text{ as in CCM}$$



Combining CCM / DCM

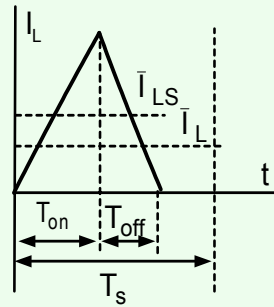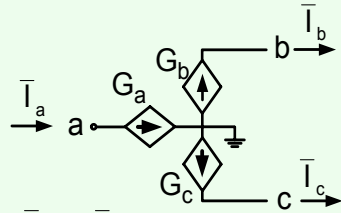

- * \bar{I}_a is \bar{I}_L
- * \bar{I}_b is sampled during T_{on}
- * \bar{I}_c is sampled during T_{off}
- * \bar{I}_b is \bar{I}_c are sampling \bar{I}_{Ls}

$$\bar{I}_{Ls} = \frac{\bar{I}_L T_s}{T_{on} + T_{off}} = \frac{\bar{I}_L}{D_{on} + D_{off}}$$

Combining CCM / DCM

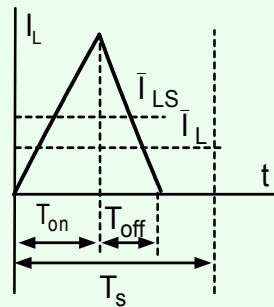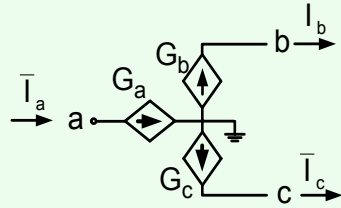

$$G_a = \bar{I}_L$$

$$G_b = \frac{\bar{I}_L D_{on}}{D_{on} + D_{off}}$$

$$G_c = \frac{\bar{I}_L D_{off}}{D_{on} + D_{off}}$$

in CCM: $(D_{on} + D_{off}) = 1$

Doff in DCM

$$I_{pk} = \frac{V(a,b)T_{on}}{L}$$


$$\bar{I}_L = \frac{1}{2} \left(\frac{V(a,b)T_{on}}{L} \right) \frac{(T_{on} + T_{off})}{T_s}$$

$$\bar{I}_L = \frac{V(a,b)D_{on}}{2Lf_s} (D_{on} + D_{off})$$


$$D_{off} = \frac{2\bar{I}_L L f_s}{V(a,b)D_{on}} - D_{on}$$

$$D'_{off} = 1 - D_{on}$$

$$D_{off} \leq 1 - D_{on}$$

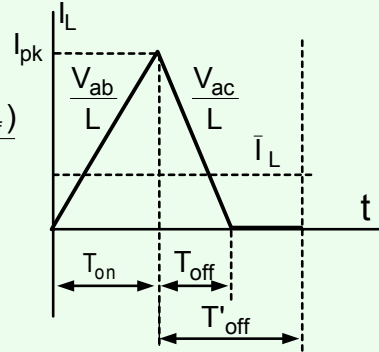

The combined DCM / CCM mode

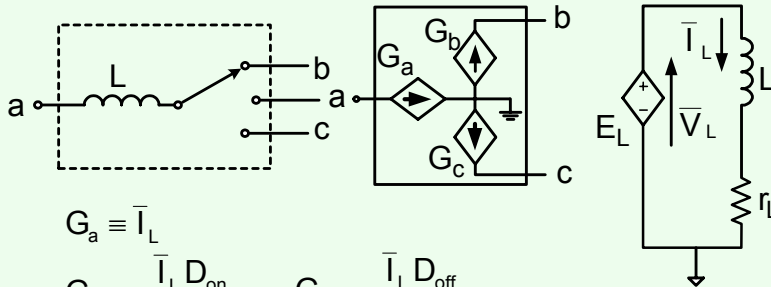

$$G_a \equiv \bar{I}_L$$


$$G_b \equiv \frac{\bar{I}_L D_{on}}{D_{on} + D_{off}}$$

$$G_c \equiv \frac{\bar{I}_L D_{off}}{D_{on} + D_{off}}$$

$$E_L = V(a,b) \cdot D_{on} + V(a,c) \cdot D_{off}$$

$$D_{off} = \min \left\{ (1 - D_{on}), \left(\frac{2\bar{I}_L L f_s}{V(a,b)D_{on}} - D_{on} \right) \right\}$$

Example: Boost average model simulation

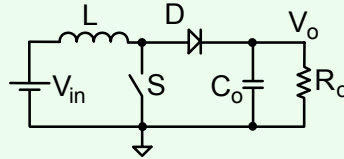


PARAMETERS:
VIN_DC = 10v
VDON = 0.5


PARAMETERS:
LMAIN = 75u
COUT = 220u
RLOAD = 10

PARAMETERS:
RESR = 0.07
RINDUCTOR = 0.1
RSW = 0.1



PARAMETERS:
FS = 100k
TS = {1/fs}

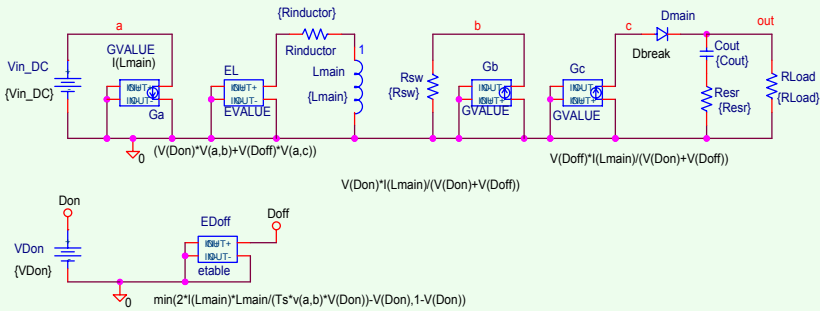



Example: Boost average model simulation

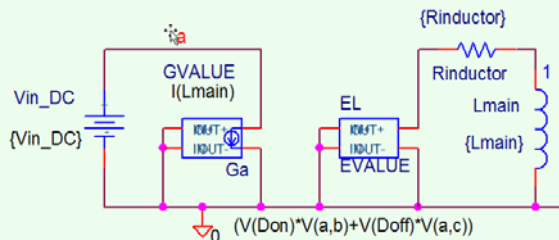


Example: Boost average model simulation

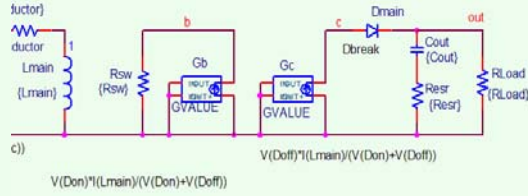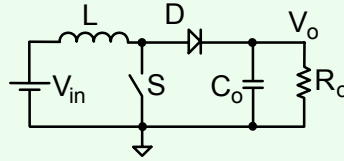


Example: Boost average model simulation

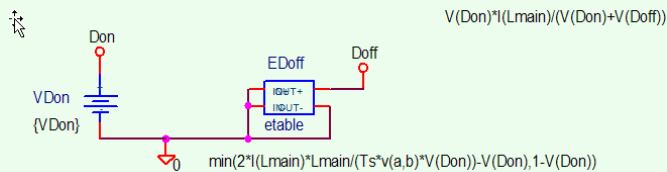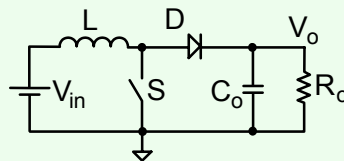

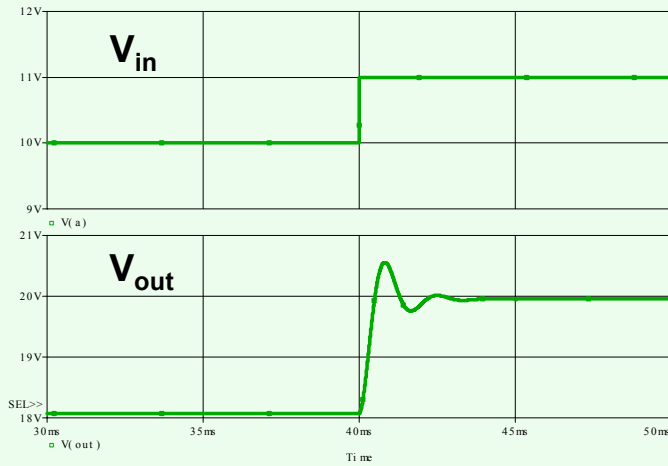Boost: Response to step of input voltage (average model simulation)



Boost: Response to step of duty cycle

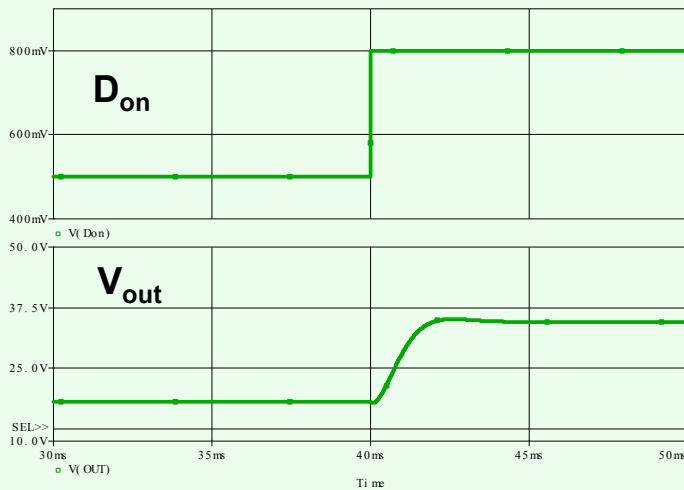

Boost transfer function (CCM)

DC Sweep simulation

