

### Current Sensing

- 9.1 Resistor
- 9.2 Current transformer

---

---

---

---

---

---


---

---

### Current Sensing



- \* Control PCM, ACM
- \* Protection

Sense Resistor

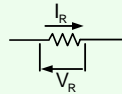

Problems

- \* Inductive component

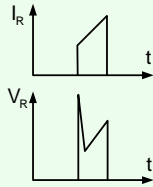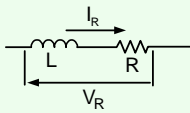


---

---

---

---

---

---

---

---

### Losses

$$P_d = RI_{Rms}^2 = V_{Rms}I_{Rms}$$

For a reasonable  $\frac{S}{N}$   $V_R \approx 100mV$  at least

Assuming  $V_R, V_{Rms}$  same order of magnitude

$$P_d \approx 0.1 I_{Rms}$$

$$I_{rms} = 10 A \quad P_d \approx 1 W$$

Not practical for  $I > 10A$

---

---

---

---


---

---

---

---

### Current transformer

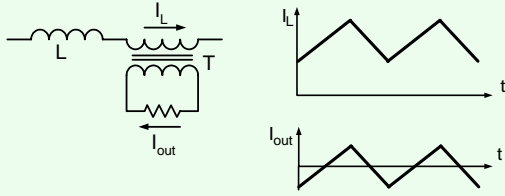

DC component via primary lost !  
 DC component may saturate transformer !

---

---

---

---



---

---

---

---

### Current Transformer

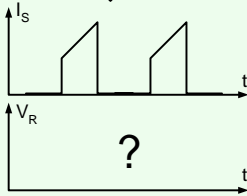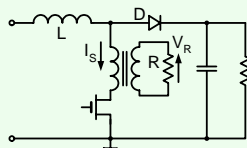


---

---

---

---



---

---

---

---

### Current Transformer

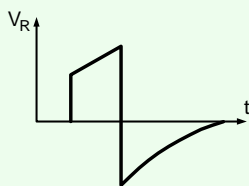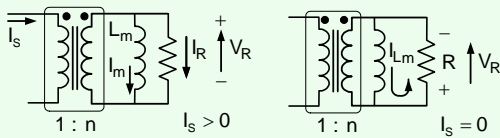


---

---

---

---

---

---

---

---

### Conclusions

- Linear Current transformers are useful only if current to be measured is AC
- In Power Electronics, Pulse Current transformer is useful for measuring pulsed current

---

---

---

---


---

---

---

---

### Pulse Current transformer Design

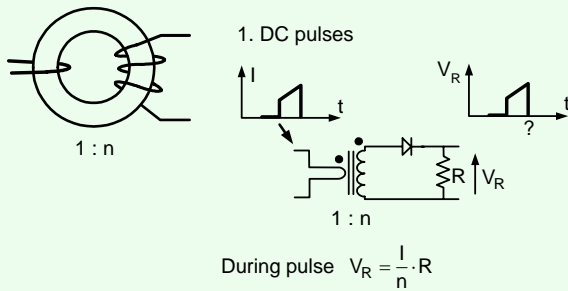


---

---

---

---


---

---

---

---

### Resistor reset

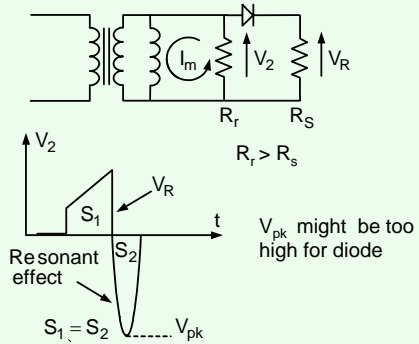


---

---

---

---


---

---


---

---

**Reset**

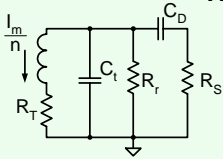

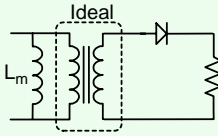$C_i$  - Transformer capacitance  
 $C_D$  - Diode capacitance  
 $R_T$  - Transformer Resistance



Sometime no resistor is used.

---

---

---

---



---

---

---

---

**Reset - Clamp**

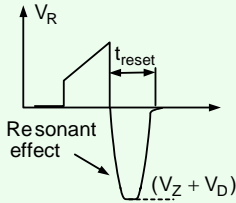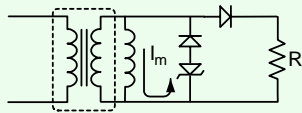

$t_{reset} < t_{off}$

---

---

---

---

---


---

---


---

**Place to put current transformer**

O.K.

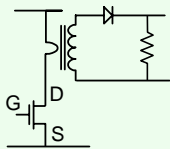

avoid

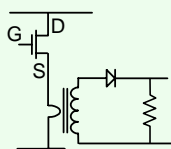

Why ?

---

---

---

---

---



---

---

---
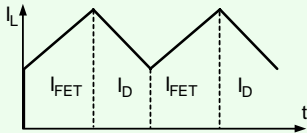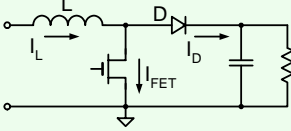
### Measuring "DC" current with pulse current transformer

Need to measure  $I_L$   $I_L = I_D + I_{FET}$




---

---

---

---

---

---



---

---

---

---

### Inductor DC Current

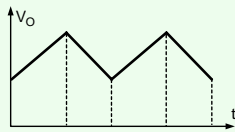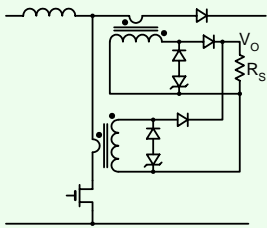

Long wire for illustration only

---

---

---

---

---

---


---

---

---

---

### Problem

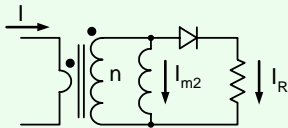

$$\frac{I}{n} = I_{m2} + I_R$$

$I_{m2}$  must be smaller than  $I_R$  or  $2\pi f_s L_m > R$   
This becomes a problem at low frequencies

---

---

---

---

---

---


---

---

---

---

### Design of current transformer

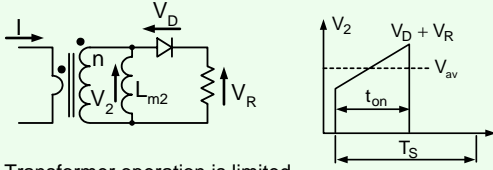

Transformer operation is limited by voltage NOT CURRENT

$$B_{max} = \frac{\int V dt}{nA_e} \quad V_R \cong \frac{I}{n} R$$

$$B_{max} = \frac{I_{av} R D_{max}}{nA_e f_s}$$

$$\int V dt = V_{av} t_{on} = \frac{V_{av} D_{on}}{f_s}$$

If  $I_{av}$  large need R small.  
Problem at low frequencies

---

---

---

---


---

---

---

---

### DC Current transformer

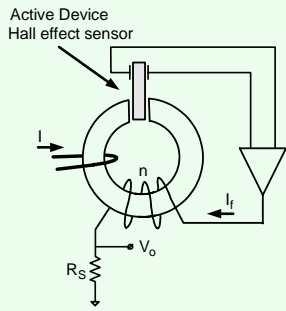

Null operation  $\Phi=0$   
by feedback

$$I_s \cdot n = I \quad V_o = \frac{I}{n} R_s$$

---

---

---

---

---

---

---

---