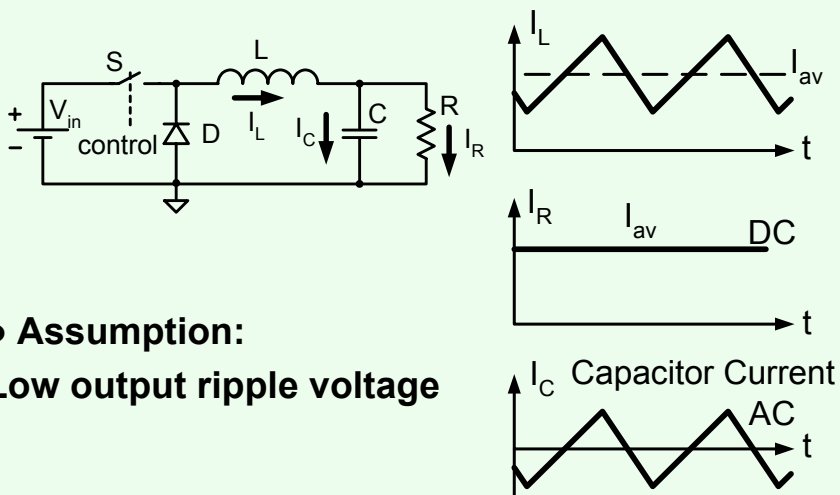


## Output Voltage Ripple, Parasitic Effects


- 6.1 Output voltage ripple (Buck)
- 6.2 Parasitic effects
  - 6.2.1 Diode recovery
  - 6.2.2 Internal delay of switching
  - 6.2.3 Stray and leakage inductances
    - Clamp
    - Diode snubber (clamp)
    - Switch snubbers

### Output voltage ripple



- **Assumption:**  
Low output ripple voltage

**Ripple**

 

$$\Delta V_C = \frac{\Delta Q}{C}; \quad \Delta Q = \int_{t_1}^{t_2} I_L dt; \quad \Delta V_C = \frac{\Delta I_L}{8C f_s}$$

$$\Delta Q = \frac{\Delta I_L}{2} \cdot \frac{T_s}{2} \cdot \frac{1}{2}; \quad \Delta Q = \frac{\Delta I_L}{8} T_s$$

**Ripple**

$$\Delta I_L = V_o t_{off} / L \quad \Delta I_L = \frac{V_o D_{off}}{L} T_s = \frac{V_o D_{off}}{L f_s}$$

$$\Delta V_C = \frac{V_o D_{off}}{C L f_s} \frac{1}{8 f_s} = \frac{V_o D_{off}}{8 C L f_s^2}$$


The effect of  $f_s$   $\Delta I = \frac{V_o D_{off}}{L f_s}$

$L; f_s$  can be traded for same  $\Delta I$   $\Delta V_C = \frac{\Delta I_L}{8 f_s C}$

$C; f_s$  can be traded for same  $\Delta I$  &  $\Delta V_C$   
 if  $f_s$  is increased for given  $L, C$   $\Delta V_C = \frac{V_o D_{off}}{8 L C f_s^2}$

$\Delta V_C$  goes down -40 db/dec (second order)

### Example

 

$\Delta I_L = 1A$   
 $C = 47 \mu F$   
 $T_s = 10 \mu S$   
 $ESR = 10 m\Omega$

Find the output voltage ripple  $\Delta V$


$$\Delta V_C = \frac{1A \cdot 10 \mu S}{8 \cdot 47 \mu F} = 25 mV$$

$$\Delta V_{ESR} = 10 m\Omega \cdot 1A = 10 mV$$

• Approximate (upper limit) of total ripple)

$$\Delta V = \Delta V_C + \Delta V_{ESR} = 25 mV + 10 mV = 35 mV$$

### Application of Simulation

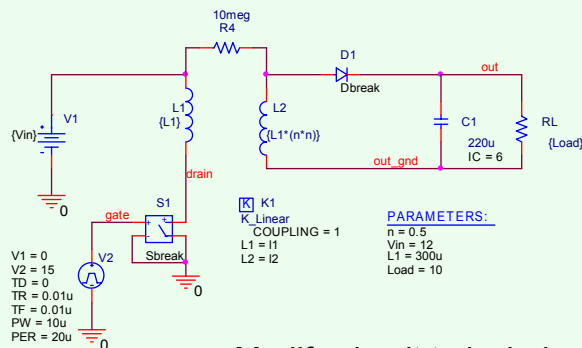


Modify circuit to include

ESR=100mΩ


Find ripple at output

## Diodes Recovery – Implications


 


Reverse current at switch turn on


- Soft and hard recovery

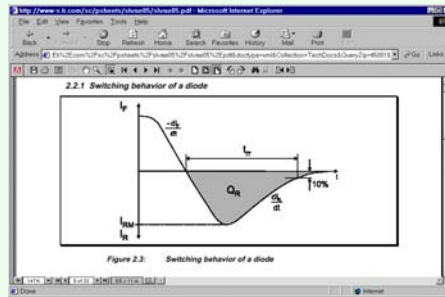


## Stages in diode recovery

  

### Turn "off" of transistor


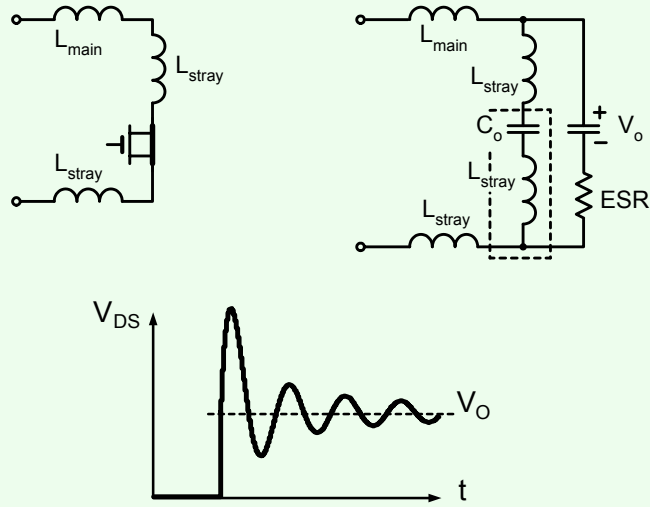


### Diode forward recovery

 

### Parasitic effects: Internal delay




To turn "on"

  


$$Q = \frac{\sqrt{L_{GS}}}{R_L + R_G} \sqrt{C_{GS}}$$

### Clamps

\* limiting maximum voltage

   


### Solutions

 

$$V_z > V_{in} + V_o' = V_{in} + nV_o$$

### Simple Example

 


Clamp B is better from the point of view of efficiency.

$$V_C(A) = V_{in} + V_o'$$

But ...

## Parasitic inductance

 


Energy of  $L_1 L_2 L_3 L_4$  will cause high spike on C (FET).  
The FET is not protected!


Rule:

Connect clamps and snubbers directly to the elements to be protected

## To protect FET

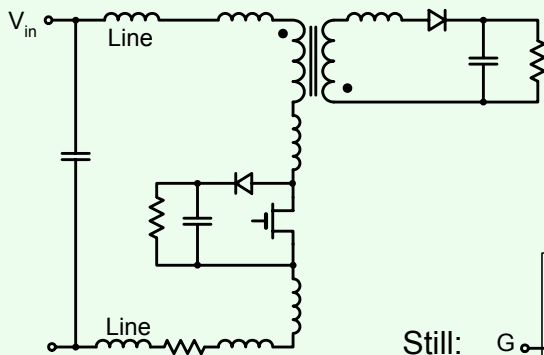


Still:


 





## Designing the Snubber Components

 


## Snubber

  

$$V_{Cc} > V_o'$$

 

## Leakage discharge

 

$$I_{p\ av} \cdot R_c = V_{C_{cav}}$$

$$R_c \cdot C_c = T > T_s$$

$$\frac{dl_p}{dt} = \frac{V_{C_{cav}} - V_o'}{L_{lkg}}$$

$$t_p = \frac{L_{lkg} I_{pk}}{V_{C_{cav}} - V_o'}$$


## Leakage average current

$$I_{pav} = \frac{I_{pk} \cdot t_p}{2} \cdot f_s$$

Procedure


1. Select  $V_{C_{cav}}$
2. Calculate  $I_{p\ av}$
3. Select  $R_c = \frac{V_{C_{cav}}}{I_{pav}}$
4. Select  $C_c \quad T > T_s$
5. Trim in-circuit

### Simulation Exercise

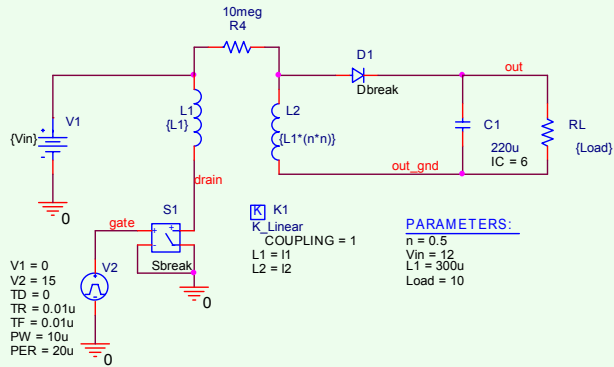


- Add 1uH leakage to Flyback converter. Design a clamp and check it by simulation.

### Diode Snubber (clamp)

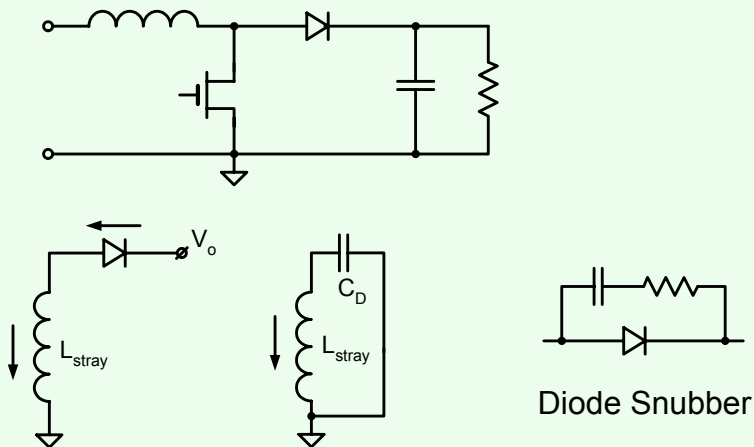

### Snubber waveforms

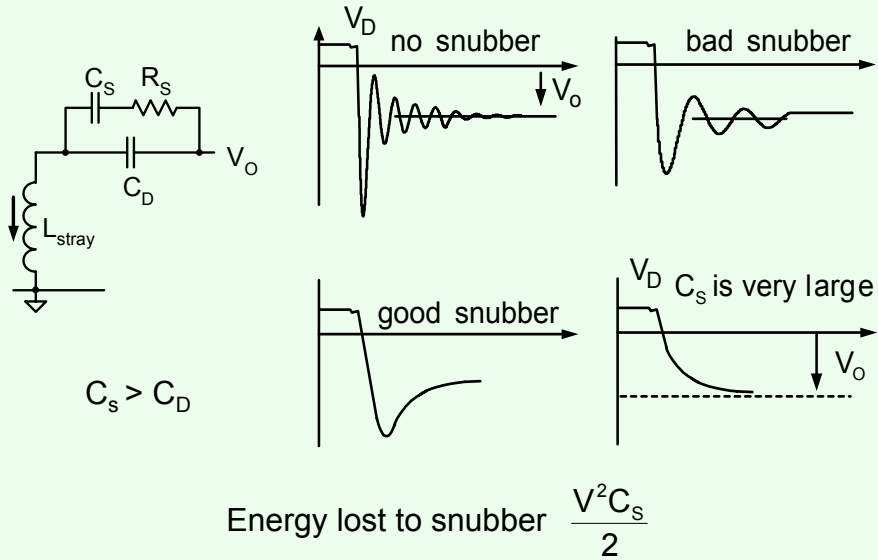


### Snubber design

Design - use simulation in circuit tuning

Needed information

$I_{pk}$  ( Reverse )


$L_{stray}$

 

$$\frac{L_{stray} I_{pk}^2}{2} \Rightarrow \text{moves to } C_s \Rightarrow V_o + \Delta V$$

$R_s \Rightarrow$  damping

## Switch Snubbers

 

Switching losses due to overlap  $P_d$  linear with  $f_s$  !

## Snubber types

Snubbers = control of  $\frac{dV}{dt}$  or  $\frac{dI}{dt}$

$\frac{dV}{dt}$  snubbers

$\frac{dI}{dt}$  snubbers

## Snubber types

Passive (dissipative) snubber

\* Energy lost to heat

Non-dissipative (lossless) snubber

\* Energy recovered


Passive Snubbers

\* by passive network


Active snubbers

\* by auxiliary active devices


## Switching overlap

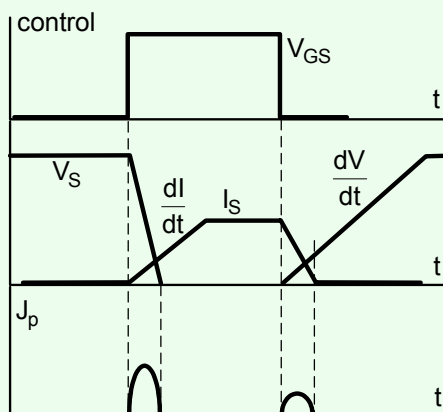

## Switch Snubber

 

 $dV/dt$  (at turn off) can be slow down by adding external snubber capacitor C



## $dV/dt$

$$\frac{dV}{dt} = \frac{I}{C + C_{dss}}$$


$C_{dss}$  - output capacitance of FET

$$I = 1 \text{ Amp}$$

$$C + C_{dss} = 1\text{nF}$$

$$\frac{dV}{dt} = \frac{1}{10^{-9}} = \frac{10^3}{10^{-6}} = 1 \text{ kV}/\mu\text{S}$$

### Capacitor losses


 


Problem at turn on !  $E_c = \frac{CV_o^2}{2} \text{ (J)}$   $P_d = \frac{CV_o^2}{2} \cdot f_s$

Example :  $V_o = 400 \text{ V}$   $C = 1 \text{ nF}$   
 $f_s = 100 \text{ kHz}$


$$P_d = \frac{10^{-9} \cdot 16 \cdot 10^4}{2} \cdot 10^5 = 8 \text{ W}$$

### Solution

  




## Reset

 

If  $R_{ds\ on} < R_s$  most energy will be lost to  $R_s \rightarrow$  Heat  
 Selection of  $C_s \rightarrow$   
 Selection of  $R_s \rightarrow$  to ensure reset

$$T = \frac{1}{R_s C_s} \ll t_{on} \quad t_{on} \approx 4R_s C_s$$


## $\frac{CV^2}{2}$ Losses

 


$$\left[ \frac{C_{dss} V_{max}^2}{2} \right] f_s \rightarrow \text{lost to heat}$$

Linear with  $f_s$  !  
 Switching losses (overlap) also  
 linear with  $f_s$  !

## Lossless snubbing (simple example)

 

 $C_1, C_2$  of transistor plus external (if any)



## Dead time requirement

