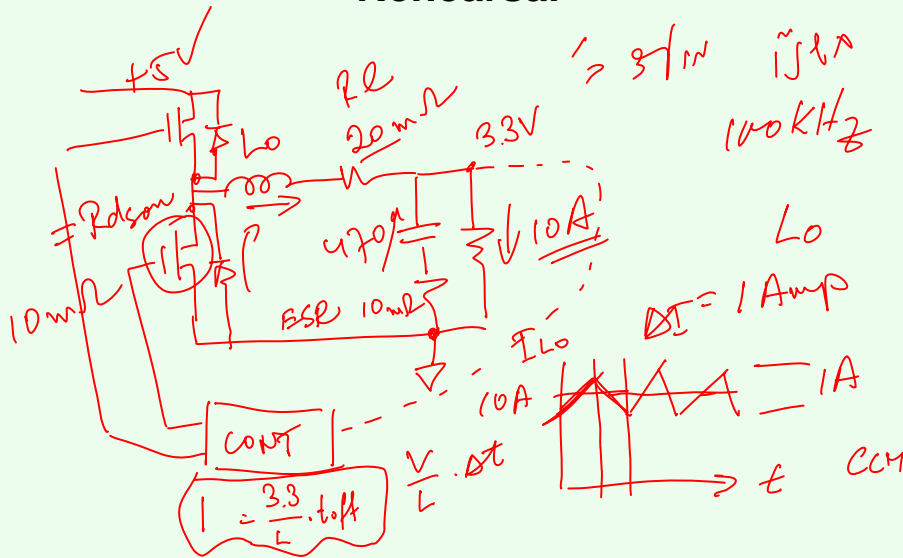


### Rehearsal



$$\frac{V_o}{V_{in}} = D_{on}$$

$$3.3 = \frac{5}{5} \cdot D_{on}$$

$$3.3 \cdot 3.4 \mu = I$$

$$L = 3.3 \cdot 3.4 \mu \approx 10 \mu H$$

$$R = \frac{V}{I} = \frac{3.3}{10} = 0.33 \Omega$$

$$t_{on} = D_{on} \cdot 10 \mu S$$



$$t_{on} = \frac{3.3}{5} \cdot 10 = 6.6 \mu$$



$$t_{off} = 3.4 \mu S$$



$$\frac{1}{\omega C} = \frac{1}{2\pi \cdot 10^4 \cdot 470}$$



$\Delta V = \frac{\Delta Q}{C}$   
 $\Delta Q = \frac{1}{2} \Delta I \frac{1}{2} \Delta t \frac{1}{2}$   
 $h.b \frac{1}{2}$   
 $V_{ripp} = \frac{1 \cdot 10\mu}{8}$   
 $\Delta V = \frac{1.25}{470} \cdot \frac{2.5}{103} \approx 2.5mV$   
 $\Delta Q = \frac{\Delta I \cdot 10\mu}{8}$   
 $V_{ripp\ mV} \approx 12mV$

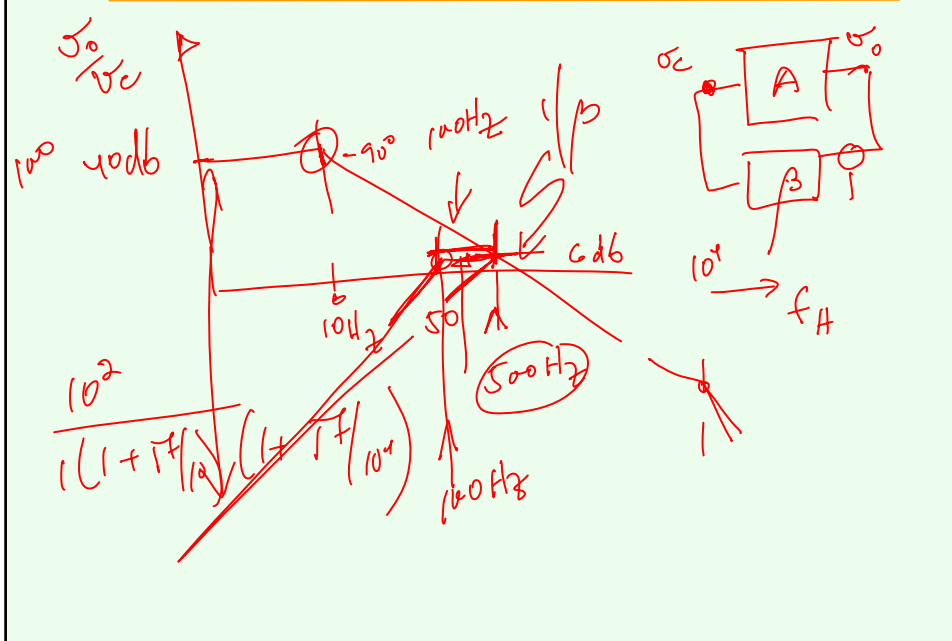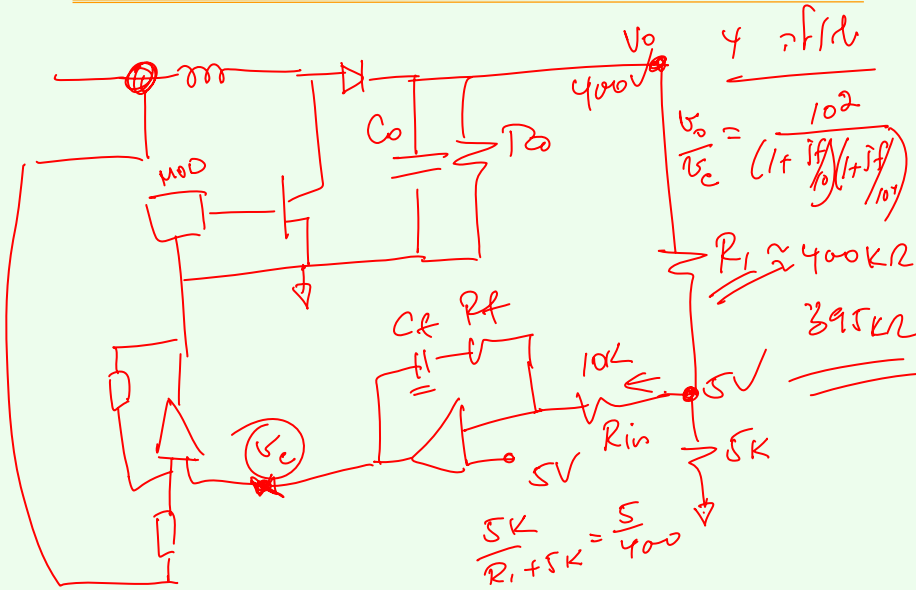$P_0 = 3.3 \cdot 10 = 33W$   
 $100 \cdot 20 \cdot 10^{-3} = 2W$   
 $100 \cdot 10 \cdot 10^{-3} = 1W$   
 $\left(\frac{1}{2}\right) \frac{1}{3} \cdot 10 \cdot 10^{-3} = 1mW$   
 $\eta = \frac{P_0}{P_n} = \frac{33}{36}$   
 $\left(\frac{1}{2}\right) \frac{1}{3}$



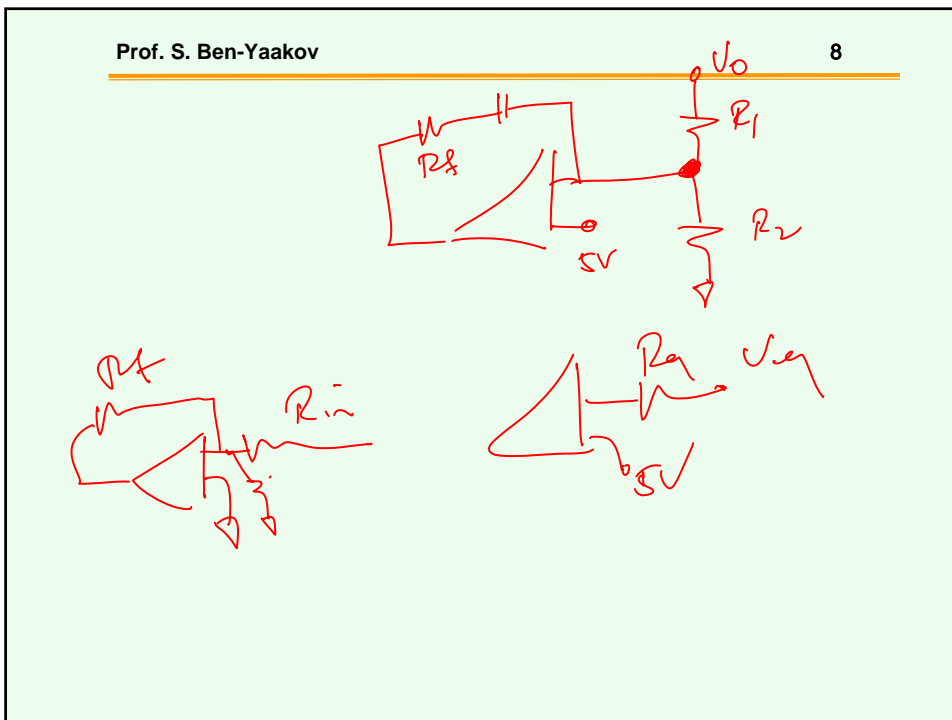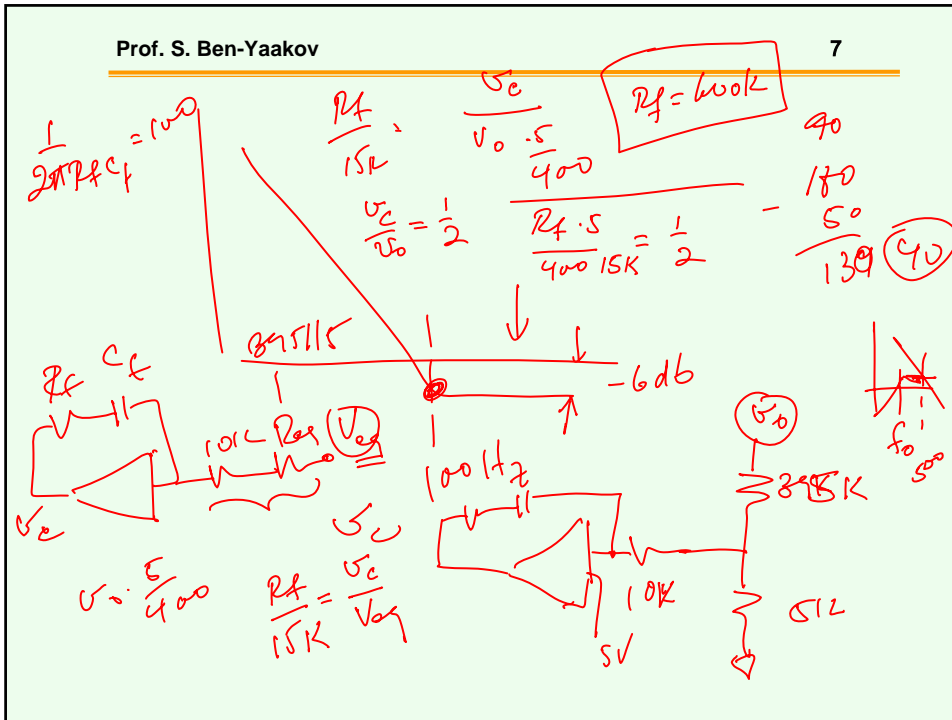

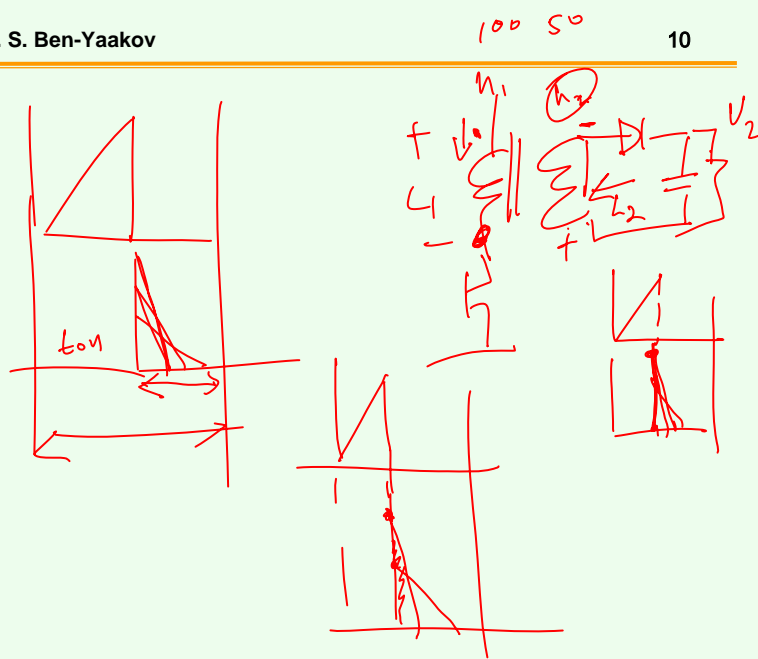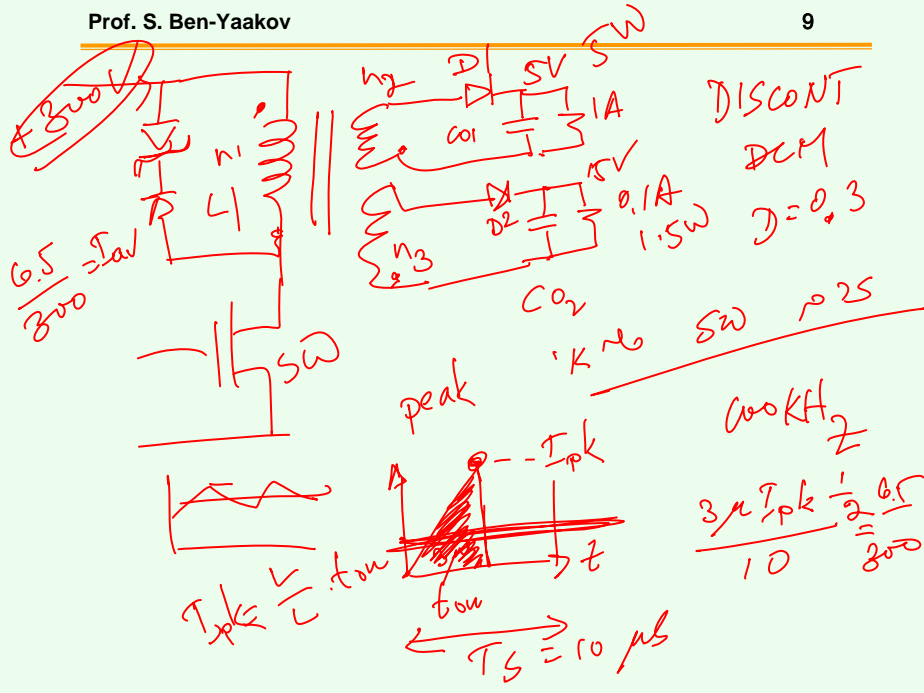

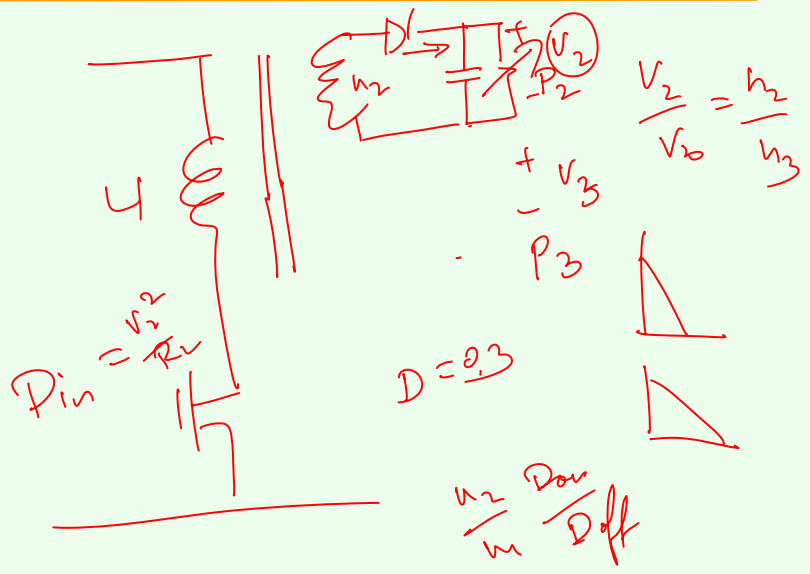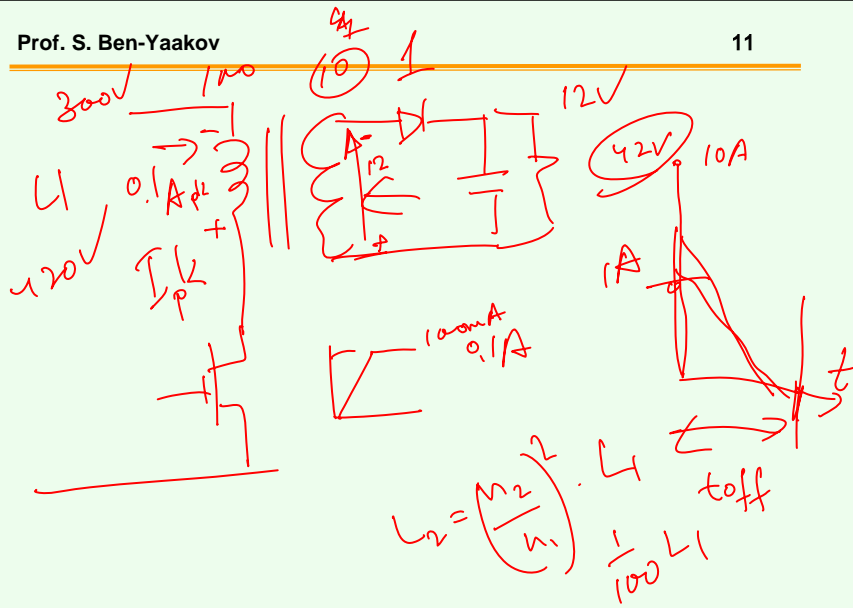

$\mu_n = 600 \text{ cm}^2/\text{Vs}$   $n_i = ?$   
 $l_e = 5 \text{ cm}$   
 $A_e = 0.5 \text{ cm}^2$

$L_1 = \frac{n_i^2 \mu_n A_e}{l_e}$

